

(2 pts) Name:

---

**AME 3623: Embedded Real-Time Systems**

**Midterm Exam**

**Solution Set**

March 9, 2006


Problem	Topic	Max	Grade
0	-	2	
1	Digital Logic	37	
2	Number Systems	15	
3	Sequential Logic and Finite State Machines	20	
4	Memory	10	
5	Microcontroller I/O	18	
Total			

---

1. Digital Logic

(37 pts)

Given the following circuit:

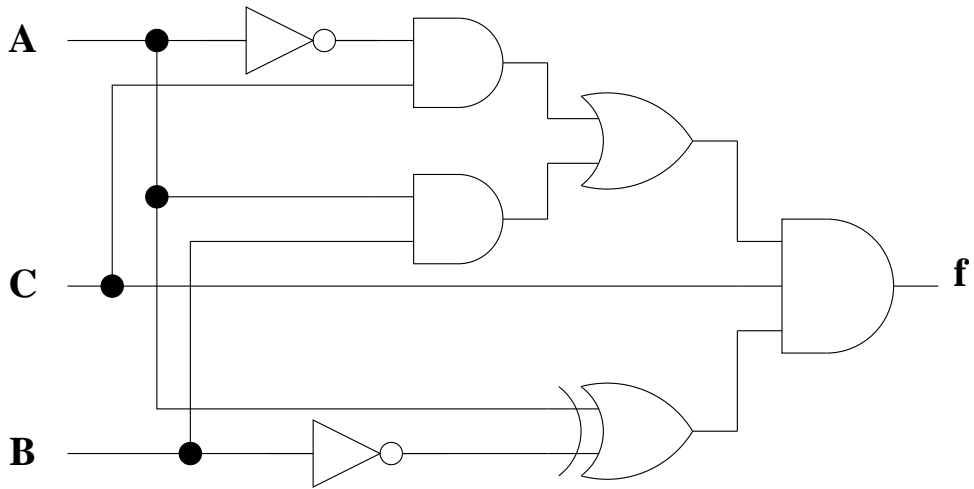

(a) (10 pts) Show the corresponding truth table.

<i>A</i>	<i>B</i>	<i>C</i>	<i>f</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

*Observations: C = 0 implies that f = 0. A ≠ B implies that f = 0.*

Given the following truth table:

A	B	C	D	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0


(b) (7 pts) Give the Karnaugh map and show the clusters.

		A			
		B			
CD	AB	00	01	11	10
	D	00	1	1	0
01		1	1	0	0
C	11	0	0	0	0
	10	1	0	0	1

(c) (5 pts) What is the corresponding algebraic description for  $f$  (that comes directly from the clusters)?

$$f = \overline{A}\overline{C} + \overline{B}\overline{D}$$

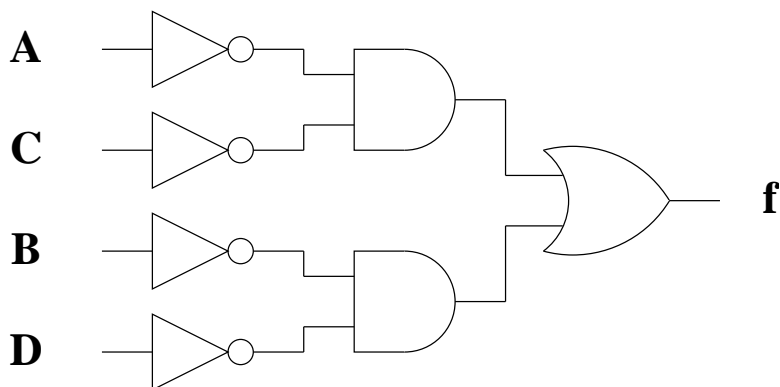(d) (5 pts) Draw the corresponding circuit.



(e) (10 pts) Prove that  $A \oplus \overline{B} = \overline{A \oplus B}$

$$\begin{aligned}
 A \oplus \overline{B} &= A\overline{\overline{B}} + \overline{A}\overline{B} && \text{XOR definition} \\
 &= AB + \overline{A}\overline{B} && X = \overline{\overline{X}} \\
 &= \overline{\overline{AB} * \overline{\overline{A}\overline{B}}} && \text{DeMorgan's Law} \\
 &= \overline{(\overline{A} + \overline{B}) * (\overline{\overline{A}} + \overline{\overline{B}})} && \text{DeMorgan's Law} \\
 &= \overline{(\overline{A} + \overline{B}) * (A + B)} && X = \overline{\overline{X}} \\
 &= \overline{\overline{AA} + \overline{BA} + \overline{AB} + \overline{BB}} && \text{Distributive Law} \\
 &= \overline{\overline{BA} + \overline{AB}} && Y + \overline{X}X = Y \\
 &= \overline{A \oplus B} && \text{XOR definition}
 \end{aligned}$$

## 2. Number Systems

(15 pts)

Given the following number in hexadecimal:  $2E$ .

- (a) (5 pts) What is the binary equivalent of this number?

$$0x2E = 101110$$

- (b) (5 pts) What is the decimal equivalent of this number?

*The decimal equivalent of this is:  $32 + 8 + 4 + 2 = 46$*

(separate question) Given the decimal number 178:


- (c) (5 pts) What is the binary equivalent of this number? (show your work)

<b>value</b>	<b>binary</b>	<b><math>i</math></b>	<b><math>2^i</math></b>
<i>178</i>	<i>00000000</i>		
		<i>7</i>	<i>128</i>
<i>50</i>	<i>10000000</i>		
		<i>5</i>	<i>32</i>
<i>18</i>	<i>10100000</i>		
		<i>4</i>	<i>16</i>
<i>2</i>	<i>10110000</i>		
		<i>1</i>	<i>2</i>
<i>0</i>	<i>10110010</i>		

### 3. Sequential Logic

(20 pts)

Given the following circuit:

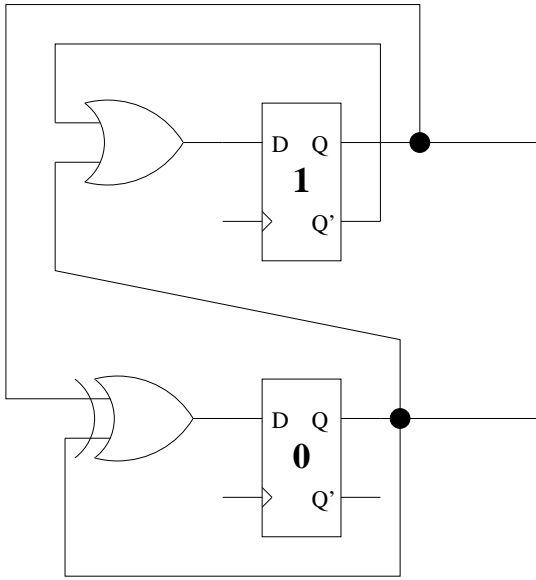

- (a) (5 pts) What are the possible states (list all of them)?


*All combinations of the individual bit values (there are 4 in total):*

00, 01, 10, 11

- (b) (10 pts) Assume an initial state of  $Q_1 = 0$  and  $Q_0 = 1$ . What is the sequence of states over 5 clock cycles?

01, 11, 10, 01, 11, 10

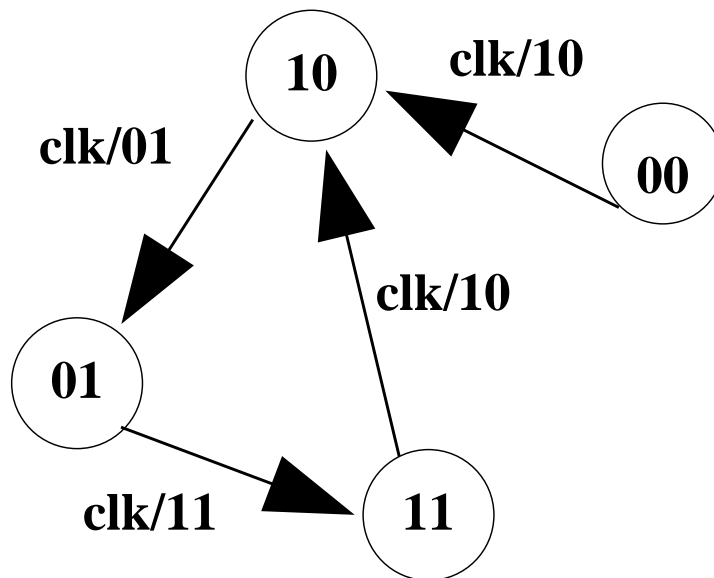(c) (5 pts) Draw the finite state machine representation of this circuit.




*(In this case, I will accept your answer if you did not place the output labels on the transitions).*

4. Memory

(10 pts)

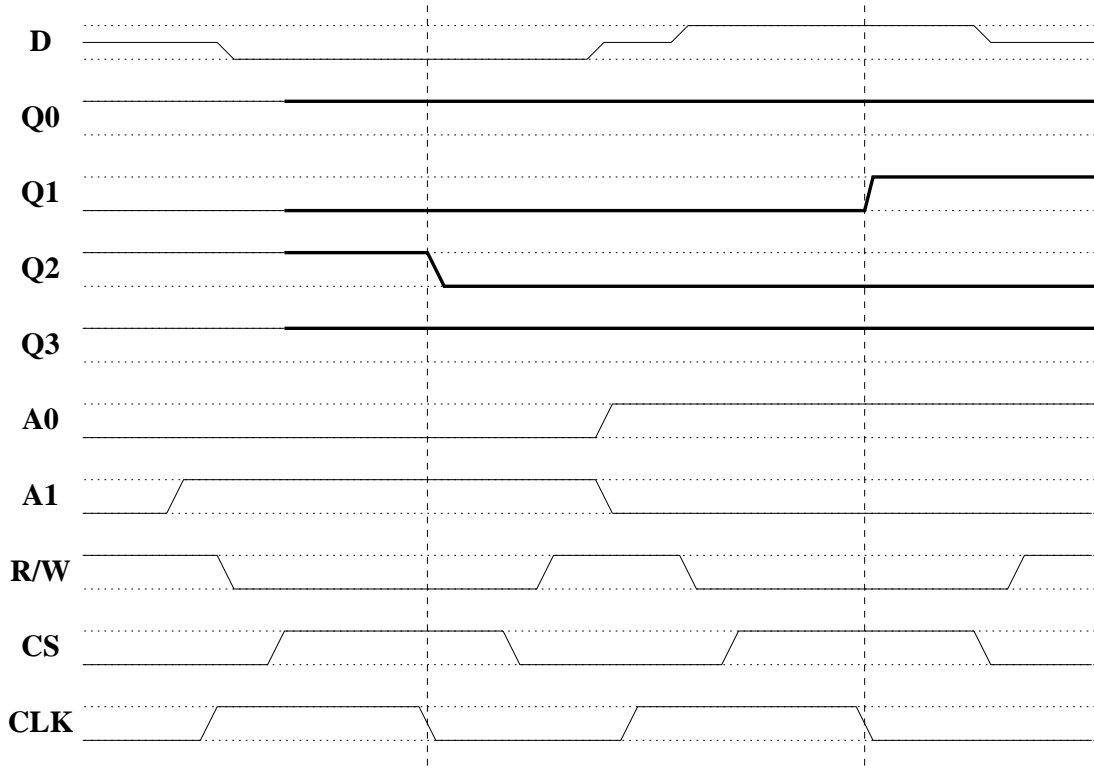(a) (10 pts) For the timing diagram below, fill in the missing traces.



*Both memory operations are write operations (to elements 3 and 0, respectively). Note, however, that the state of Q0 does not change (it was already in a state of "1").*



