

Last Time

- Introduction to embedded systems
 - Properties
 - Examples
- Class structure

Administrivia

Lab hours proposal:

- Monday (Alois): 1-5
- Tuesday (Me): 10:30-3:30
- Wednesday (Alois): 9-1
- Thursday (Me): 12-5

Lab location: EL 124


- If you do not find the lab open, find me in my office (EL 152)

Administrivia

Office hours (until lab opens):

- Andrew Fagg (EL 152):
 - Tuesday: 10:30-11:30
 - Thursday: 1-2
 - Or by appointment
- Alois:
 - Monday: 1-2
 - Wednesday: 9-10
 - Or by appointment

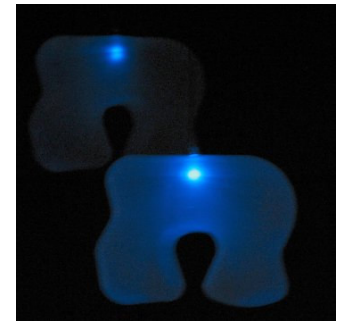“Bion:” An Experiment in Sensor Networks and Art



- Test installation in Stephenson Research and Technology Center (South Campus)
- Best viewing will be Friday

Today: Introduction to Digital Logic

- Binary encoding
- Boolean algebra
- Transistors to logic gates

Encoding Information

In your 'circuits and sensors' class: how did you encode information?

- e.g., the acceleration measured by your accelerometer?
- or the rate of bend of a piezoelectric device?

Encoding Information

Following some form of (implementation dependent) analog conditioning:

- Acceleration (or bend rate) is encoded in the voltage that is output from the circuit
- As acceleration increases, the voltage also increases

Encoding Information

Following some form of (implementation dependent) analog conditioning:

- Acceleration (or bend rate) is encoded in the voltage that is output from the circuit
- As acceleration increases, the voltage also increases
- We say that this is an **analog** or **continuous** encoding of the information

Analog Encoding

What is the problem with analog encoding?

Analog Encoding

What is the problem with analog encoding?

- Small injections of noise – either in the sensor itself or from external sources – will affect this analog signal
- This leads to errors in how we interpret the sensory data

How do we fix this?

Digital Encoding

How do we fix this?

- At any instant, a single signal encodes one of two values:
 - A voltage around 0 (zero) Volts is interpreted as one value
 - A voltage around +5 V is interpreted as another value

Binary Encoding

- Binary digits can have one of two values: 0 or 1
- We call 0V a binary “0” (or FALSE)
- And +5V a binary “1” (or TRUE)

Binary Encoding

- Exactly what these levels are depends on the technology that is used (it is common now to see +1.8V as a binary 1 in low-power processors)
- This encoding is much less sensitive to noise: small changes in voltage do not affect how we interpret the signal

Transistors

What do transistors do for us?

Transistors

What do transistors do for us?


- They act as current amplifiers
- But: we can use them as electronic switches to process digital signals

Transistors to Digital Processing

- Input: 0V $\rightarrow$ Output +5V
- Input: +5V $\rightarrow$ Output 0V
- We call this a “NOT” gate

The NOT Gate

- Logical Symbol:

 

- Algebraic Notation: $B = \overline{A}$


- Truth Table:

A	B
0	1
1	0

A Two-Input Gate


What does this
circuit compute?

- A and B are inputs
- C is the output

 

The “NAND” Gate

- Logical Symbol:

 


- Algebraic Notation: $C = \overline{A * B} = \overline{AB}$

- Truth Table:

A	B		C
0	0		1
0	1		1
1	0		1
1	1		0

The “AND” Gate

- Logical Symbol:

 

- Algebraic Notation: $C = A * B = AB$


- Truth Table:

A	B		C
0	0		0
0	1		0
1	0		0
1	1		1

Yet Another Gate

The “NOR” Gate

- Logical Symbol:

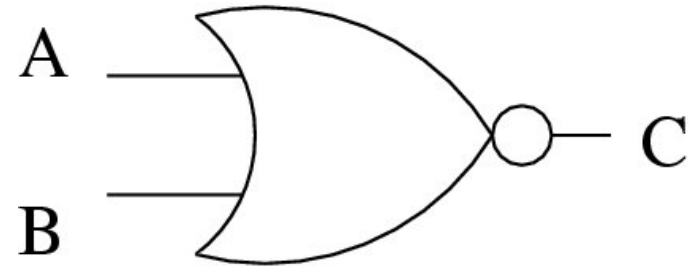


- Algebraic Notation: $C = \overline{A+B}$

- Truth Table:

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

The “OR” Gate

- Logical Symbol:

 



- Algebraic Notation: $C = A+B$

- Truth Table:

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1


N-Input Gates

  Gates can have an arbitrary number of inputs (2,3,4,8,16 are common)



Exclusive OR (“XOR”) Gates

- Logical Symbol:

 


- Algebraic Notation: $C = A \oplus B$

- Truth Table:

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

How would we
implement this
with
AND/OR/NOT
gates?


An XOR Implementation

 


Next Time

- Some notes on Boolean Algebra
- DeMorgan's Laws
- Multiplexers
- Demultiplexers
- Circuit reduction with Karnaugh Maps
- Readings from play-hookey.com (see the schedule)






Bions ...

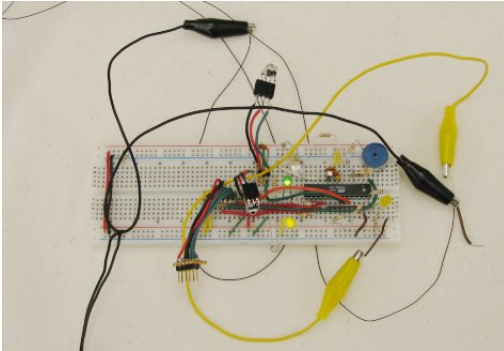

?

 

Bions

  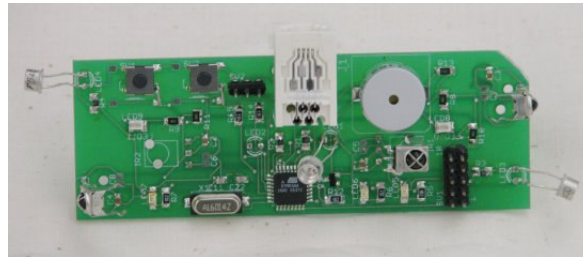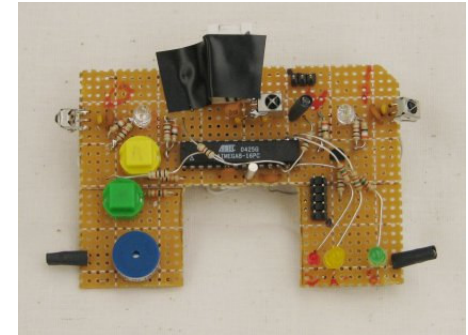 


Andrew H. Fagg: Embedded Real-Time Systems: Digital Logic

Bion Installation



Andrew H. Fagg: Embedded Real-Time Systems: Digital Logic

Bion

 

Andrew H. Fagg: Embedded Real-
Time Systems: Digital Logic

Bion



Andrew H. Fagg: Embedded Real-
Time Systems: Digital Logic

Bion



Andrew H. Fagg: Embedded Real-Time Systems: Digital Logic

Bion



Andrew H. Fagg: Embedded Real-
Time Systems: Digital Logic

Last Time

- Transistors (analog) to logic (digital)
- Basic gates: AND, OR, NOT
- Other gates: XOR, NOR, NAND

These tools form the basis of computation in digital computers

Today

More complicated circuits

Circuit reduction tools:

- Boolean Algebra
- DeMorgan's Laws
- Karnaugh Maps

Administrivia

- Homework 1 goes out tonight; it is due in one week
- A second test email message will go out announcing the homework. If you don't get the message – then we need to fix it ASAP
- General announcements to email list?

An Example

Problem: implement an alarm system

- There are 3 inputs:
 - Door open (“1” represents open)
 - Window open
 - Alarm active (“1” represents active)
- And one output:
 - Siren is on (“1” represents on) when either the door or window are open – but only if the alarm is active

What is the truth table?


Alarm Example: Truth Table

D	W	A		Siren
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		0
1	1	1		1

$$\begin{aligned} &\rightarrow \bar{D} W A \\ &\quad + \\ &\rightarrow D \bar{W} A \\ &\quad + \\ &\rightarrow D W A \end{aligned}$$

Alarm Example: Circuit
 
$$\text{Siren} = \overline{D} W A + D \overline{W} A + D W A$$




Alarm Example: Circuit

Is a simpler circuit possible?

Alarm Example: Truth Table

D	W	A		Siren
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		0
1	1	1		1

Alarm: An Alternative Circuit

 

Boolean Algebra

- There are exactly two numbers in Boolean System: “0” and “1”
- You are already familiar with the “integers”: $\{\dots -2, -1, 0, 1, 2, \dots\}$
– (and Integer Algebra)

Boolean Algebra

- Like the integers, Boolean Algebra has the following operators:

		Integers	Boolean
+		addition	OR
*		product	AND
inverse		negation	NOT

NOT Operator

Definition:

- $\overline{0} = 0' = 1$
- $\overline{1} = 1' = 0$

NOTE: this is identical to our truth table (just a slightly different notation)

Suppose that “X” is a Boolean variable,
then:

- $\overline{\overline{X}} = X'' = X$

OR (+) Operator

Definition:

- $0+0 = 0$
- $0+1 = 1$
- $1+0 = 1$
- $1+1 = 1$

OR (+) Operator

Suppose “X” is a Boolean variable, then:

- $0 + X = X$
- $1 + X = 1$
- $X + X = X$
- $X + X' = 1$

AND (*) Operator

Definition:

- $0 * 0 = 0$
- $0 * 1 = 0$
- $1 * 0 = 0$
- $1 * 1 = 1$

AND (*) Operator

Suppose “X” is a Boolean variable, then:

- $0 * X = 0$
- $1 * X = X$
- $X * X = X$
- $X * X' = 0$

Boolean Algebra Rules: Precedence

The AND operator applies before the OR operator:

$$A * B + C = (A * B) + C$$

$$A + B * C = A + (B * C)$$

Boolean Algebra Rules:

Association Law

If there are several AND operations, it does not matter which order they are applied in:

$$A * B * C = (A * B) * C = A * (B * C)$$

Boolean Algebra Rules: Association Law

Likewise for the OR operator:

$$A + B + C = (A + B) + C = A + (B + C)$$

Boolean Algebra Rules: Distributive Law

AND distributes across OR:

$$A * (B + C) = (A * B) + (A * C)$$

$$A + (B * C) = (A + B) * (A + C)$$

Boolean Algebra Rules:

Commutative Law

Both AND and OR are symmetric operators
(the order of the variables does not
matter):

$$A + B = B + A$$

$$A * B = B * A$$

DeMorgan's Laws

$$(A * B)' = A' + B'$$

How do we convince ourselves that this is true?

Proof by Truth Table

A	B		$(A * B)'$	$A' + B'$
0	0		1	1
0	1		1	1
1	0		1	1
1	1		0	0

NOTE:
change in
the NOT
notation

DeMorgan's Laws (cont)

$$(A + B)' = A' * B'$$

Proof by Truth Table

A	B		$(A + B)'$	$A' * B'$
0	0		1	1
0	1		0	0
1	0		0	0
1	1		0	0

Alarm Example: Truth Table

D	W	A		Siren
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		0
1	1	1		1

→ $D' W A$
+
→ $D W' A$
+
→ $D W A$


Reduction with Algebra

$D' W A + D W' A + D W A$	
$= D' W A + D W' A + D W A + D W A$	$X + X = X$
$= D' W A + D W A + D W' A + D W A$	Commutative Law
$= D' W A + D W A + W' D A + W D A$	“
$= (D' + D) W A + (W' + W) D A$	Assoc + Dist Laws
$= 1 * W A + 1 * D A$	$X + X' = 1$

Reduction with Algebra (cont)

$1 * W A + 1 * D A$	
$= W A + D A$	$X * 1 = X$
$= (W + D) * A$	Distributive Law

We have the same circuit as before!

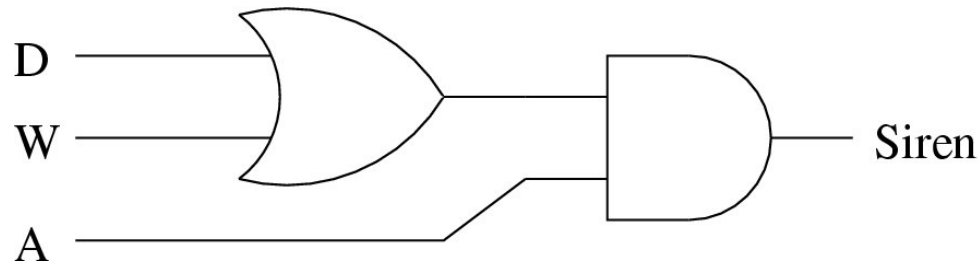

Karnaugh Maps

Geometric technique for reducing circuits

- Step 1: Construct the map
- Step 2: Fill in the output
- Step 3: Identify “clusters” in the map
- Step 4: Read out the terms

Suppose We Have the Following Truth Table:

A	B	C		D
0	0	0		0
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		1

3 Inputs

1 Output


Karnaugh Maps

Step 1: Construct Map

C \ AB	00	01	11	10
0				
1				


Karnaugh Maps

Step 1: Construct Map

 


Karnaugh Maps

Step 1: Construct Map

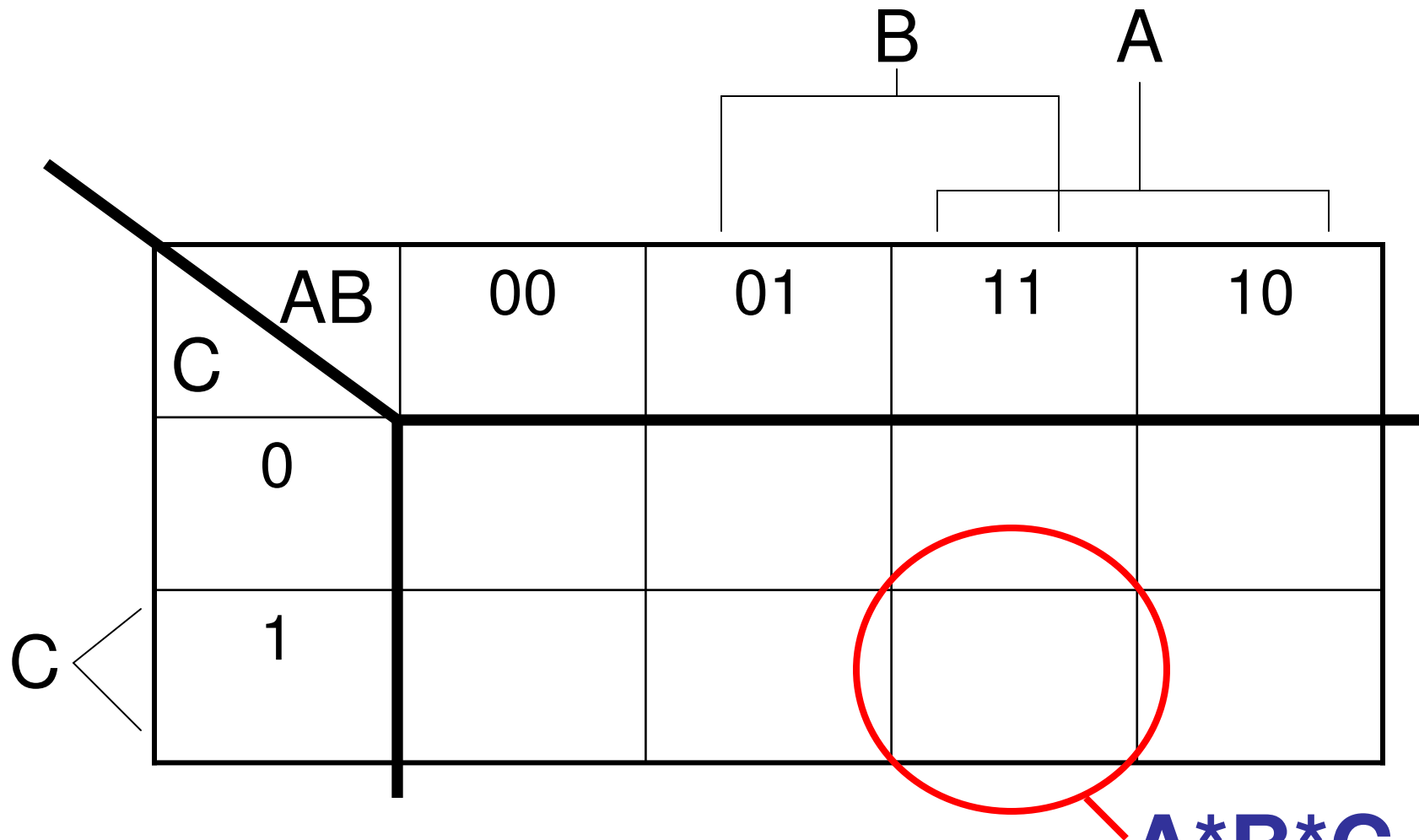

Karnaugh Maps

Step 1: Construct Map

 

Karnaugh Maps

Step 2: Insert Output Values

A	B	C		D
0	0	0		0
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		1

Enter output
values into
map


Karnaugh Maps

Step 2: Insert Output Values

		B		A	
		01		11	
		00		10	
C	AB	00	01	11	10
	0	0	1	1	0
C	1	1	1	1	0


Karnaugh Maps

Step 3: Identify Clusters of 1's

 


Karnaugh Maps

Step 3: Identify Clusters of 1's

 


Karnaugh Maps

Step 3: Identify Clusters of 1's

 

Karnaugh Maps

Step 3: Identify Clusters of 1's

 

Karnaugh Maps


Step 3: Identify Clusters of 1's

Clustering Rules:

- A cluster may not contain a '0'
- All '1's must be covered
- But: it is OK for a '1' to be covered by more than one cluster

Karnaugh Maps

Step 3: Identify Clusters of 1's

 

Karnaugh Maps

Step 4: Read Out the Terms

“OR” the clusters together

Resulting logical rule:

$$B + A'C$$

Next Time

- More on Karnaugh Maps
- Multiplexers
- Demultiplexers

Thinking About Graduate School?

- Research Experiences for Undergraduates: Embedded Machine Learning Systems
 - www-symbiotic.cs.ou.edu/reu
- McNair Scholars Program
 - Supporting underrepresented groups in PhD programs
 - www.ou.edu/special/mcnair
- Computer Science PhD Fellowships
 - fellowships.cs.ou.edu

Administrivia

- Homework 1 is due this coming Tuesday
- My office hours today: 10:15-11:00


The Alarm Example (again)

D	W	A		Siren
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		0
1	1	1		1

→ $D' W A$
+
→ $D W' A$
+
→ $D W A$

Karnaugh Maps

Step 1: Construct Map

 

Karnaugh Maps

Step 2: Insert Output Values


W D

		DW			
		00	01	11	10
A	0	0	0	0	0
	1	0	1	1	1

A

Karnaugh Maps

Step 3: Identify Clusters of 1's

 

Karnaugh Maps

Step 4: Read Out the Terms

Resulting logical rule:

$$WA + DA$$

Karnaugh Maps


Step 4: Read Out the Terms

Resulting logical rule:

$$WA + DA$$

Which can be simplified to:

$$A * (W + D)$$

 

A New K-Map Example


- Four input variables: A, B, C, D
- One output variable: E

Truth Table


A	B	C	D		E
0	0	0	0		0
0	0	0	1		1
0	0	1	0		1
0	0	1	1		1
0	1	0	0		0
0	1	0	1		0
0	1	1	0		1
0	1	1	1		1

A	B	C	D		E
1	0	0	0		0
1	0	0	1		1
1	0	1	0		0
1	0	1	1		1
1	1	0	0		1
1	1	0	1		0
1	1	1	0		0
1	1	1	1		0

Step 1: Construct Map

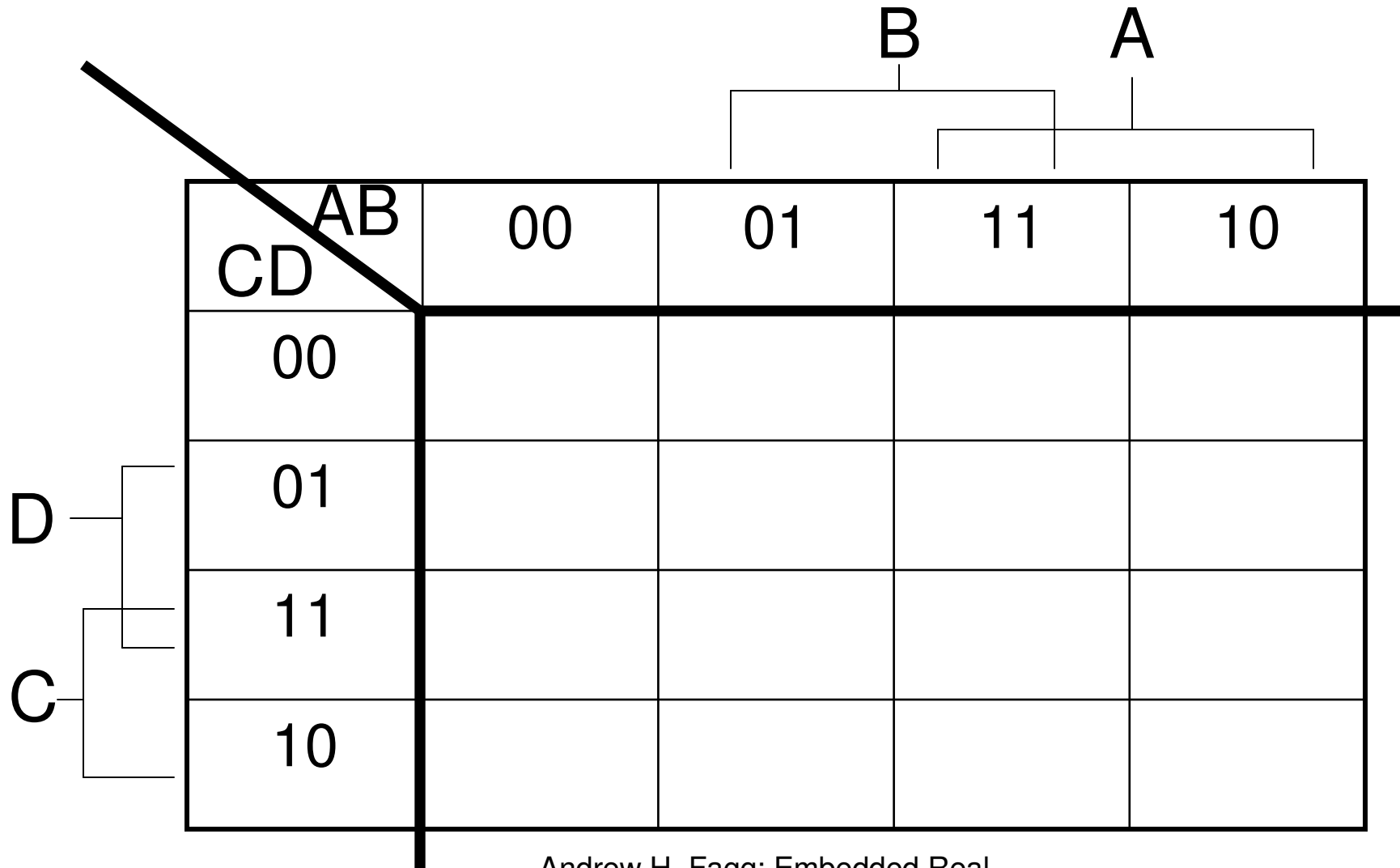


Step 2: Insert Output Values

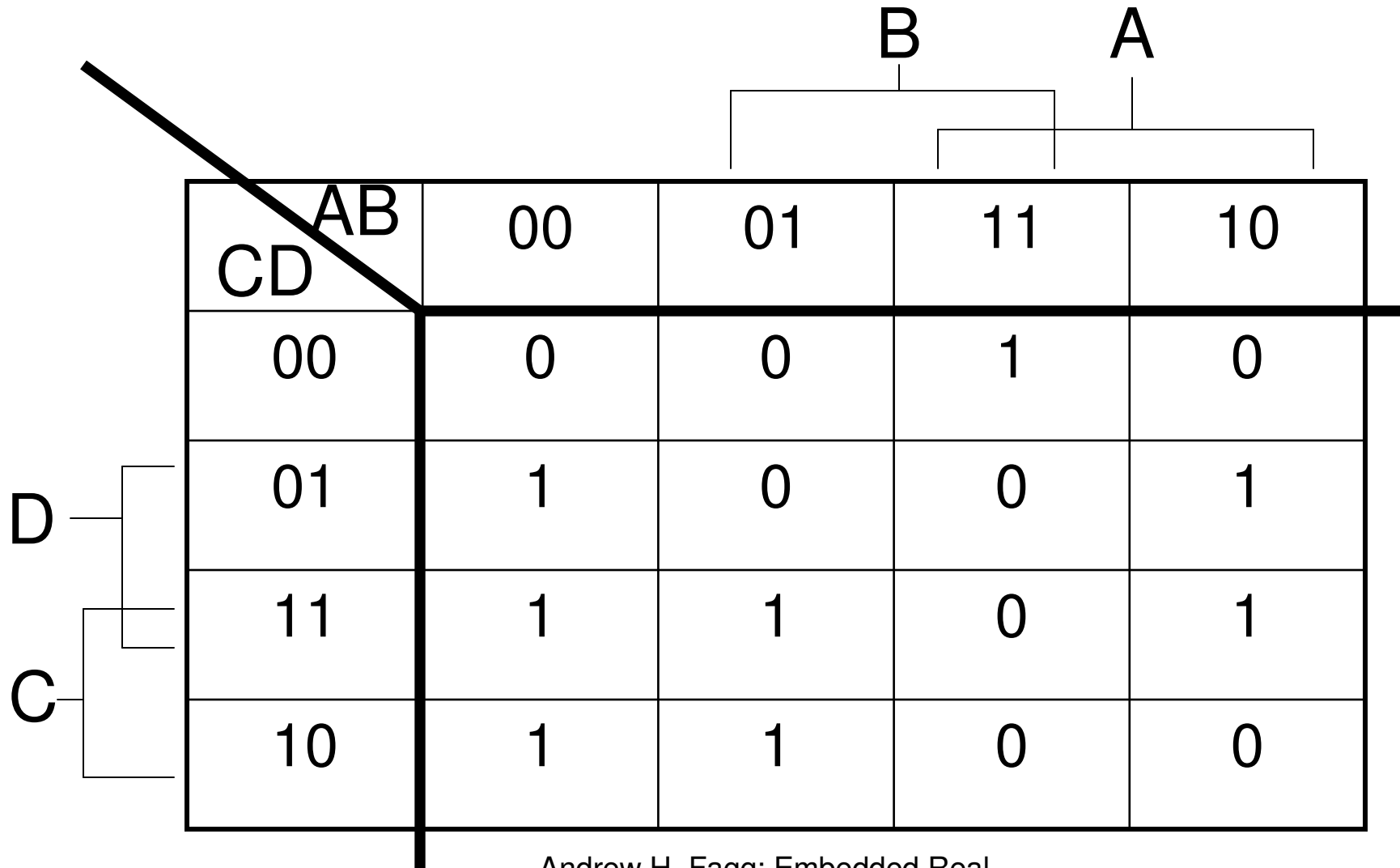


The diagram shows a Karnaugh map for a 4-variable function with variables A, B, C, and D. The map is a 5x5 grid. The top row is labeled with 'AB' and its values '00', '01', '11', '10'. The left column is labeled with 'CD' and its values '00', '01', '11', '10'. A diagonal line is drawn from the top-left corner to the middle of the first row. Above the map, 'B' is labeled with a bracket over the '01' and '11' columns, and 'A' is labeled with a bracket over the '11' and '10' columns. To the left of the map, 'D' is labeled with a bracket over the '01' and '11' rows, and 'C' is labeled with a bracket over the '11' and '10' rows. The output values are inserted into the cells of the 4x4 grid.

AB	00	01	11	10
CD	0	0	1	0
01	1	0	0	1
11	1	1	0	1
10	1	1	0	0


Step 3: Identify Clusters

 


Step 3: Identify Clusters

 

Step 3: Identify Clusters

 

Step 3: Identify Clusters

 


Step 4: Read Out the Terms

$$C A' + B' D + A B D' C'$$

What does the circuit look like?

Resulting Circuit

$$C A' + B' D + A B D' C'$$

 

“Don’t Care” Cases


- For some functions that we will implement, some of the input cases will never occur
- How does this affect our Karnaugh Map?

Modified Truth Table

A	B	C	D		E
0	0	0	0		0
0	0	0	1		1
0	0	1	0		1
0	0	1	1		1
0	1	0	0		0
0	1	0	1		0
0	1	1	0		1
0	1	1	1		1

A	B	C	D		E
1	0	0	0		0
1	0	0	1		1
1	0	1	0		X
1	0	1	1		1
1	1	0	0		1
1	1	0	1		X
1	1	1	0		0
1	1	1	1		0


Step 2: Insert Output Values

 


The diagram shows a Karnaugh map for a 4-variable function with variables A, B, C, and D. The map is a 5x5 grid. The top row is labeled with 'AB' and its values '00', '01', '11', '10'. The left column is labeled with 'CD' and its values '00', '01', '11', '10'. A diagonal line is drawn from the top-left corner to the middle of the grid. Above the grid, 'B' is labeled with a bracket over the '01' and '11' columns, and 'A' is labeled with a bracket over the '11' and '10' columns. To the left of the grid, 'D' is labeled with a bracket over the '01' and '11' rows, and 'C' is labeled with a bracket over the '11' and '10' rows. The output values are: 0 for (00,00), (01,00), (11,00), (00,01), (01,01), (11,01), (00,11), (01,11), (11,11), (00,10), (01,10), (11,10), and 1 for (10,00), (10,01), (10,11), (10,10). Two cells contain a green 'X': (11,01) and (10,10).

AB \ CD	00	01	11	10
00	0	0	1	0
01	1	0	X	1
11	1	1	0	1
10	1	1	0	X

Step 3: Identify Clusters

 

Step 3: Identify Clusters

 

Step 4: Read Out the Terms

$$C A' + B' D + A B C'$$

The resulting circuit is simpler (but just a little in this case)

Multiple Output Variables

Suppose we have a function with multiple output variables?

- How do we handle this with Karnaugh Maps?

Multiple Output Variables

How do we handle this with Karnaugh Maps?

- We produce one Karnaugh Map for each output variable
- But: in the final implementation, some sub-circuits may be shared


Karnaugh Maps: Final Notes

- Always use clusters that are as large as possible
- Possible to extend technique to 5 and 6 inputs (and more), but it starts to get hairy
 - Tend to make use of circuit design “assistants”

Multiplexer

A multiplexer is a device that selects between two input lines

 - A & B are the inputs
- S is the selection signal (also an input)
- C is a copy of A if $S=0$
- C is a copy of B if $S=1$




Multiplexer Truth Table

What would the
Karnaugh map look
like?


S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Multiplexer K-Map

 

Multiplexer Implementation


$$C = S'A + SB$$

 

N-Input Multiplexer

Suppose we want to select from between N different inputs.

 - This requires more than one select line. How many?




N-Input Multiplexer


How many select lines?

- $M = \log_2 N$
or
- $N = 2^M$

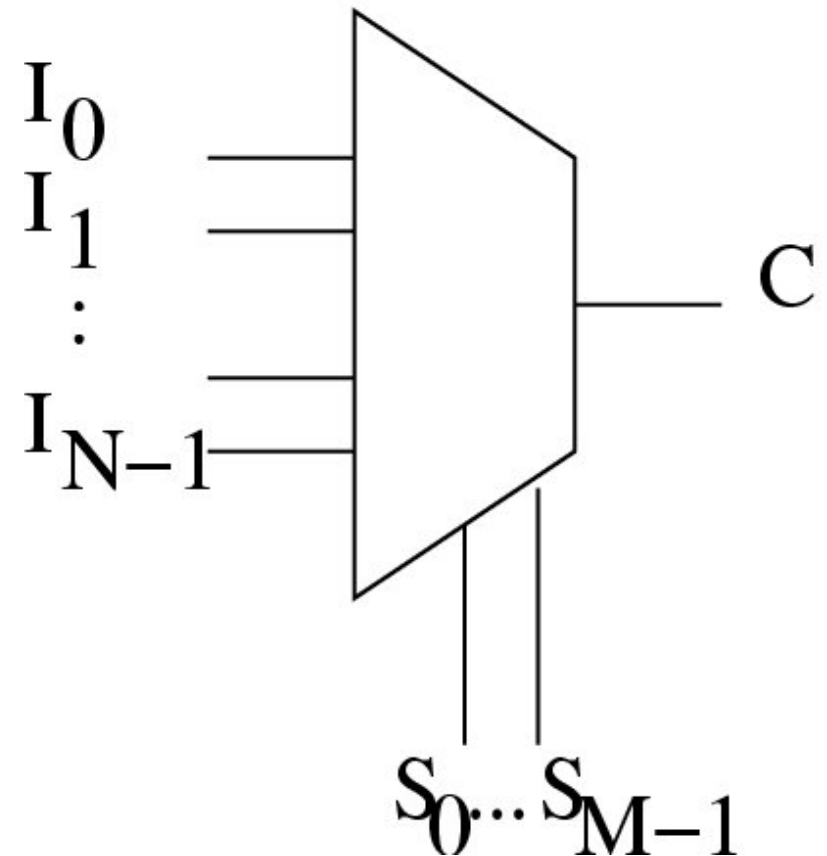What would the $N=8$
implementation look
like?



8-Input Multiplexer Implementation
 
$$C = I_0 S'_2 S'_1 S'_0 + I_1 S'_2 S'_1 S_0 + I_2 S'_2 S_1 S'_0 + \\ I_3 S'_2 S_1 S_0 + I_4 S_2 S'_1 S'_0 + I_5 S_2 S'_1 S_0 + \\ I_6 S_2 S_1 S'_0 + I_7 S_2 S_1 S_0$$


Note that we have one of each possible select line combination (or addressing terms)

Next Time

- Digital logic in practice
- Reading (listed on the schedule):
 - ESA 3.3, 3.5.1, 3.5.2, 3.6.1, 3.7, Appendix B

Bion Installation at Long Island University



Andrew H. Fagg: Embedded Real-
Time Systems: Digital Logic

Bion



Andrew H. Fagg: Embedded Real-Time Systems: Digital Logic



Andrew H. Fagg: Embedded Real-Time Systems: Digital Logic

Bion



Andrew H. Fagg: Embedded Real-
Time Systems: Digital Logic

Bion



Andrew H. Fagg: Embedded Real-
Time Systems: Digital Logic

Last Time

- Karnaugh Maps and Circuit Reduction
- Multiplexers

Today

- Demultiplexers
- Tristate buffers
- Practical issues in digital logic implementation

Administrivia

- Homework 1 is due today at 5:00
- Homework 2 available later today (and is due in 1 week)

Administrivia II


Make sure you fill out and hand-in group placement forms today

“Experimental Group:”

- First 2 labs would be with the mobile robots; last 2 would be with a custom robot
- Between now and the 3rd lab: we would be responsible for designing and constructing the robot

Demultiplexer

 - The multiplexer reduces N signals down to 1 (with M select lines)
- A demultiplexer routes a data input (D) to one of N output lines (As)
 - Which A depends on the select lines



2-Input Demultiplexer

Inputs

Truth Table


Outputs

S_1	S_0	D		A_3	A_2	A_1	A_0
0	0	0		0	0	0	0
0	0	1		0	0	0	1
0	1	0		0	0	0	0
0	1	1		0	0	1	0
1	0	0		0	0	0	0
1	0	1		0	1	0	0
1	1	0		0	0	0	0
1	1	1		1	0	0	0

Demultiplexer Implementation

- What does it look like?

Demultiplexer Implementation

 

M-Input (Select) Demultiplexer


- Will have 2^M output lines
- Useful for converting a binary address into select lines for devices and memory elements
 - (more on binary soon)

Tristate Buffers

- Until now: the output line(s) of each device are driven either high or low
 - So the line is either a source or a sink of current
- Tristate buffers can do this or leave the line floating (as if it were not connected to anything)

Tristate Buffers


S	A	B
0	0	floating
0	1	floating
1	0	0
1	1	1

 

How are tristate buffers useful?

Tristate Buffers

 
We can wire the outputs of multiple tristate buffers together without any other logic



Tristate Buffers

- We must guarantee that only one select line is active at any one time
- Tristate buffers will turn out to be useful when we start building data and address buses

Another Tristate Buffer

 

What does the truth table look like?

Another Tristate Buffer

S	A		B
0	0		0
0	1		1
1	0		floating
1	1		floating

