

# Time

Until now: we have essentially ignored the issue of time


- We have assumed that our digital logic circuits perform their computations instantaneously
- Our digital logic circuits have been “stateless”
  - Once you present a new input, they forget everything about previous inputs

# Time


In reality, time is an important issue:

- Even our logic gates induce a small amount of delay (on the order of a few nanoseconds)
- For much of what we do – we actually want our circuits to have some form of memory

# Timing Notation

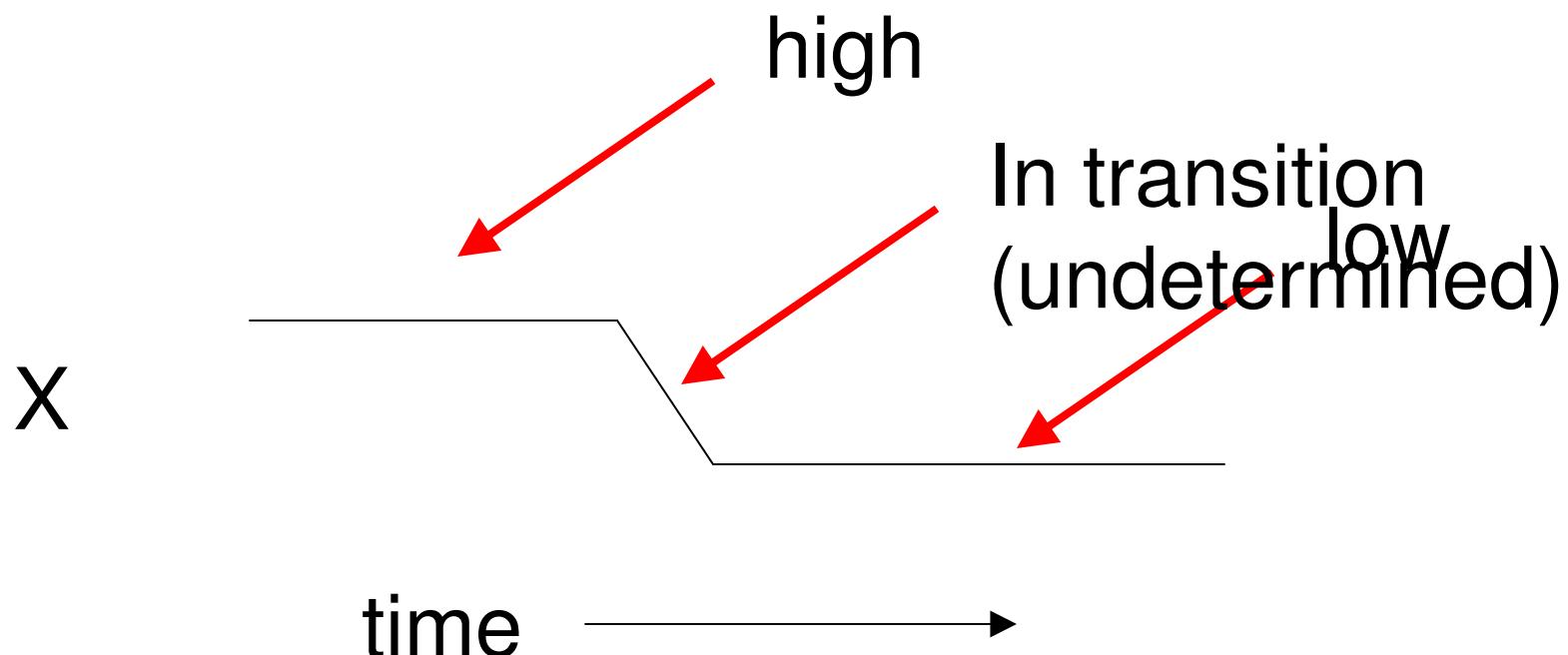

# Timing Notation

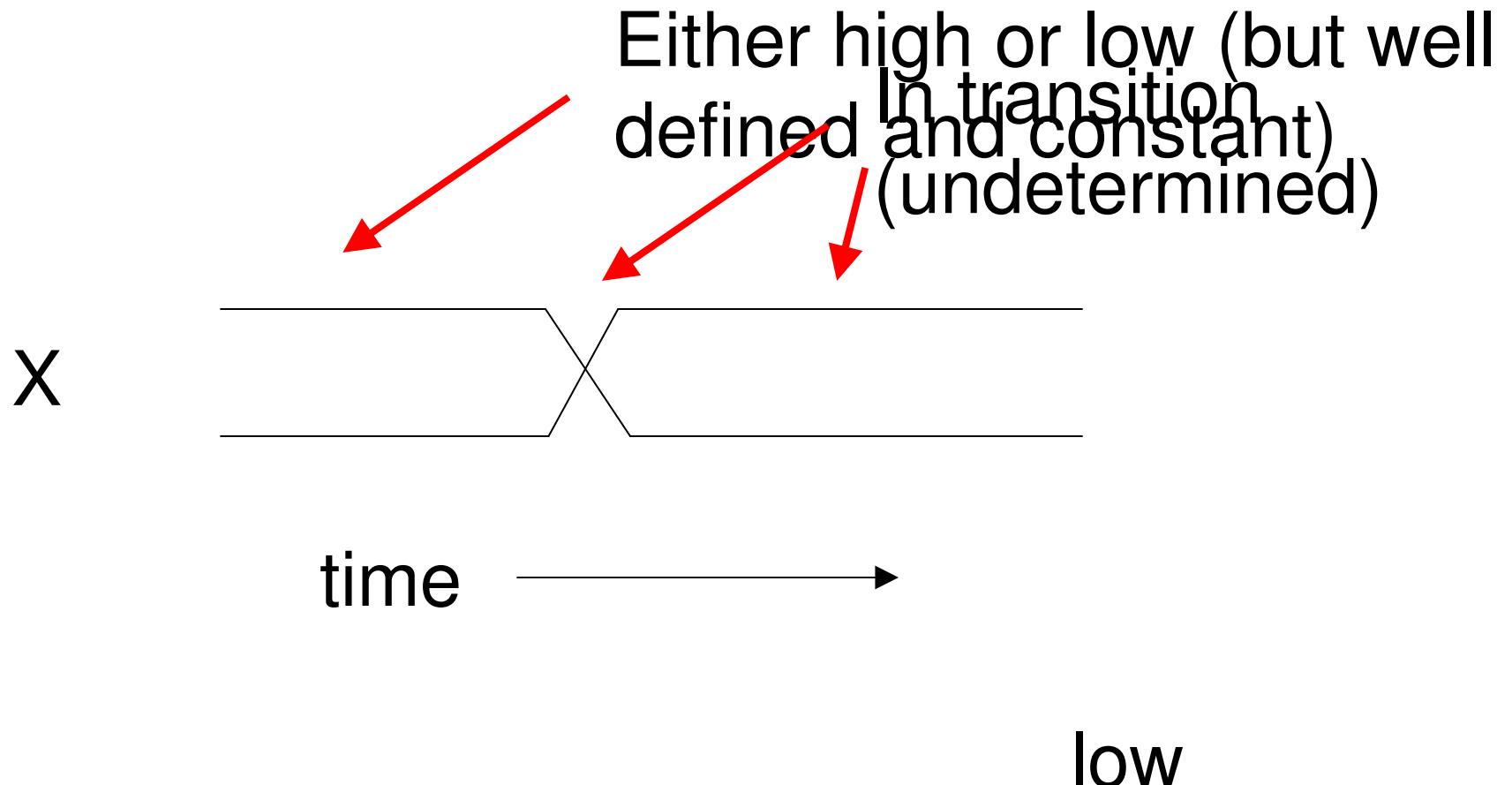

# Today

- Project 1 continued
- Sequential logic

- Homework 3 will be out next Tuesday

# Beacon Receiver

The preprocessor translates the IR sensor signal into a 2-bit number

The state of each IR sensor is encoded with its own pair of bits

<b>B1</b>	<b>B0</b>		<b>Semantics</b>
0	0		No signal
0	1		Low signal
1	0		Medium signal
1	1		Strong signal

# Robot Control Interface

3 output lines  
will  
determine  
the motion  
of the robot

<b>C2</b>	<b>C1</b>	<b>C0</b>	<b>Semantics</b>
0	0	0	Stop
0	0	1	Forward
0	1	0	Backward
0	1	1	Left
1	0	0	Right
1	0	1	Forward-Right
1	1	0	Forward-Left
1	1	1	X

# Robot Control Interface

2 output  
lines will  
determine  
the turret  
position

<b>T1</b>	<b>T0</b>		<b>Semantics</b>
0	0		Forward
0	1		Left
1	0		Right
1	1		x

# Your Job

Design and build a controller from basic logic gates


- Design the function: given each possible input from the sensors, what should the robot do?
- For each of these cases what command must you generate ( $C_2$ ,  $C_1$ ,  $C_0$ ,  $T_1$ ,  $T_0$ )?
- What circuit will generate this command?
- Build the circuit

# Group Design (Now)


- What are the different possible sensor states?
- Can you simplify this set of states?
- A: For each state, what should the robot do?
- B: What is the truth table?
- C: Generate the K-maps

By end of class: hand in A, B & C


# D Flip Flops

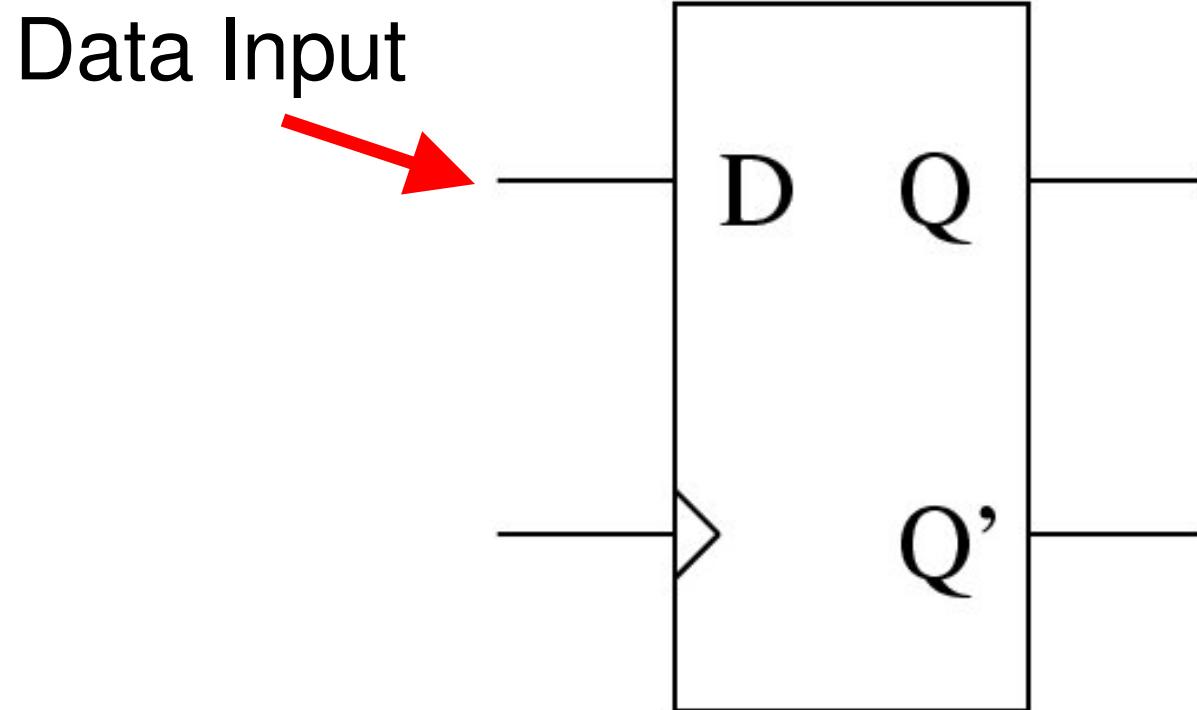


# D Flip Flops

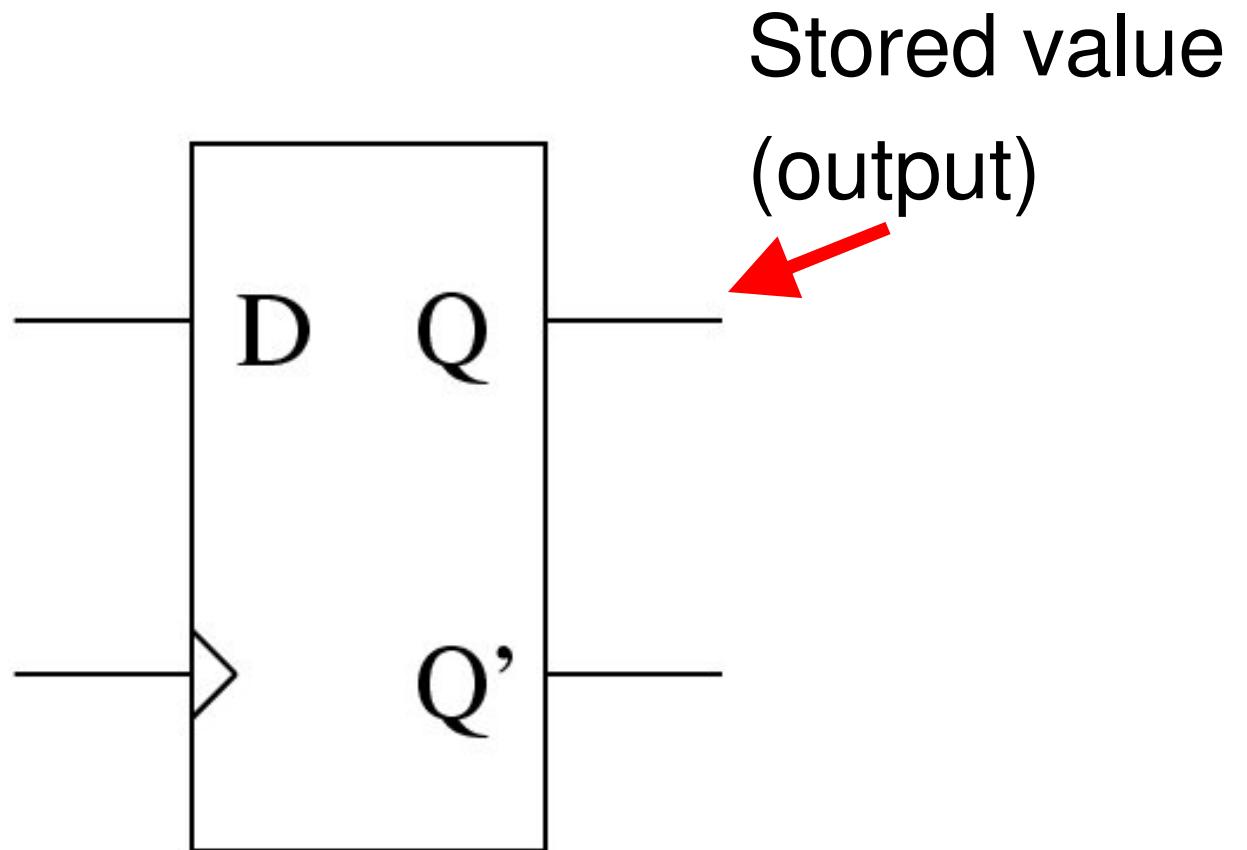


# D Flip Flops

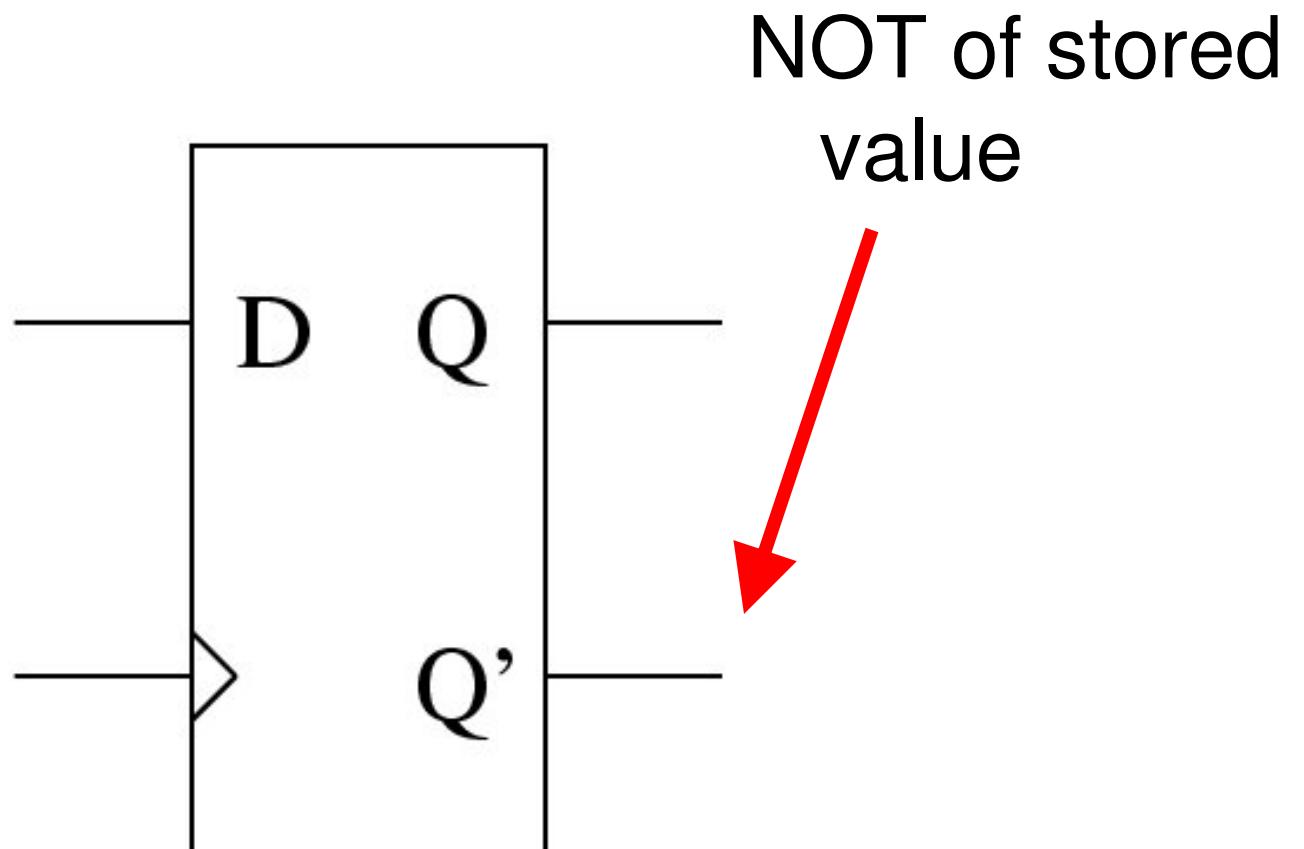

# D Flip Flops


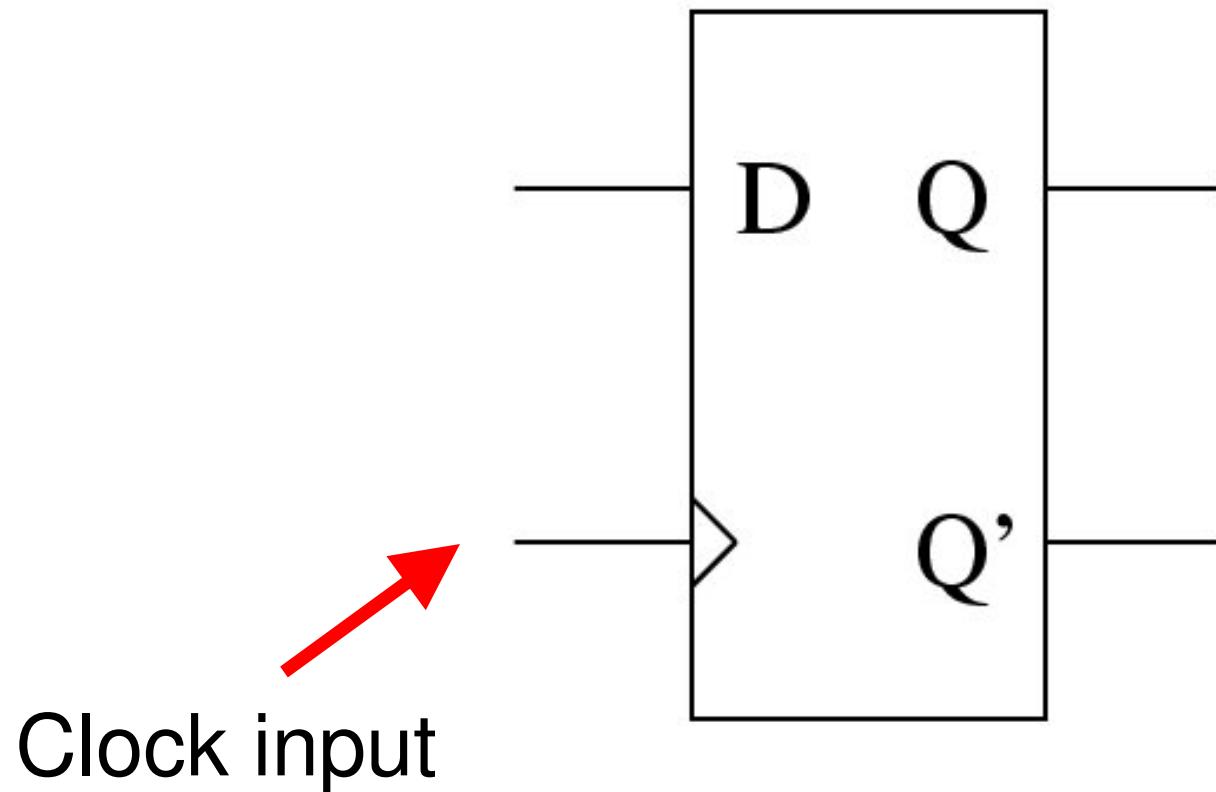


# D Flip Flops

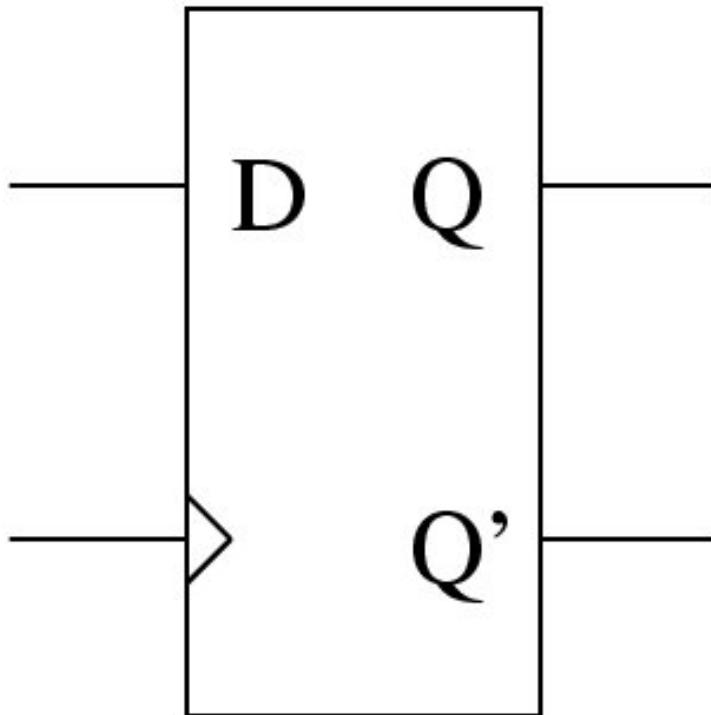

When the clock transitions from high to low:  
the value of D is stored

# D Flip Flop

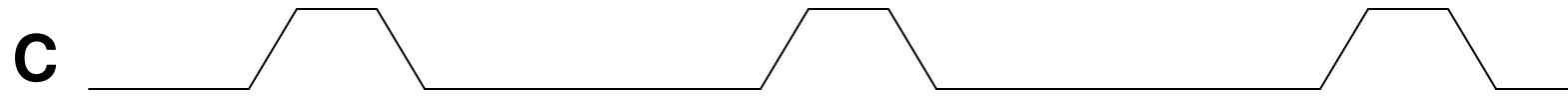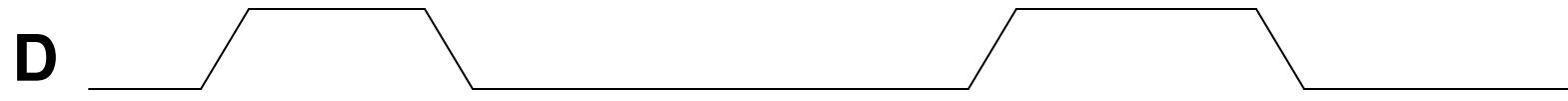


**Q** —


**Q'** —

What happens to  
Q and Q'?

# D Flip Flop

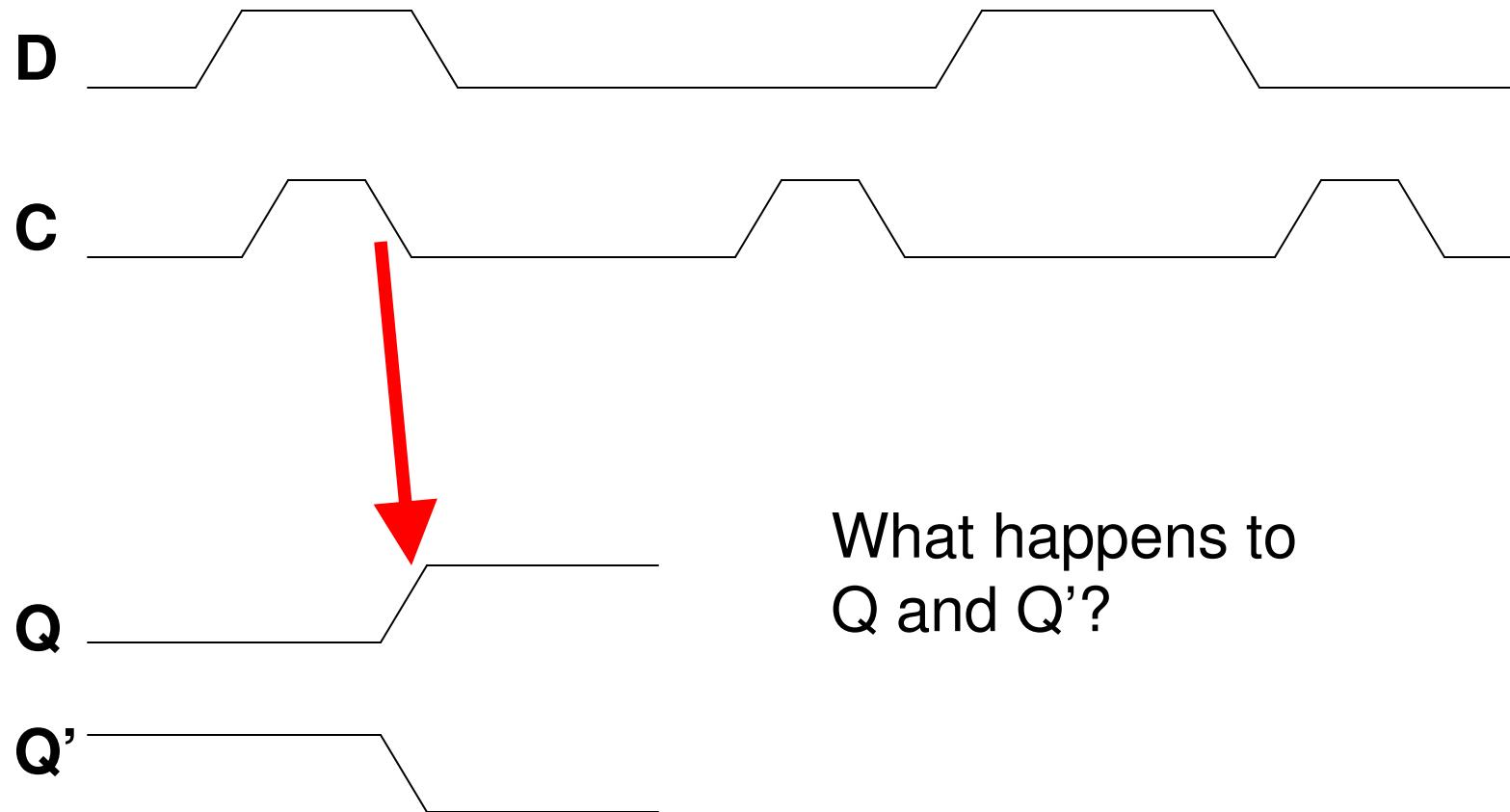


# D Flip Flop

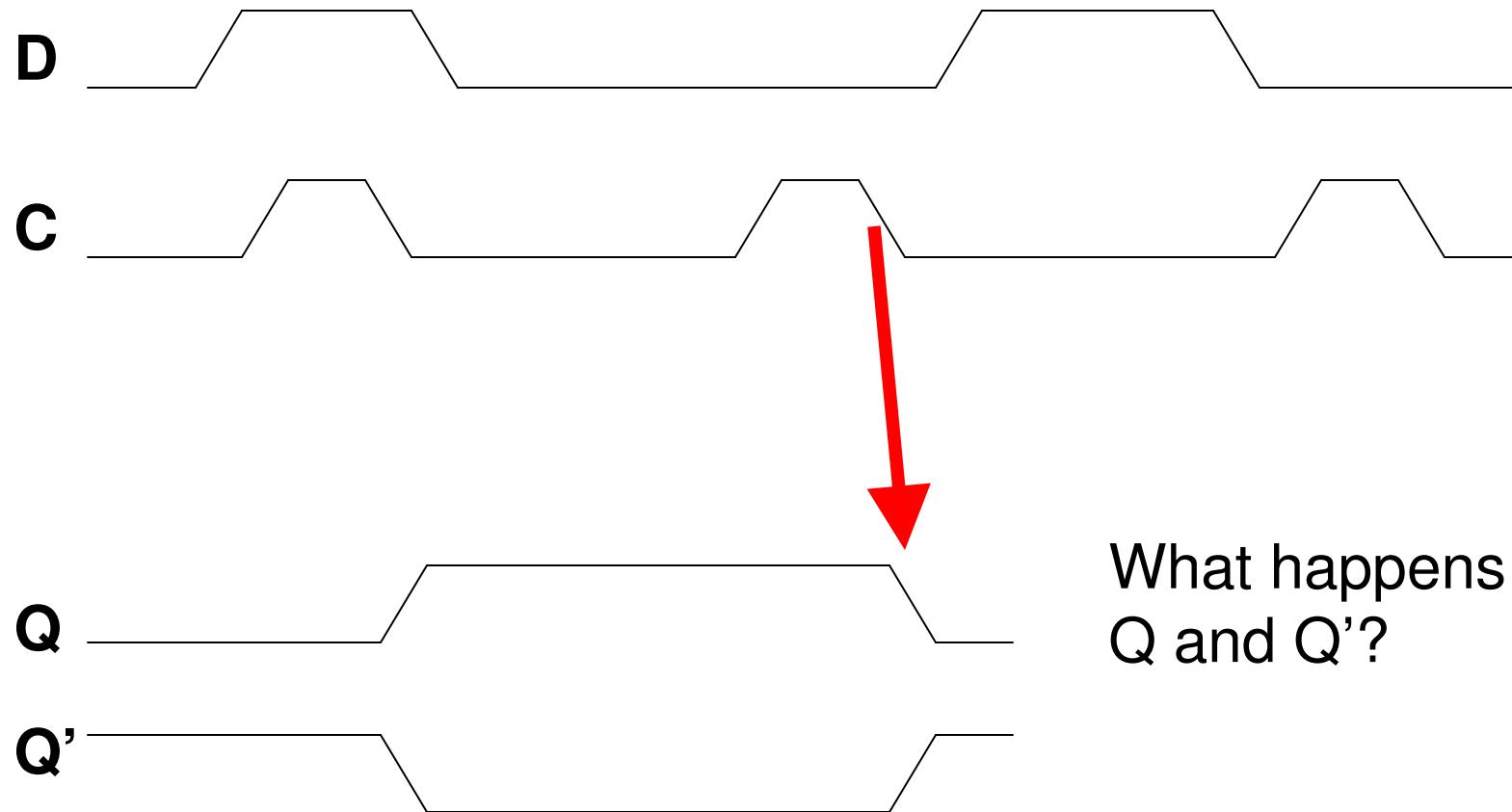


What happens to  
Q and Q'?

# D Flip Flop

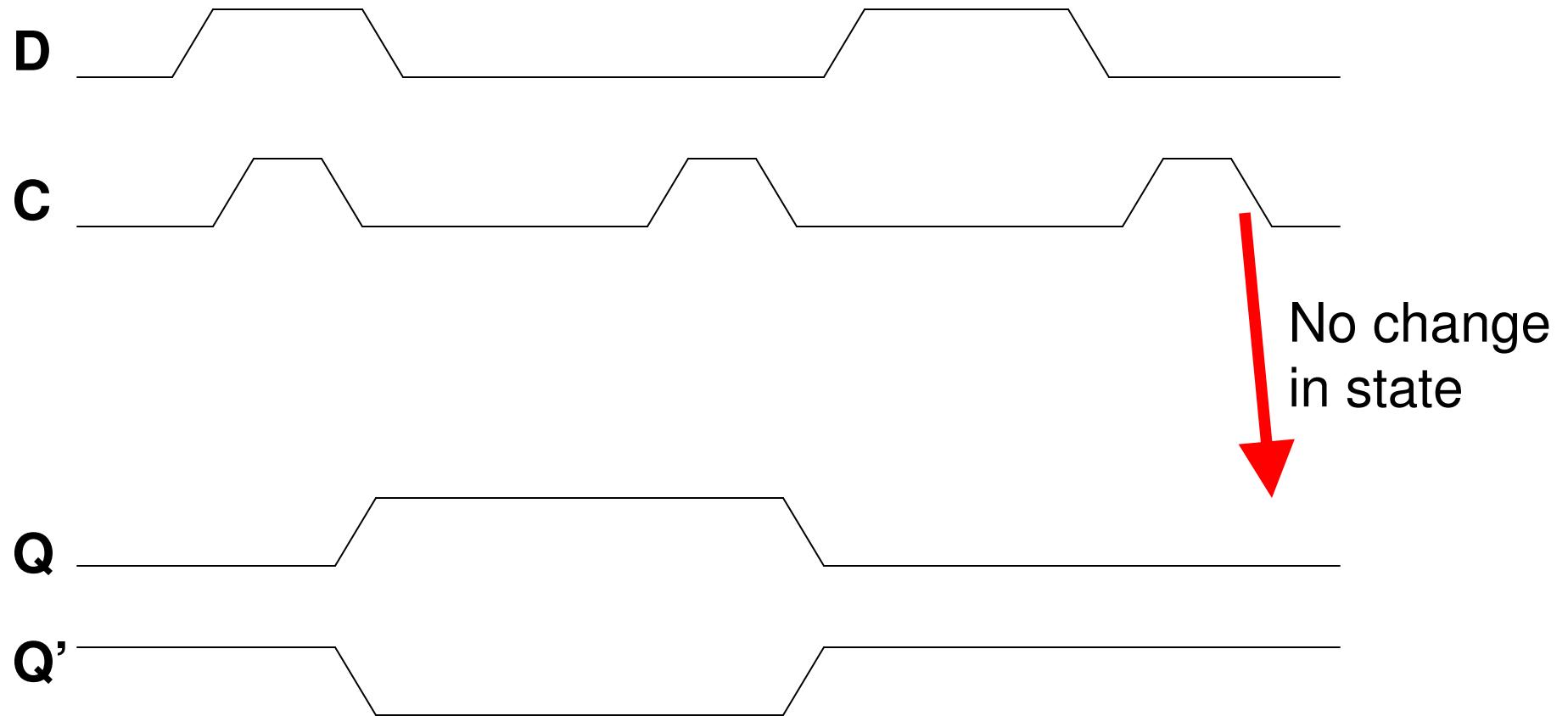

# An Application of D Flip Flops


What does this circuit do?

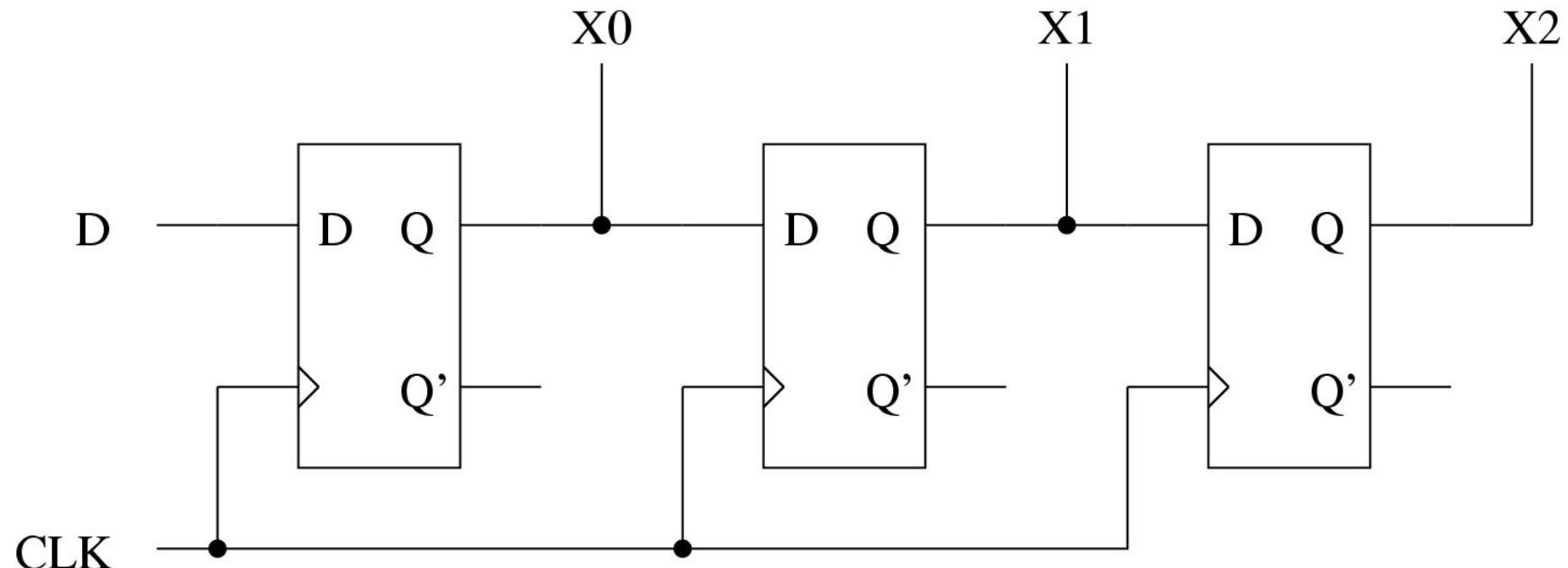
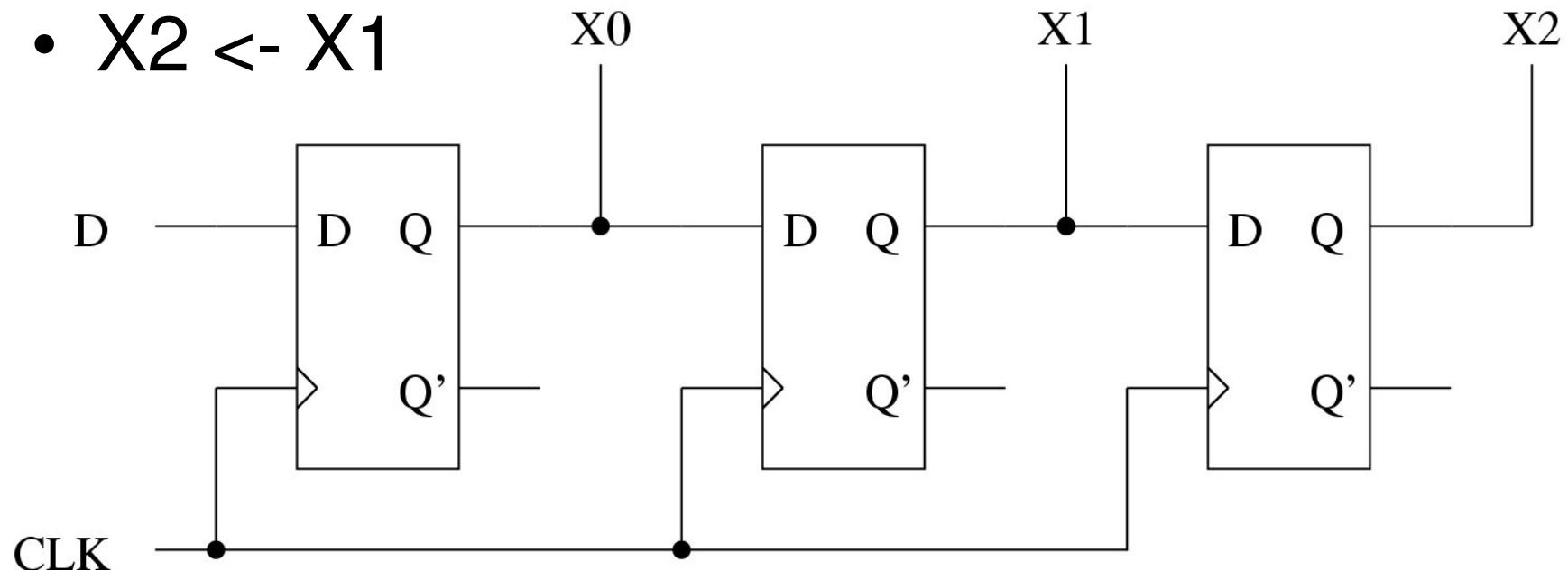
# Shift Register


On each clock transition from high to low:

- $X_0$  takes on the current value of  $D$
- $X_1 \leftarrow X_0$
- $X_2 \leftarrow X_1$




# Another D Flip Flop Circuit

How does this circuit behave?

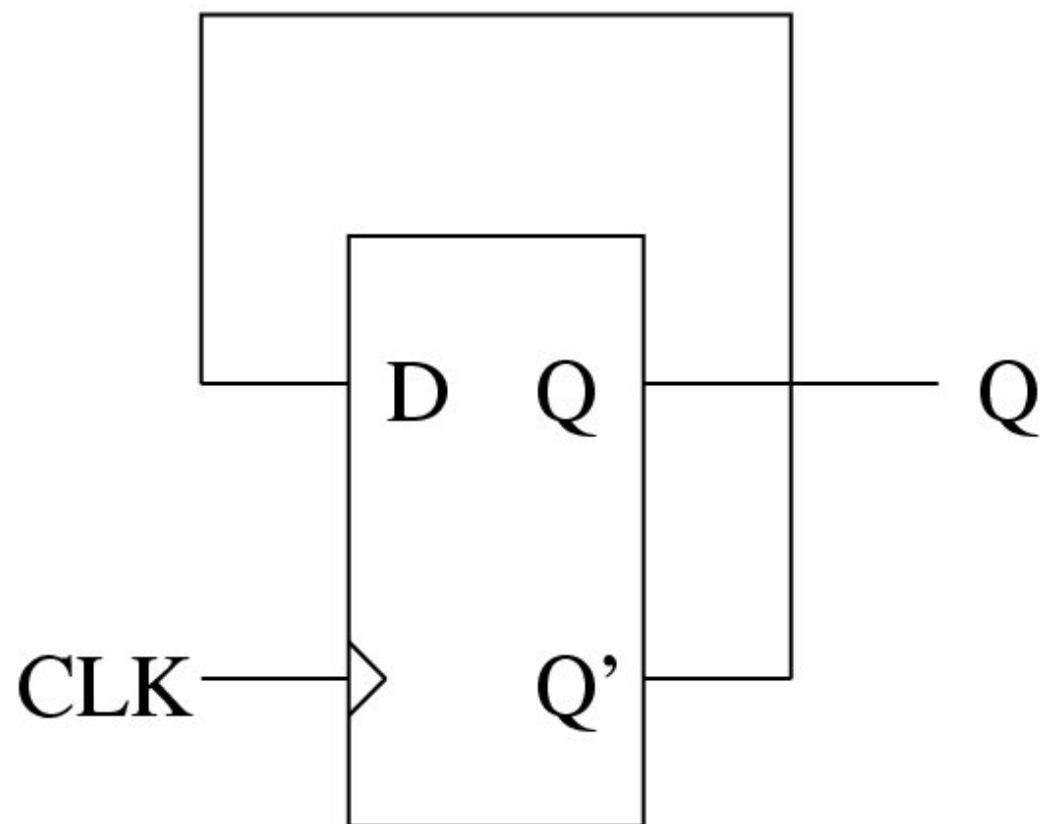


# Frequency Divider

How does this circuit behave?

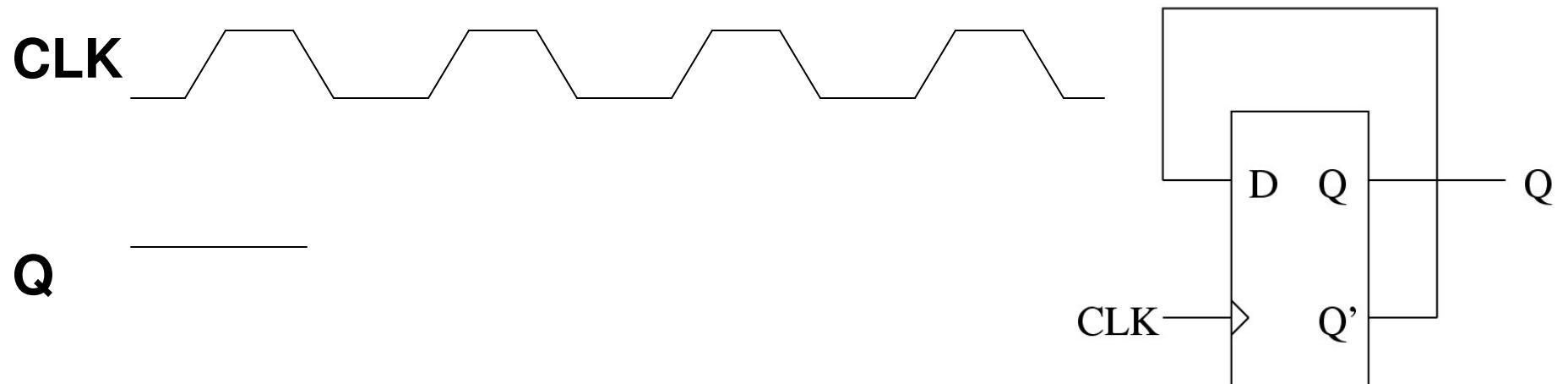


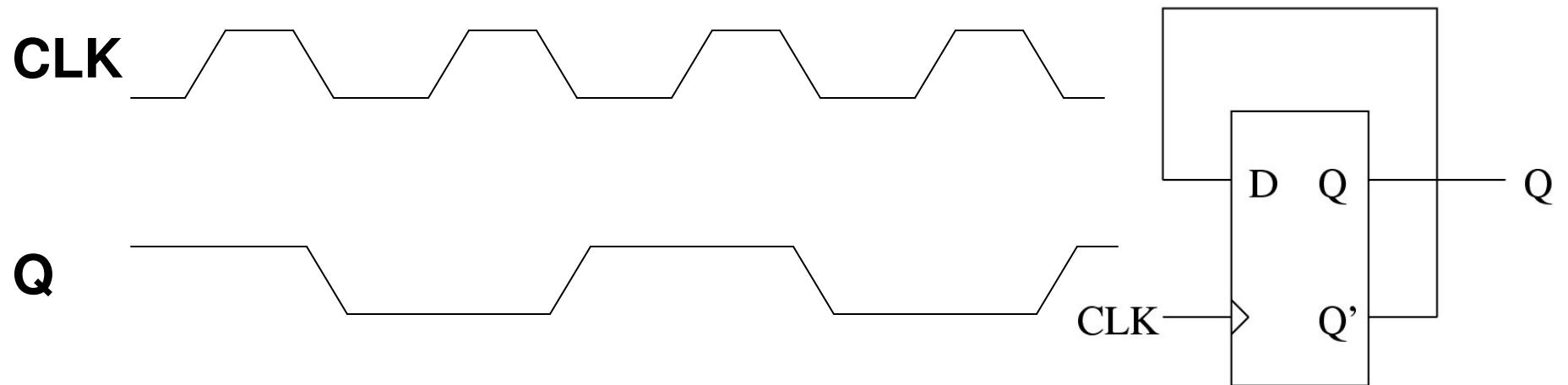
# Frequency Divider

Q flips state on every downward edge of the clock


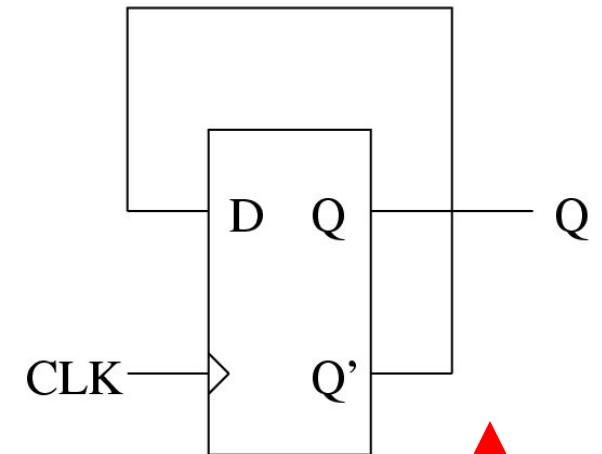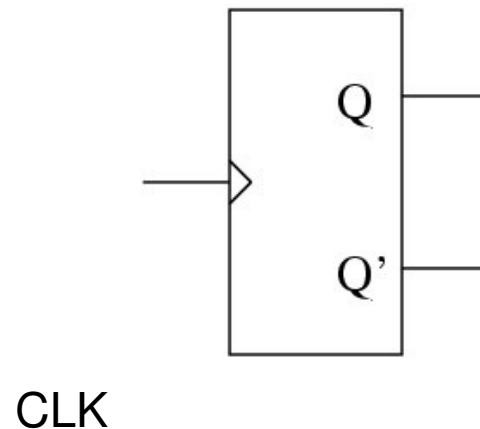
# T Flip-Flops

T flip-flops change state every time the clock transitions from high to low




This is the same behavior as our D flip-flop circuit
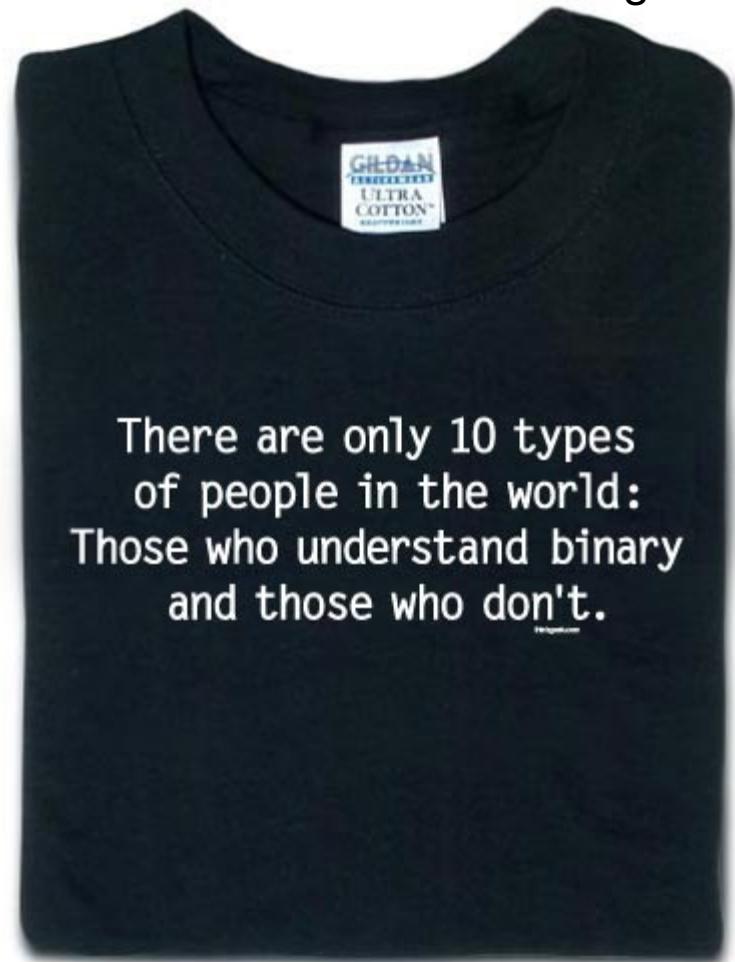
# A Bit About Binary Encoding

[www.thinkgeek.com](http://www.thinkgeek.com)

If a boolean variable can only encode two different values, how do we represent a larger number of values?



# Binary Encoding

How do we represent a larger number of values?

- As with our decimal number system: we concatenate binary digits (or “bits”) into strings

# Binary Encoding

- The first (rightmost) bit is the 1's digit
- The second bit is the 2's digit
- The  $i$ th bit is the  $2^{i-1}$  's digit

# Binary Encoding

How do we convert from binary to decimal in general?

B2	B1	B0		decimal
0	0	0		0
0	0	1		1
0	1	0		2
0	1	1		3
1	0	0		4
1	0	1		5
1	1	0		6
1	1	1		7

# Last Time

## Sequential Logic

- D Flip Flops
- Shift registers
- Binary number system

# Today

- A little more on number systems
- Use of flip-flops
- Homework 2
- NAND latches

# Administrivia

- Homework 3 available tonight
- Project 1:
  - Four robots are now up and stable
  - Due in 9 days

# Binary to Decimal Conversion

$$value = B_0 + B_1 * 2^1 + B_2 * 2^2 + B_3 * 2^3 + \dots$$

$$value = \sum_{i=0}^{N-1} B_i * 2^i$$

How do we convert from decimal  
to binary?

# Decimal to Binary Conversion

$\forall i : B_i \leftarrow 0$

*while*( $value \neq 0$ )

{

*Find i such that*  $2^{i+1} > value \geq 2^i$

$B_i \leftarrow 1$

$value \leftarrow value - 2^i$

}

# Binary Counter

How would we build a circuit that counts the number of clock ticks that have gone by?

B2	B1	B0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

# Binary Counter

How would we build a circuit that counts the number of clock ticks that have gone by?


Insight:

- B1 changes state at half the frequency that B0 does
- B2 changes state at half the frequency of B1

B2	B1	B0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

# Ripple Counter

The carry “ripples” down the chain ...

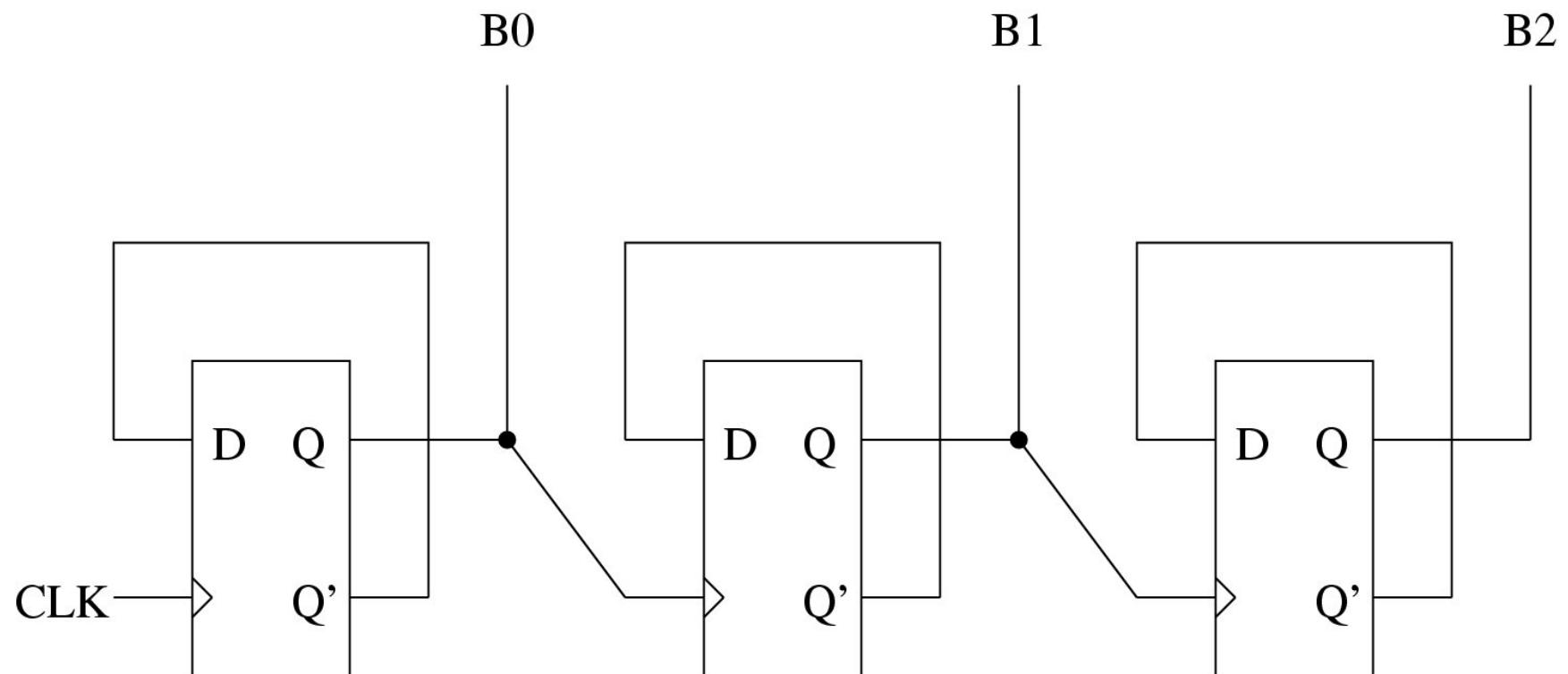


# Ripple Counter

- Problem: the bits do not change state at the same time
- How would we go about designing a circuit to fix this?

# Sequential Counter


# NAND Latch

What does this circuit do?

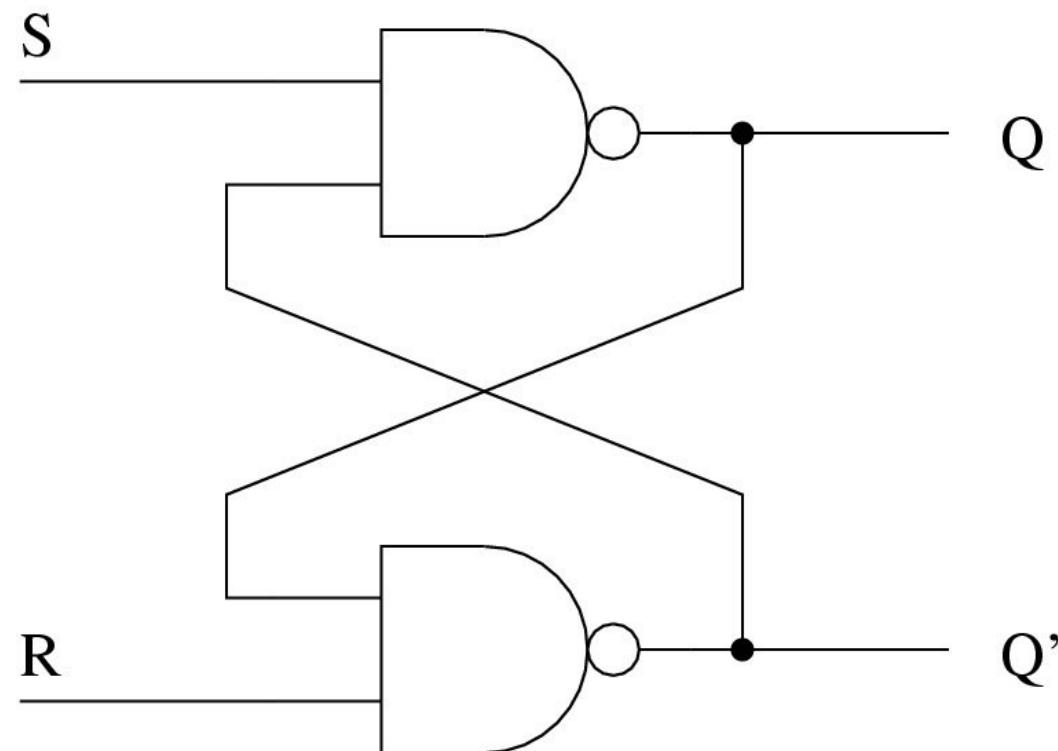

# NAND Latch

Consider this initial state

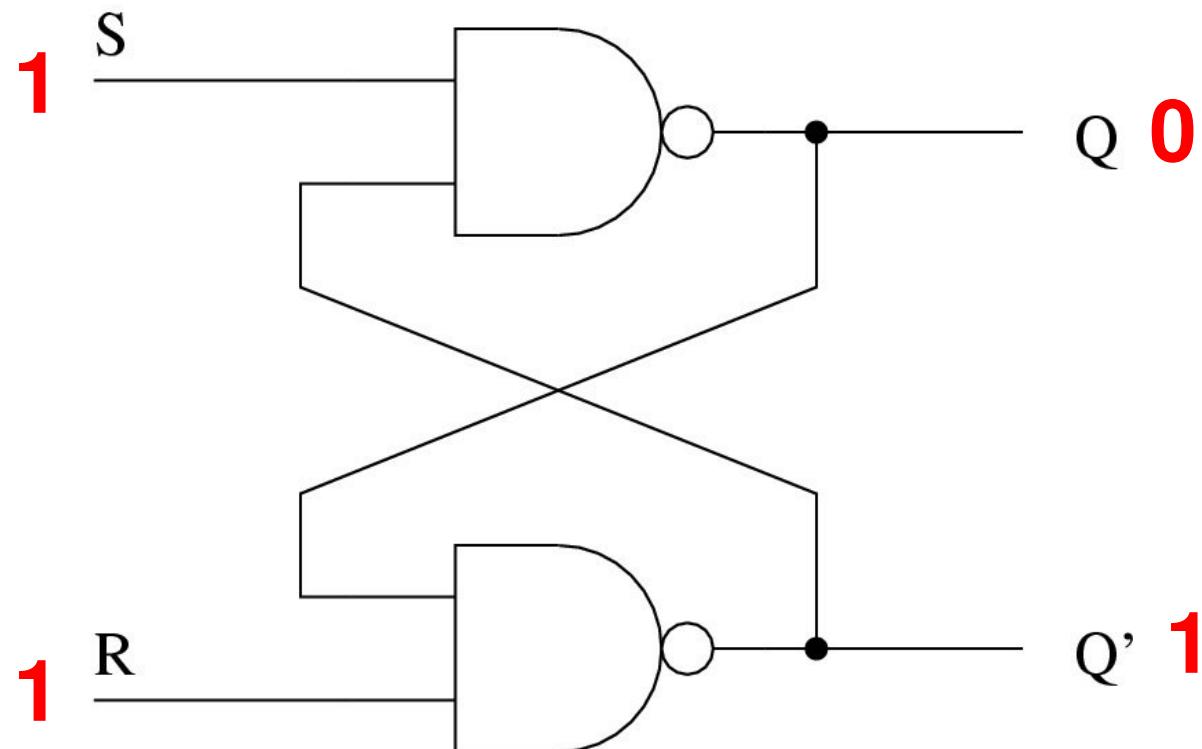


Is this a stable state?

Yes!


# NAND Latch

What happens with S is set to 0?

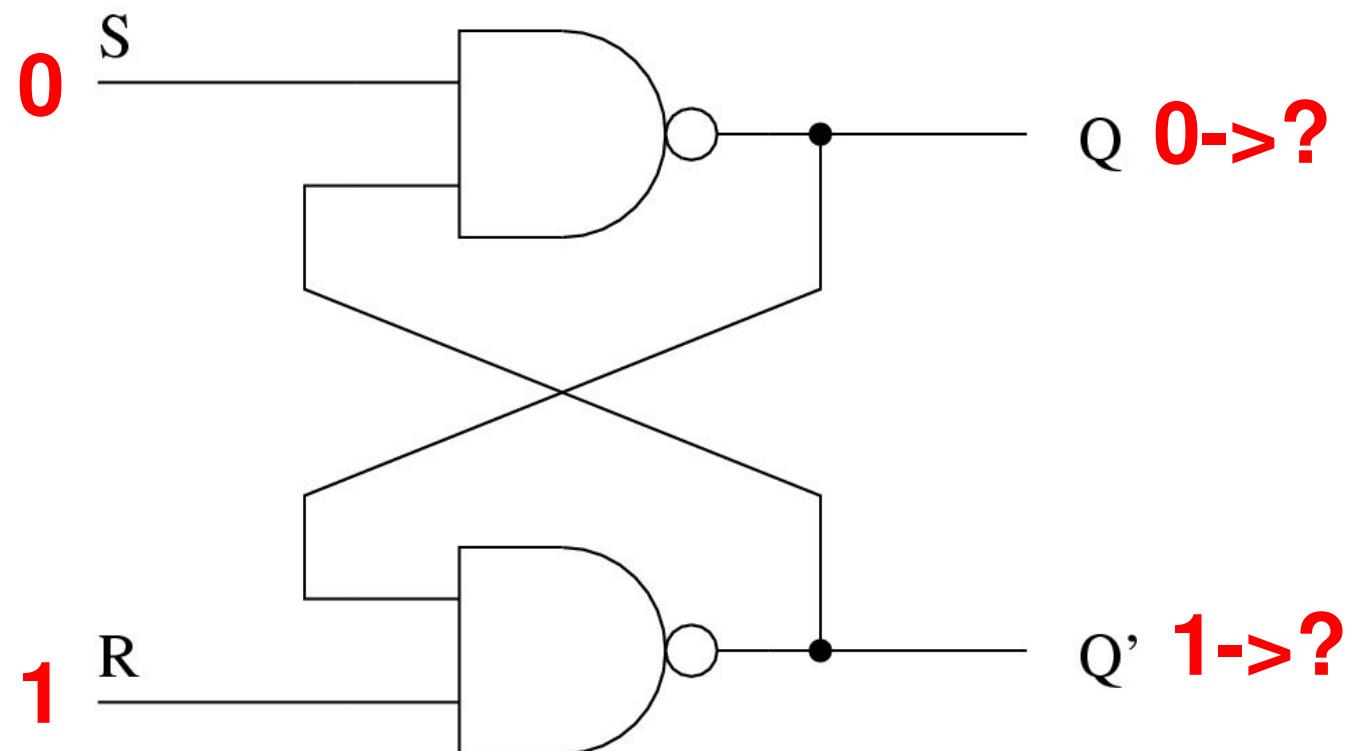

# NAND Latch


What happens with S is set to 0?

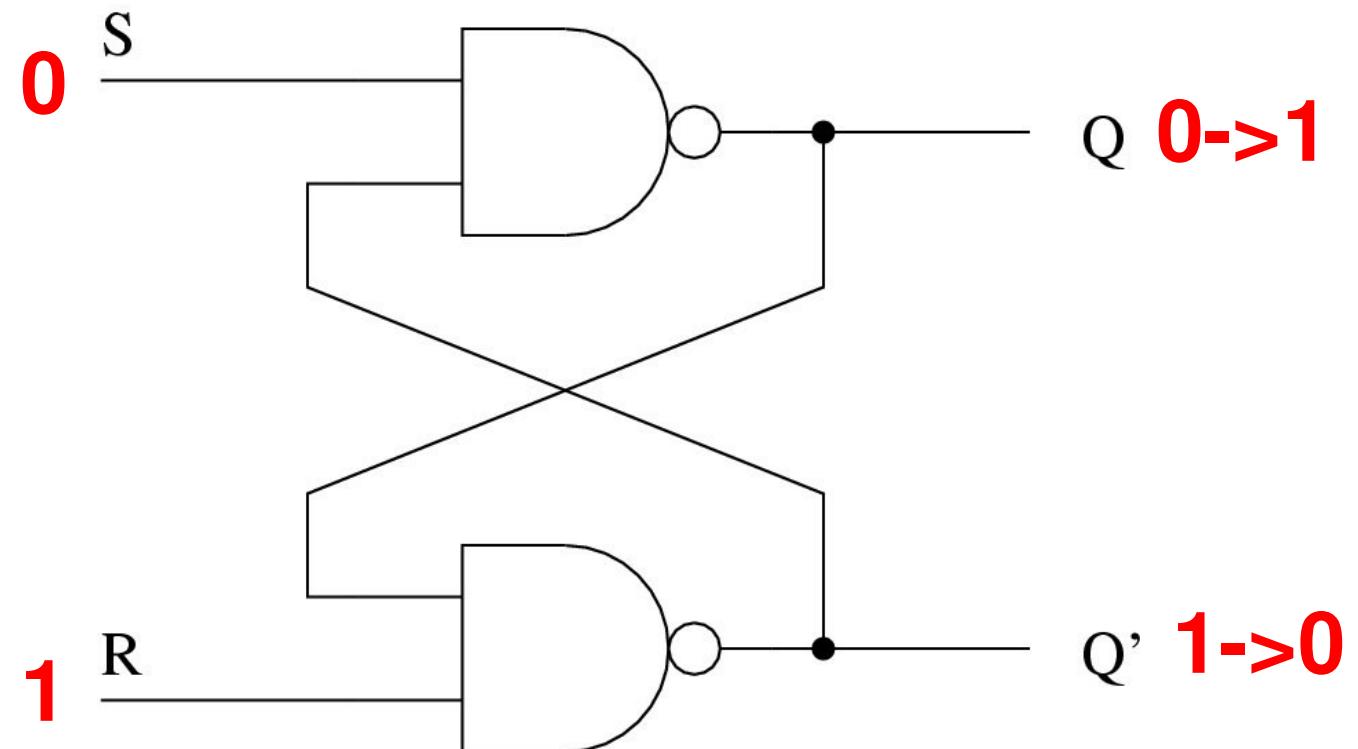

Q becomes 1 (thus S 'sets' Q)


# NAND Latch

Now S is set 1 – what happens?

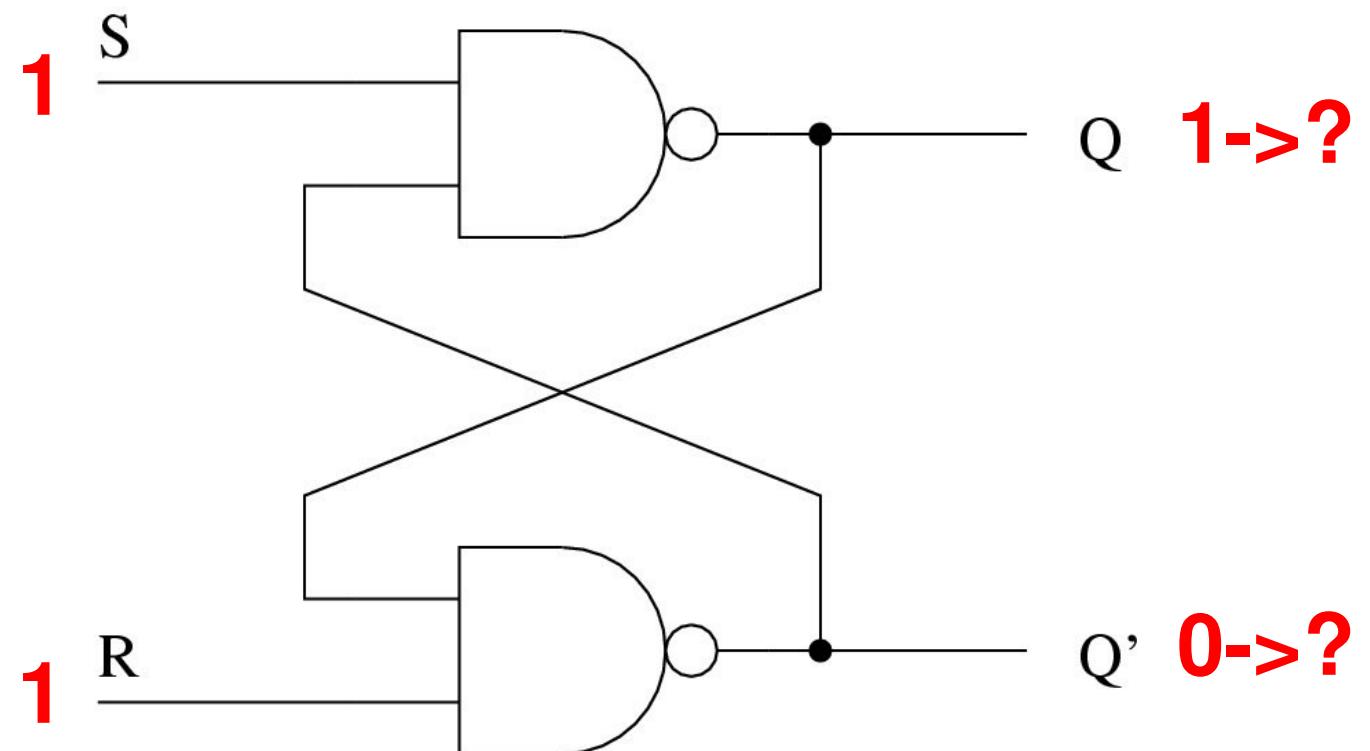

# NAND Latch


Q and Q' remain the same!

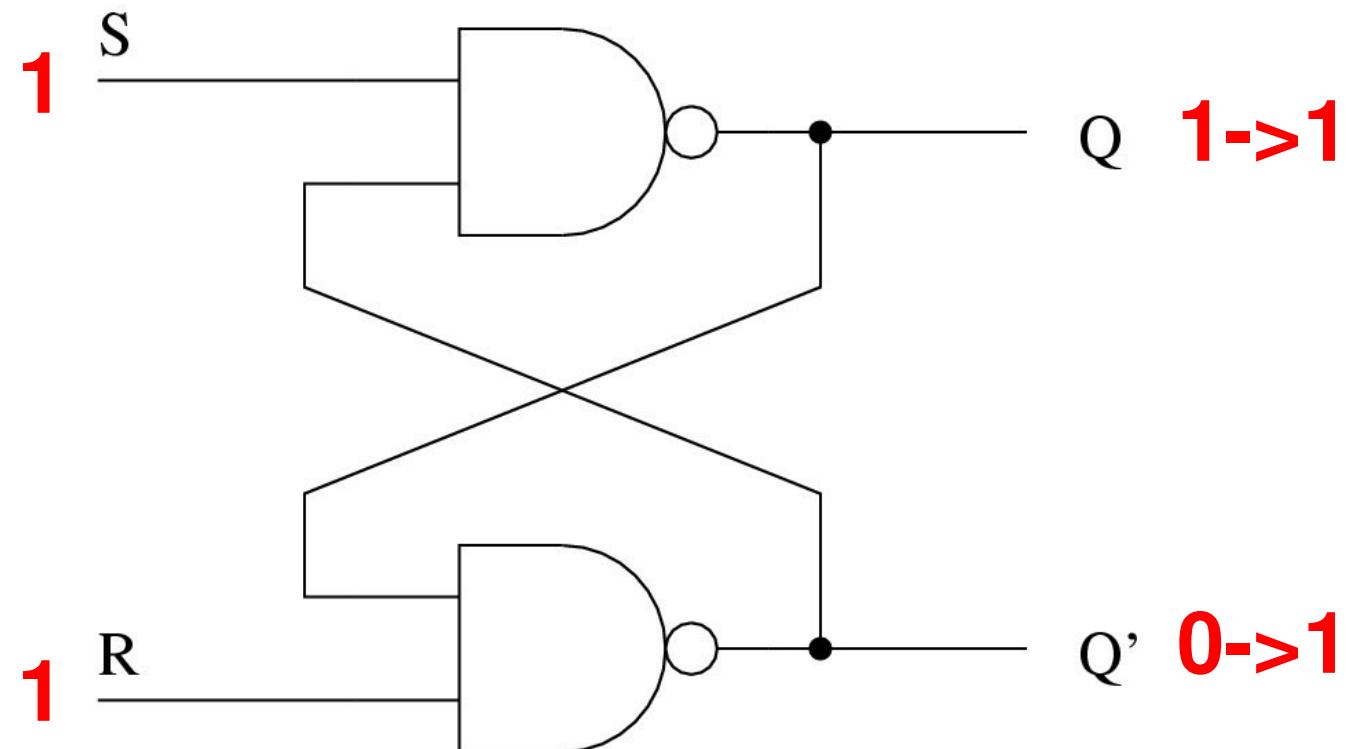

So Q and Q' retain a memory of old state!


# NAND Latch

Now set R to 0 – what happens?

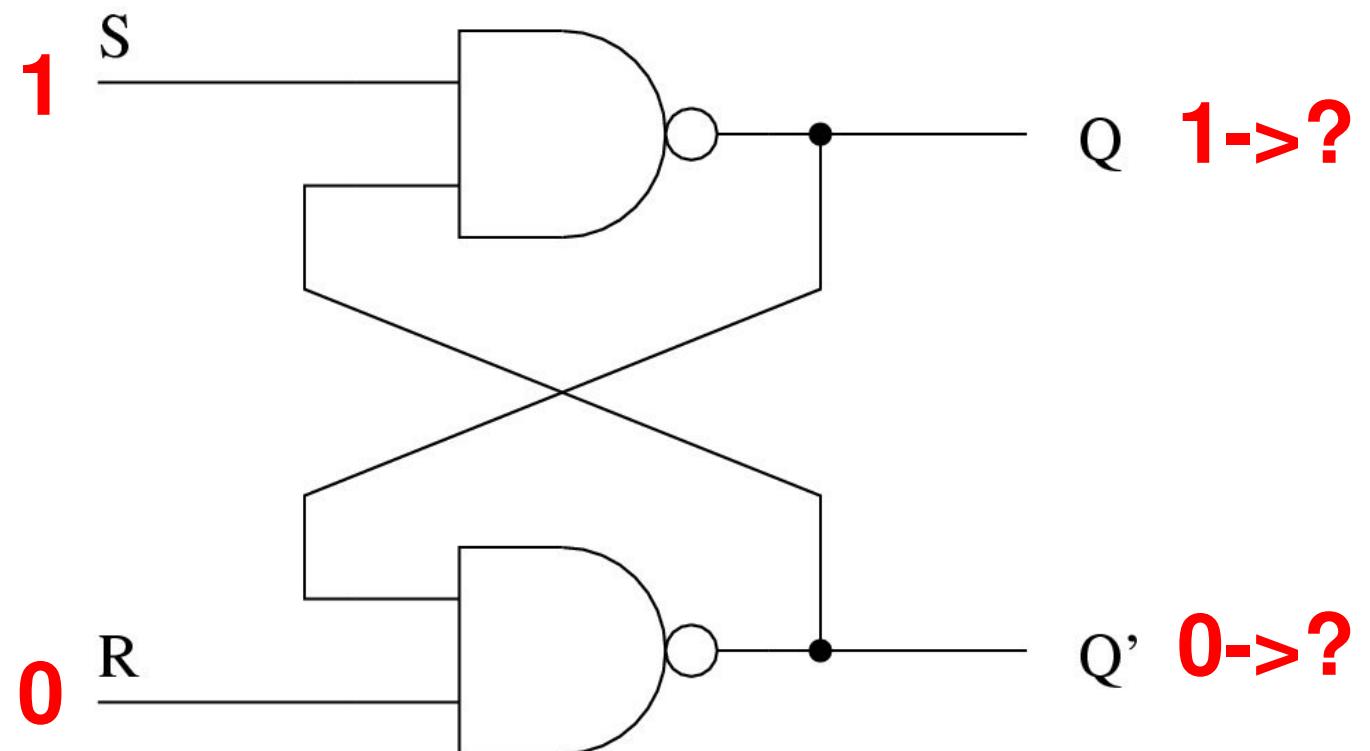

# NAND Latch


Now set R to 0 – what happens?

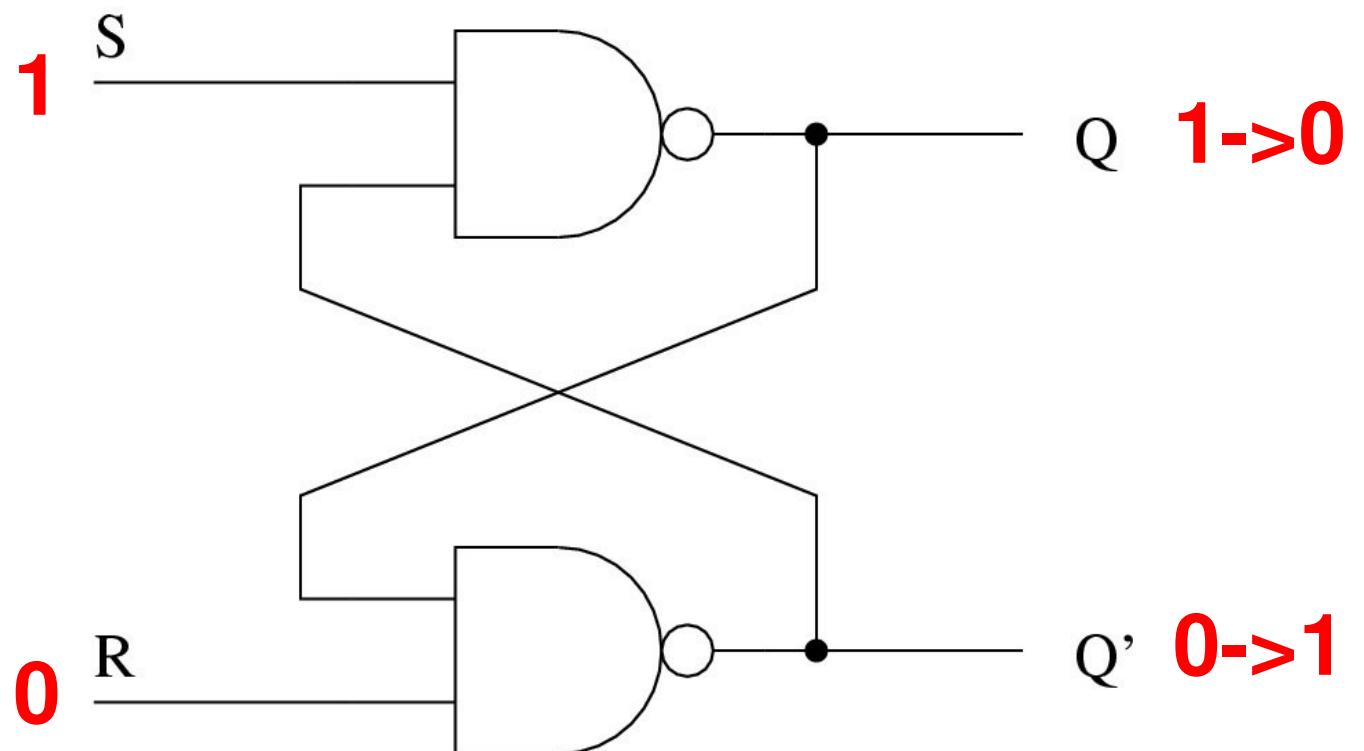

The state flips back (Q is 'reset')


# NAND Latch

Finally: set R to 1 – what happens?

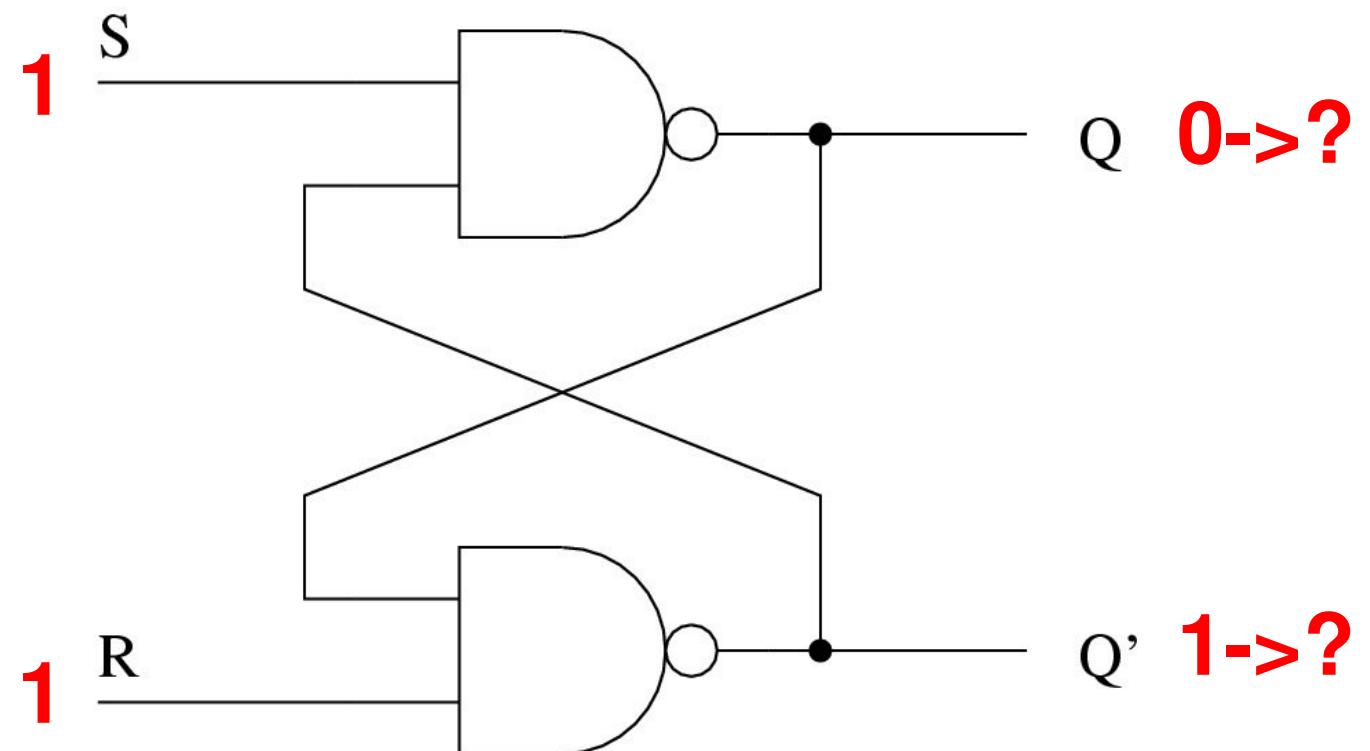


# NAND Latch

Finally: set R to 1 – what happens?

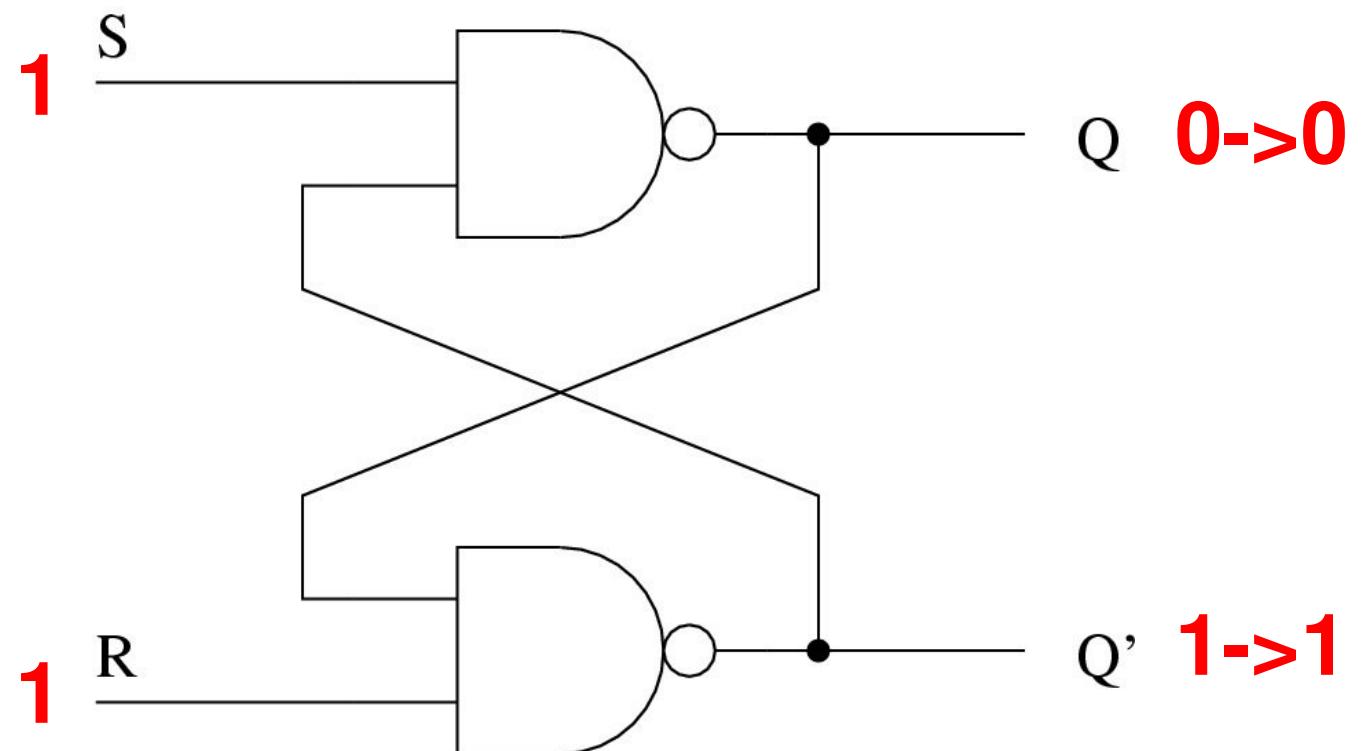


Q and Q' do not change state


# Timing Diagram Representation

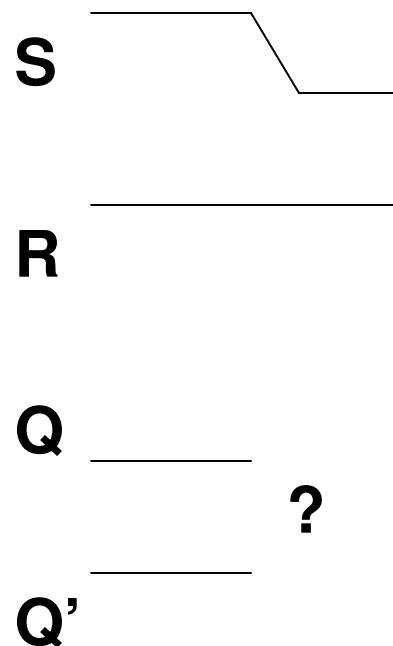

# Timing Diagram Representation

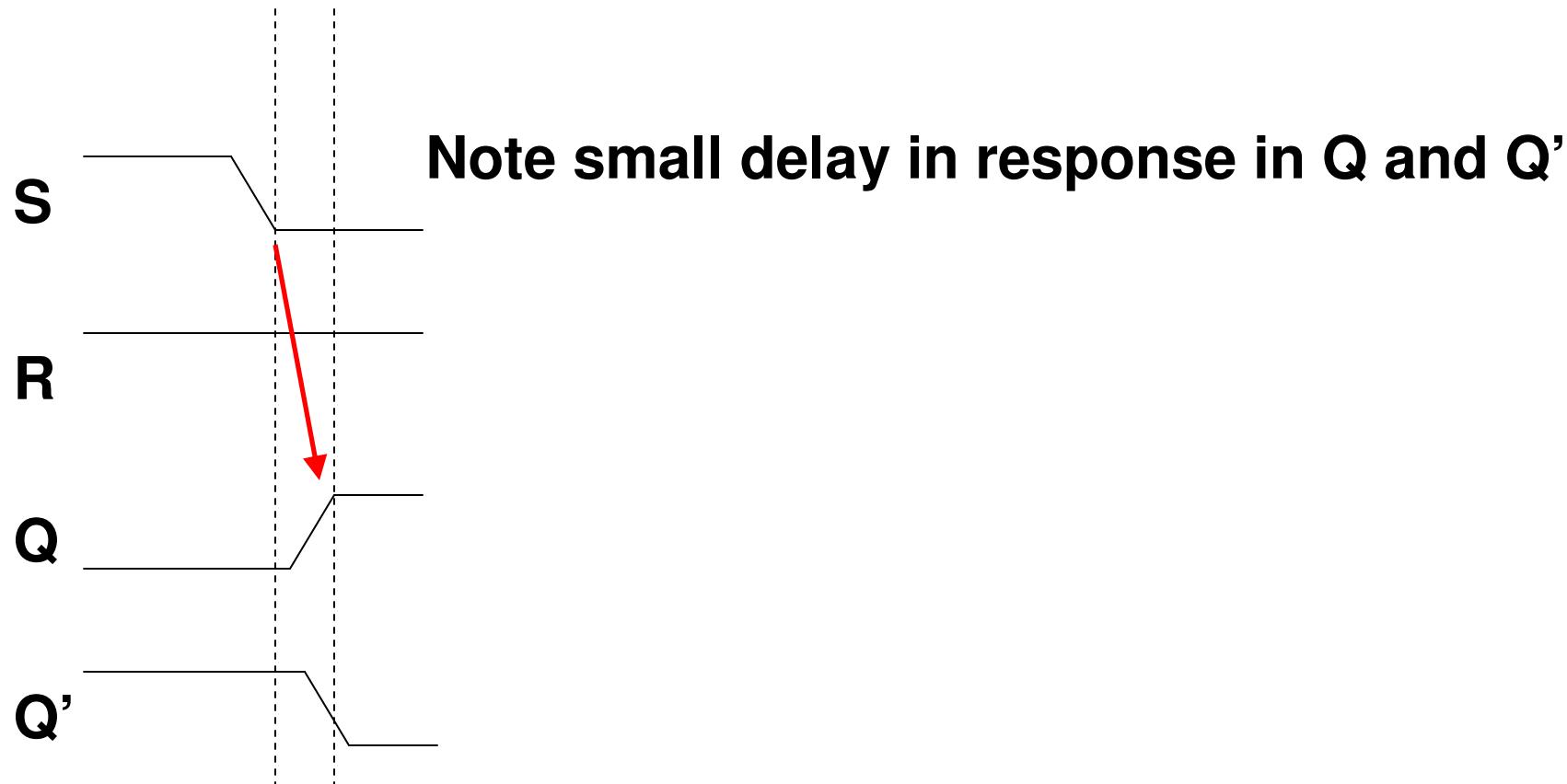


# Timing Diagram Representation

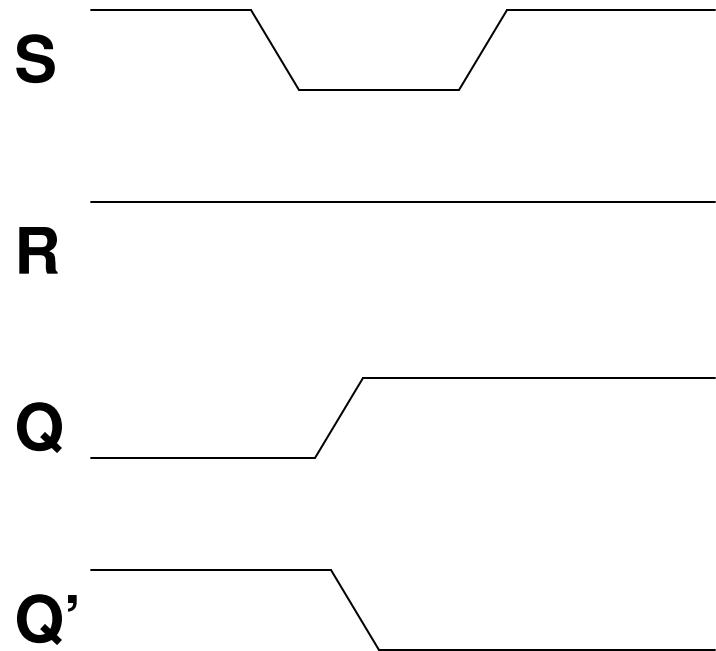


When S returns to high –  
both Q and Q' remain in  
the same state


# Timing Diagram Representation

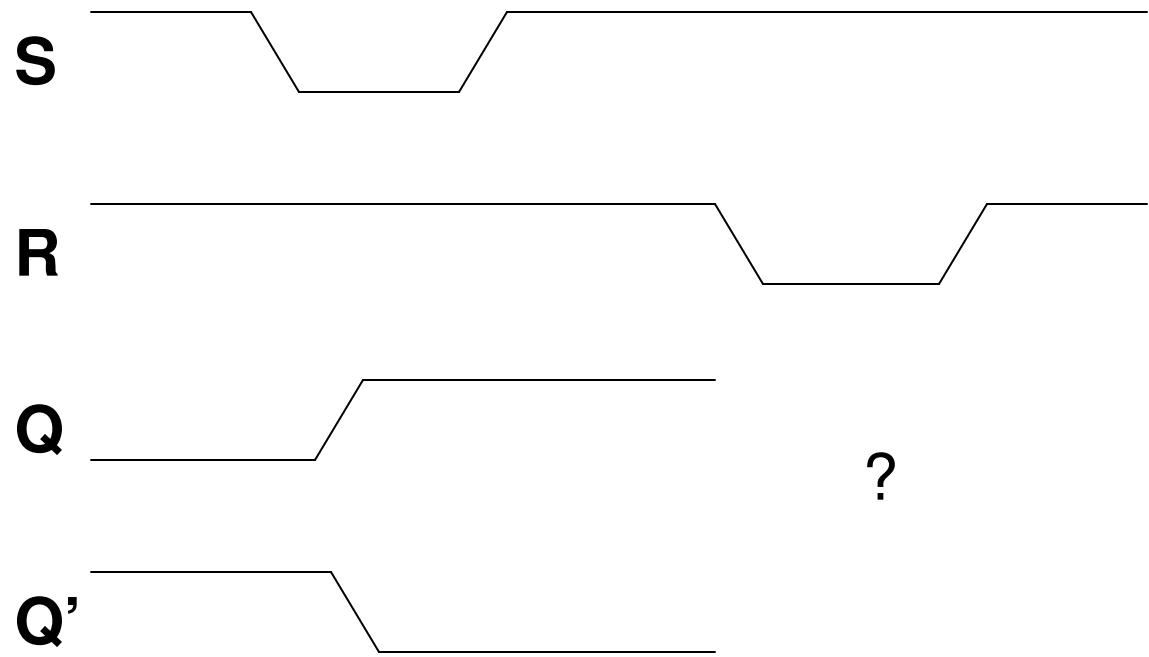


# Timing Diagram Representation

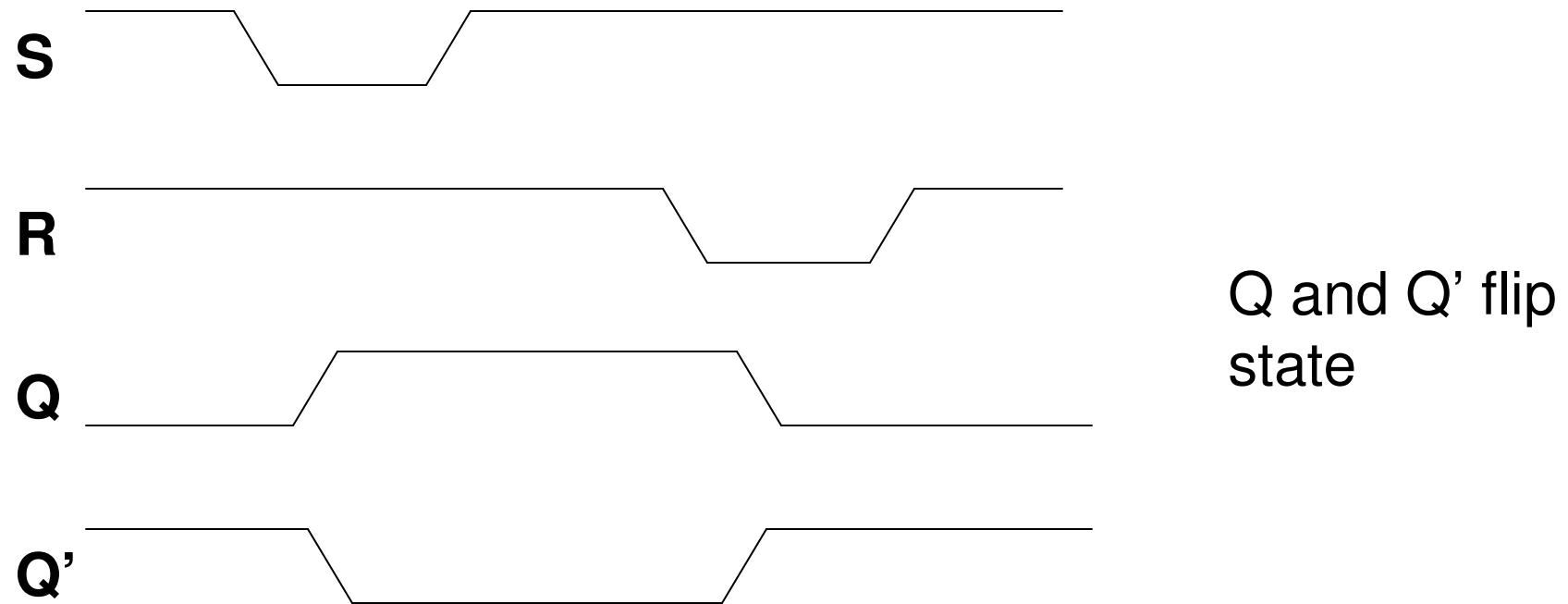

# Timing Diagram Representation

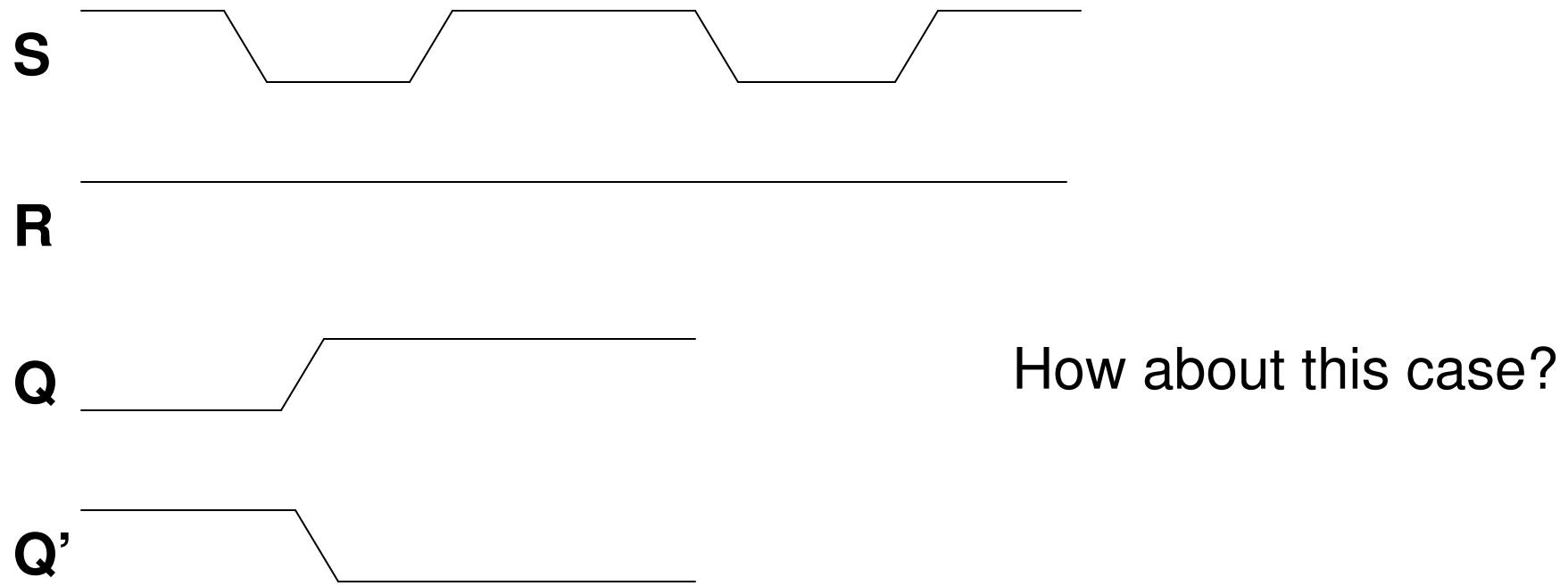

# Timing Diagram Representation

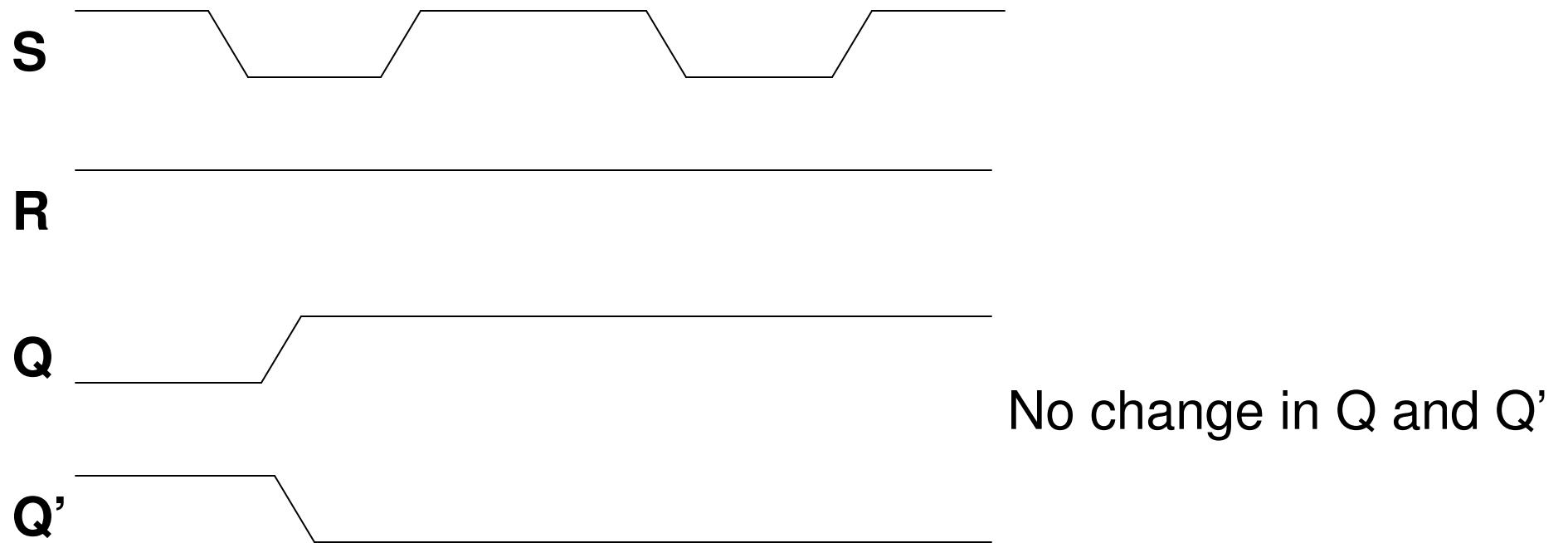

# Next Time

- Microprocessors
  - Watch the schedule page for Thursday reading