

# Last Time

## Analog Circuits Review

- Voltage
- Amperage
- Resistance
- Capacitance

# Today

- A bit more on analog circuits
  - Another RC circuit example
  - Transistors
- Analog to digital circuits
  - Transistors to basic logic gates
  - Introduction to Boolean Algebra

# Administrivia

Lab hours:

Lab location: EL 124

- If you do not find the lab open, find me in my office (EL 152)

# Today: Introduction to Digital Logic

- Binary encoding
- Boolean algebra
- Transistors to logic gates

# Encoding Information

In your ‘circuits and sensors’ class: how did you encode information?

- e.g., the acceleration measured by your accelerometer?
- or the rate of bend of a piezoelectric device?

# Encoding Information

Following some form of (implementation dependent) analog conditioning:

- Acceleration (or bend rate) is encoded in the voltage that is output from the circuit
- As acceleration increases, the voltage also increases

# Encoding Information

Following some form of (implementation dependent) analog conditioning:

- Acceleration (or bend rate) is encoded in the voltage that is output from the circuit
- As acceleration increases, the voltage also increases
- We say that this is an **analog** or **continuous** encoding of the information

# Analog Encoding

What is the problem with analog encoding?

# Last Time

- R-C circuits
- Transistors
- Analog encoding of information

# Today

- Digital encoding of information
- Using transistors to build basic computing devices
- Boolean algebra

# Administrivia

- HW 1: will go out sometime on Friday
  - Due February 6th
- Office hours posted (see the announcement on D2L)

# PulsePool Project

# Analog Encoding

What is the problem with analog encoding?

- Small injections of noise – either in the sensor itself or from external sources – will affect this analog signal
- This leads to errors in how we interpret the sensory data

How do we fix this?

# Digital Encoding

How do we fix this?

- At any instant, a single signal encodes one of two values:
  - A voltage around 0 (zero) Volts is interpreted as one value
  - A voltage around +5 V is interpreted as another value

# Binary Encoding

- Binary digits can have one of two values: 0 or 1
- We call 0V a binary “0” (or FALSE)
- And +5V a binary “1” (or TRUE)

# Binary Encoding

- Exactly what these levels are depends on the technology that is used (it is common now to see +1.8V as a binary 1 in low-power processors)
- This encoding is much less sensitive to noise: small changes in voltage do not affect how we interpret the signal

# Transistors


What do transistors do for us?

- They act as current amplifiers
- But: we can use them as electronic switches to process digital signals
 
# Transistors to Digital Processing


Consider the following circuit:

- What is the output given an input of 0V?
- An input of +5V?



 
# Transistors to Digital Processing

- Input: 0V -> Output +5V
- Input: +5V -> Output 0V
- We call this a “NOT” gate



# The NOT Gate

- Logical Symbol:

 

- Algebraic Notation:  $B = \overline{A}$

- Truth Table:


A	B
0	1
1	0

# A Two-Input Gate

+5V


What does this  
circuit compute?

- A and B are inputs
- C is the output

 

# The “NAND” Gate

- Logical Symbol:

 


- Algebraic Notation:  $C = \overline{A^*B} = \overline{AB}$

- Truth Table:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

# The “AND” Gate

- Logical Symbol:

 


- Algebraic Notation:  $C = A^*B = AB$

- Truth Table:

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


# Yet Another Gate

# What does this circuit compute?

 

# The “NOR” Gate

- Logical Symbol:

 


- Algebraic Notation:  $C = \overline{A+B}$

- Truth Table:

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

# The “OR” Gate

- Logical Symbol:

 



- Algebraic Notation:  $C = A+B$

- Truth Table:

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

  
# N-Input Gates

Gates can have an arbitrary number of inputs (2,3,4,8,16 are common)



# Exclusive OR (“XOR”) Gates

- Logical Symbol:

 


- Algebraic Notation:  $C = A \oplus B$

- Truth Table:

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

How would we implement this with AND/OR/NOT gates?

# An XOR Implementation

 

# An Example

Problem: implement an alarm system

- There are 3 inputs:
  - Door open (“1” represents open)
  - Window open
  - Alarm active (“1” represents active)
- And one output:
  - Siren is on (“1” represents on) when either the door or window are open – but only if the alarm is active

What is the truth table?


# Alarm Example: Truth Table

D	W	A	Siren
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\begin{array}{r} \overline{D} W A \\ + \\ D \overline{W} A \\ + \\ D W A \end{array}$$
 
# Alarm Example: Circuit

$$\text{Siren} = \overline{D} \text{ W A} + D \overline{W} \text{ A} + D \text{ W A}$$




# Alarm Example: Circuit

Is a simpler circuit possible?

# Alarm Example: Truth Table

D	W	A	Siren
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Alarm: An Alternative Circuit

 

# Next Time

- Some notes on Boolean Algebra
- DeMorgan's Laws
- Multiplexers
- Demultiplexers
- Readings from [play-hookey.com](http://play-hookey.com) (see the schedule)

# Last Time

- Transistors (analog) to logic (digital)
- Basic gates: AND, OR, NOT
- Other gates: XOR, NOR, NAND
- Basics of Boolean Algebra

These tools form the basis of computation in digital computers

# Today

More complicated circuits

Circuit reduction tools:

- Boolean Algebra
- DeMorgan's Laws

# Administrivia

- Homework 1 is posted already
  - With today's class, you have all of the tools that you need

# Alarm Example: Truth Table

D	W	A	Siren
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\begin{array}{l} \xrightarrow{\quad} \overline{D} W A \\ + \\ \xrightarrow{\quad} D \overline{W} A \\ + \\ \xrightarrow{\quad} D W A \end{array}$$

# Alarm Example: Truth Table

D	W	A	Siren
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

“minterm”

$$\overline{D} \overline{W} A + D \overline{W} A + D W A$$

# Minterms

- AND containing all function inputs
  - in our example these are D, W, A
- Some of the inputs may be “NOT’ed”
- Called a “minterm” because the AND is
  - 1 for exactly one case, and
  - 0 otherwise

# Minterm Approach to Representing a Truth Table/Function

- OR together a set of minterms:
  - One minterm for each row for which the output is 1
- Example:
$$\text{Siren} = \overline{D} \ W \ A + D \ \overline{W} \ A + D \ W \ A$$
- Circuit is correct, but may not be smallest

# Boolean Algebra

- There are exactly two numbers in Boolean System: “0” and “1”
- You are already familiar with the “integers”:  $\{ \dots -2, -1, 0, 1, 2, \dots \}$ 
  - (and Integer Algebra)

# Boolean Algebra

- Like the integers, Boolean Algebra has the following operators:

		Integers	Boolean
+		addition	OR
*		product	AND
inverse		negation	NOT

# NOT Operator

Definition:

- $\overline{0} = 0' = 1$
- $\overline{1} = 1' = 0$

NOTE: this is identical to our truth table (just a slightly different notation)

Suppose that “X” is a Boolean variable,  
then:

- $\overline{\overline{X}} = X'' = X$

# OR (+) Operator

Definition:

- $0+0 = 0$
- $0+1 = 1$
- $1+0 = 1$
- $1+1 = 1$

# OR (+) Operator

Suppose “X” is a Boolean variable, then:

- $0 + X = X$
- $1 + X = 1$
- $X + X = X$
- $X + X' = 1$

# AND (\*) Operator

Definition:

- $0^*0 = 0$
- $0^*1 = 0$
- $1^*0 = 0$
- $1^*1 = 1$

# AND (\*) Operator

Suppose “X” is a Boolean variable, then:

- $0 * X = 0$
- $1 * X = X$
- $X * X = X$
- $X * X' = 0$

# Boolean Algebra Rules: Precedence

The AND operator applies before the OR operator:

$$A * B + C = (A * B) + C$$

$$A + B * C = A + (B * C)$$

# Boolean Algebra Rules: Association Law

If there are several AND operations, it does not matter which order they are applied in:

$$A * B * C = (A * B) * C = A * (B * C)$$

# Boolean Algebra Rules: Association Law

Likewise for the OR operator:

$$A + B + C = (A + B) + C = A + (B + C)$$

# Boolean Algebra Rules: Distributive Law

AND distributes across OR:

$$A * (B + C) = (A * B) + (A * C)$$

$$A + (B * C) = (A + B) * (A + C)$$

# Boolean Algebra Rules: Commutative Law

Both AND and OR are symmetric operators  
(the order of the variables does not  
matter):

$$A + B = B + A$$

$$A * B = B * A$$

# DeMorgan's Laws

$$(A * B)' = A' + B'$$

How do we convince ourselves that this is true?

# Proof by Truth Table

A	B	$(A * B)'$	$A' + B'$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

NOTE:  
change in  
the NOT  
notation

# DeMorgan's Laws (cont)

$$(A + B)' = A' * B'$$

# Proof by Truth Table

A	B	$(A + B)'$	$A' * B'$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

# Alarm Example: Truth Table

D	W	A	Siren
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\begin{array}{l} \xrightarrow{\hspace{1cm}} D' W A \\ + \\ \xrightarrow{\hspace{1cm}} D W' A \\ + \\ \xrightarrow{\hspace{1cm}} D W A \end{array}$$


# Reduction with Algebra

$D' W A + D W' A + D W A$	
$= D' W A + D W' A + D W A + D W A$	$X + X = X$
$= D' W A + D W A + D W' A + D W A$	Commutative Law
$= D' W A + D W A + W' D A + W D A$	"
$= (D' + D) W A + (W' + W) D A$	Assoc + Dist Laws
$= 1^* W A + 1^* D A$	$X + X' = 1$

# Reduction with Algebra (cont)

$1^* W A + 1^* D A$	
$= W A + D A$	$X * 1 = X$
$= (W + D) * A$	Distributive Law

We have the same circuit as before!

 

# Multiple Output Variables

Suppose we have a function with multiple output variables?

- How do we handle this?

# Multiple Output Variables

How do we handle this?

- One algebraic expression for each output
- But: in the final implementation, some sub-circuits may be shared


# More Logical Components

- Multiplexer
- Demultiplexer
- Tristate buffer
 
# 2-Input Multiplexer

A multiplexer is a device that selects between two input lines


- A & B are the inputs
- S is the selection signal (also an input)
- C is a copy of A if  $S=0$
- C is a copy of B if  $S=1$


 
# 2-Input Multiplexer

A multiplexer is a device that selects between two input lines


- A & B are the inputs
- S is the selection signal (also an input)
- C is a copy of A if  $S=0$
- C is a copy of B if  $S=1$


 
# 2-Input Multiplexer

A multiplexer is a device that selects between two input lines

- A & B are the inputs
- S is the selection signal (also an input)
- C is a copy of A if  $S=0$
- C is a copy of B if  $S=1$



# Multiplexer Truth Table

What does the algebraic expression look like?

S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Multiplexer Truth Table

S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$S'AB'$  ←

$S'AB$  ←

$SA'B$  ←

$SAB$  ←

# Multiplexer

$$C = S'AB' + S'AB + SA'B + SAB$$


Is there a simpler expression?

# Reduction with Algebra

$S'AB' + S'AB + SA'B + SAB$	
$= S'A(B' + B) + SB(A' + A)$	Associative + Distributive
$= S'A 1 + SB 1$	$X + X' = 1$
$= S'A + SB$	$X + 1 = X$

# Multiplexer Implementation


$$C = S'A + SB$$

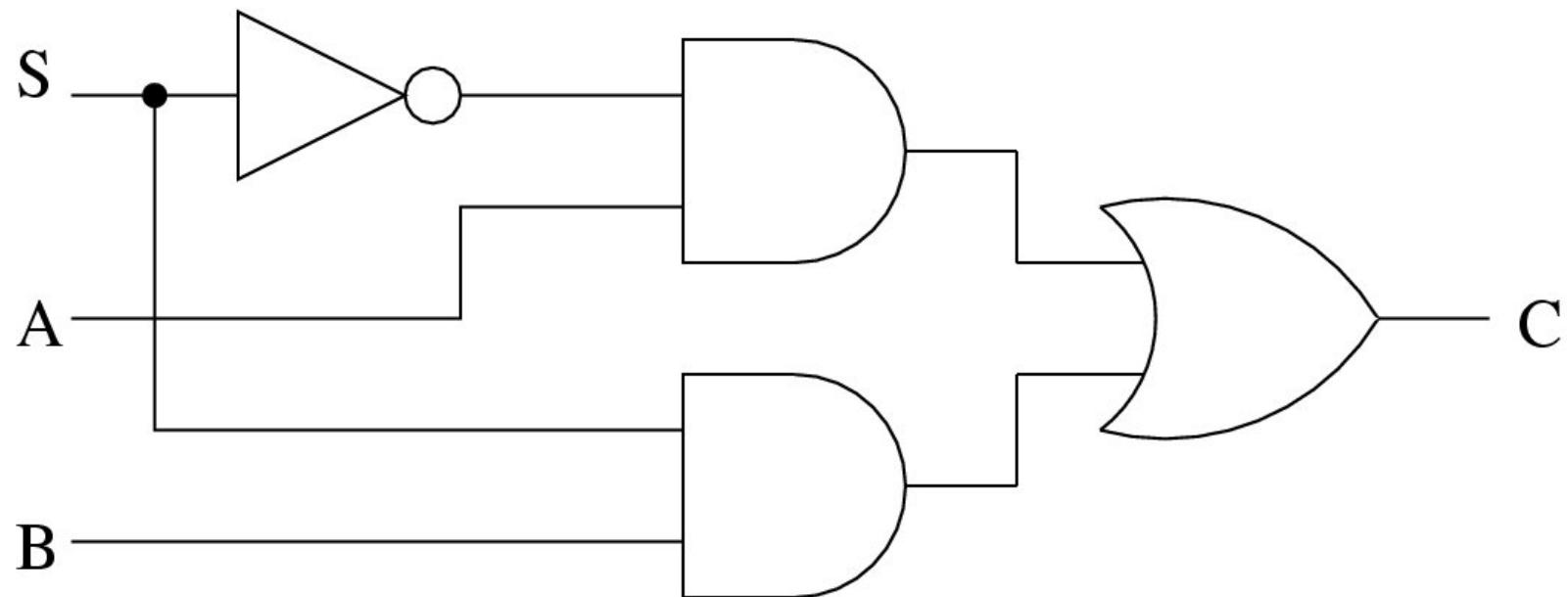
 
# N-Input Multiplexer

Suppose we want to select from between  $N$  different inputs.

- This requires more than one select line. How many?




# N-Input Multiplexer

How many select lines?

- $M = \log_2 N$   
or
- $N = 2^M$

 What would the  $N=8$  implementation look like?




# 8-Input Multiplexer Implementation

$$C = I_0 S_2' S_1' S_0' + I_1 S_2' S_1' S_0 + I_2 S_2' S_1 S_0' + \\ I_3 S_2' S_1 S_0 + I_4 S_2 S_1' S_0' + I_5 S_2 S_1' S_0 + \\ I_6 S_2 S_1 S_0' + I_7 S_2 S_1 S_0$$

Note that we have one of each possible select line combination (or addressing terms)

 
# Demultiplexer

- The multiplexer reduces  $N$  signals down to 1 (with  $M$  select lines)
- A demultiplexer routes a data input ( $D$ ) to one of  $N$  output lines ( $A_s$ )
  - Which  $A$  depends on the select lines



 
# Demultiplexer

- The multiplexer reduces  $N$  signals down to 1 (with  $M$  select lines)
- A demultiplexer routes a data input ( $D$ ) to one of  $N$  output lines ( $A_s$ )
  - Which  $A$  depends on the select lines



 
# Demultiplexer

- The multiplexer reduces  $N$  signals down to 1 (with  $M$  select lines)
- A demultiplexer routes a data input ( $D$ ) to one of  $N$  output lines ( $A_s$ )
  - Which  $A$  depends on the select lines



 
# Demultiplexer Notes

- The symbol that we use is the same as for the multiplexer
  - Select lines are still inputs
  - But the other inputs and outputs are reversed
- Multiplexer or demultiplexer in a circuit: you must infer this from the labels or from the rest of the circuit
  - When in doubt, ask




# Demultiplexer Truth Table

S	D		$A_1$	$A_0$
0	0			
0	1			
1	0			
1	1			

 


# Demultiplexer Truth Table

S	D		$A_1$	$A_0$
0	0		0	0
0	1		0	1
1	0		0	0
1	1		1	0

 


# Demultiplexer Algebraic Specification

S	D		$A_1$	$A_0$
0	0		0	0
0	1		0	1
1	0		0	0
1	1		1	0

 

# Demultiplexer Algebraic Specification

S	D		A <sub>1</sub>	A <sub>0</sub>
0	0		0	0
0	1		0	1
1	0		0	0
1	1		1	0

 


$$A_0 = S'D$$

# Demultiplexer Algebraic Specification

S	D		A <sub>1</sub>	A <sub>0</sub>
0	0		0	0
0	1		0	1
1	0		0	0
1	1		1	0

$$A_1 = SD$$

$$A_0 = S'D$$

 

# Demultiplexer Circuit


$$A_0 = S'D$$

$$A_1 = SD$$

# Demultiplexer Circuit

$$A_0 = S'D$$

$$A_1 = SD$$

 

# Next Time

- A bit more on demultiplexers
- Tristate buffers
- Sequential logic

# Last Time

- Boolean Algebra
- Circuit design process:
  - Start with a truth table
  - Convert to “minterms” algebraic representation
  - Simplify using Boolean Algebra
  - Translate into circuit diagram
- Multiplexers/demultiplexers

# Today

- A bit more on (de)multiplexers
- Sequential logic: introducing memory
- D Flip-Flops
- Circuits with memory

# Administrivia


- Homework 1 due on Tuesday

# Equivalent Circuits

- The circuits that come directly from our “minterm” algebraic expression consist of a set of AND gates whose outputs are OR’ed together
- This AND-OR cascade can be replaced directly with a NAND-NAND cascade
  - You will see some circuit examples that use this form

# Demultiplexer Algebraic Specification


S	D		$A_1$	$A_0$
0	0		0	0
0	1		0	1
1	0		0	0
1	1		1	0

 

# Demultiplexer Circuit


$$A_0 = S'D$$

$$A_1 = SD$$

 
 
# 2-Input Demultiplexer

Here, “input” refers to the number of select lines




# 2-Input Demultiplexer Truth Table

$S_1$	$S_0$	D		$A_3$	$A_2$	$A_1$	$A_0$
0	0	0		0	0	0	0
0	0	1		0	0	0	1
0	1	0		0	0	0	0
0	1	1		0	0	1	0
1	0	0		0	0	0	0
1	0	1		0	1	0	0
1	1	0		0	0	0	0
1	1	1		1	0	0	0

# Demultiplexer Implementation

- What does it look like?

# Demultiplexer Implementation

 


# Another Implementation

- Assume that you have a simple demultiplexer (1 select line / 2 outputs)
- How do you create a demultiplexer with 2 select lines and 4 outputs?
 
# Multiplexers Revisited

- Assume that you have a simple multiplexer (1 select line / 2 inputs)
- How do you create a multiplexer with 2 select lines and 4 inputs?




# Tristate Buffers

- Until now: the output line(s) of each device are driven either high or low
  - So the line is either a source or a sink of current
- Tristate buffers can do this or leave the line floating (as if it were not connected to anything)

# Tristate Buffers


S	A	B
0	0	floating
0	1	floating
1	0	0
1	1	1

 

How are tristate buffers useful?
 
# Tristate Buffers


We can wire the outputs of multiple tristate buffers together without any other logic



# Tristate Buffers

- We must guarantee that only one select line is active at any one time
- Tristate buffers will turn out to be useful when we start building data and address buses

# Another Tristate Buffer

 

What does the truth table look like?

# Another Tristate Buffer

S	A	B
0	0	0
0	1	1
1	0	floating
1	1	floating

