


Embedded Real-Time Systems (AME 3623)

Homework 1 Solutions

February 8, 2008

Question 1

Consider the following circuit.

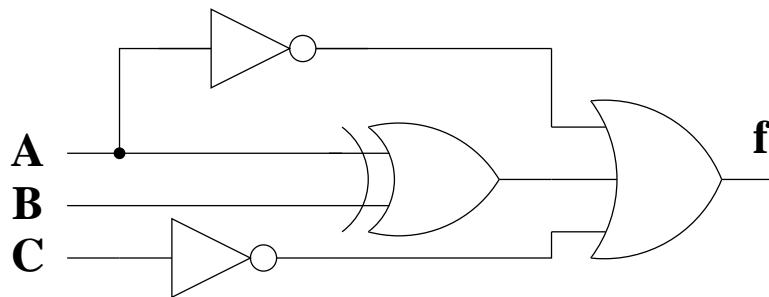

1. (10 pts) What is the corresponding truth table?


Shortcut: f is true any time A or C are false.

A	B	C	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

2. (10 pts) Show the simplified circuit (this should require very little reduction).

The short path: first design the circuit for \bar{f} and then add a NOT to the end.

This gives us:

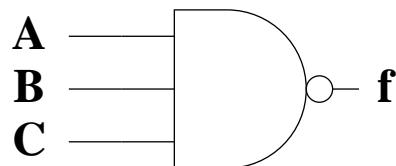

The direct reduction approach:

$$\begin{aligned}
 & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}C \\
 & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \\
 & \quad \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}C \\
 & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \\
 & \quad \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \\
 & \bar{A}\bar{B}(\bar{C} + C) + \bar{A}B(\bar{C} + C) + \bar{A}\bar{B}(\bar{C} + C) + A\bar{B}(\bar{C} + C) + \\
 & \quad \bar{A}(B + \bar{B})\bar{C} + A(\bar{B} + B)\bar{C} \\
 & \bar{A}\bar{B} + \bar{A}B + \bar{A}\bar{B} + A\bar{B} + A\bar{C} + A\bar{C} \\
 & \bar{A}(\bar{B} + B) + (\bar{A} + A)\bar{B} + (\bar{A} + A)\bar{C} \\
 & \bar{A} + \bar{B} + \bar{C}
 \end{aligned}
 \quad \boxed{\begin{array}{l} \text{start} \\ \text{$X + X = X$} \\ \text{Commutative Law} \\ \text{Distributive Law} \\ \text{$X + \bar{X} = 1$, and} \\ \text{$X * 1 = X$} \\ \text{Distributive Law} \\ \text{$X + \bar{X} = 1$, and} \\ \text{$X * 1 = X$} \\ \text{DeMorgan's Law} \end{array}}$$

Note: partial reduction (so that complexity is less than the original circuit) is worth partial credit.

Question 2


Consider the following function:

A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

1. (10pts) Show the algebraic expression for the “minterm” form of the circuit (set of 3-term ANDs that are then ORed together).

$$f = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C + ABC$$

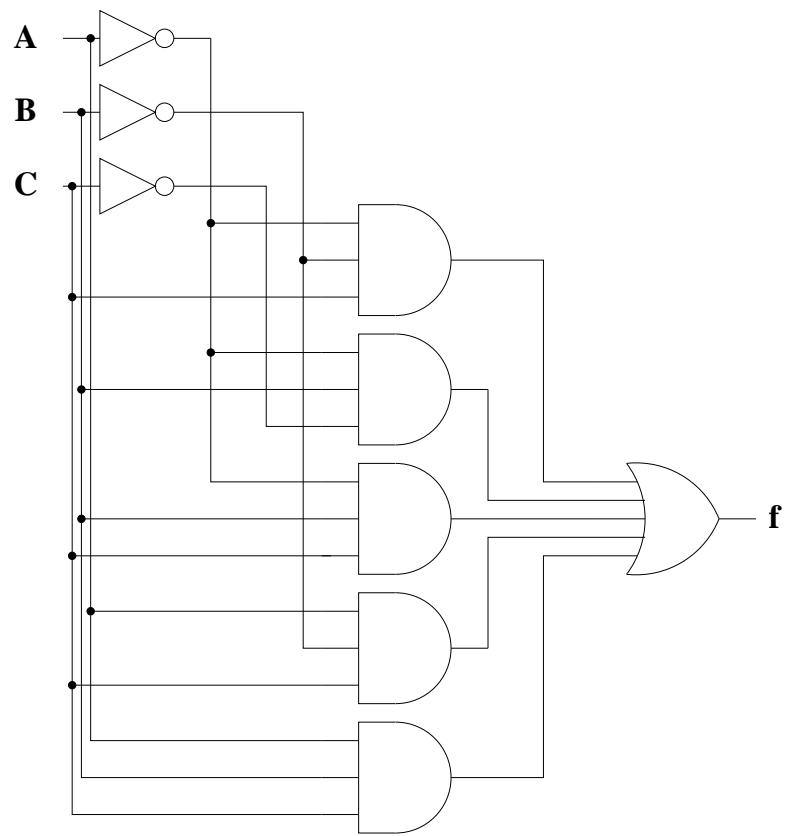2. (10pts) Show the corresponding circuit




3. (10pts) Reduce this algebraic expression to a minimal form (note that there may be more than one correct answer). **Show each step, showing the name of the algebraic rule that you use.**


$$\begin{aligned}
 & \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C + ABC & \text{Start} \\
 & \bar{A}(\bar{B}C + B\bar{C} + BC) + A(\bar{B} + B)C & \text{AssociativeLaw} \\
 & \bar{A}(\bar{B}C + B\bar{C} + BC + BC) + A(\bar{B} + B)C & X + X = X \\
 & \bar{A}(\bar{B}C + BC + B\bar{C} + BC) + A(\bar{B} + B)C & \text{CommutativeLaw} \\
 & \bar{A}((\bar{B} + B)C + B(\bar{C} + C)) + A(\bar{B} + B)C & \text{AssociativeLaw} \\
 & \bar{A}(C + B) + AC & X + \bar{X} = 1; X * 1 = X \quad (1) \\
 & \bar{A}C + \bar{A}B + AC & \text{DistributiveLaw} \\
 & \bar{A}B + \bar{A}C + AC & \text{CommutativeLaw} \\
 & \bar{A}B + (\bar{A} + A)C & \text{DistributiveLaw} \\
 & \bar{A}B + C & X + \bar{X} = 1; X * 1 = X
 \end{aligned}$$

Note: equation 1 is sufficient to receive full credit.

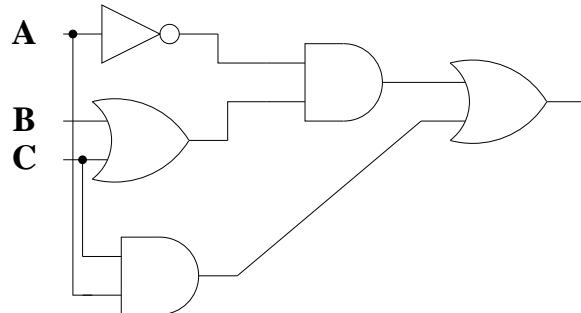4. (10pts) Show the corresponding circuit



OR

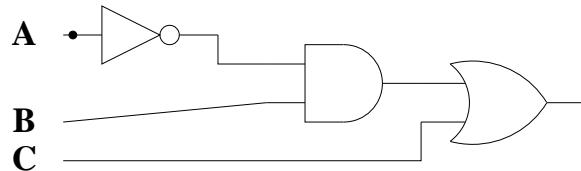

Question 3

Consider the following function:

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


1. (10pts) Show the algebraic expression for the “minterm” form of the circuit.

$$\bar{A}B\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$

2. (10pts) Reduce this algebraic expression to a minimal form. Show each step, showing the name of the algebraic rule that you use.

$$\begin{aligned}
 & \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C} + ABC \\
 & \bar{A}B\bar{C} + AB\bar{C} + A\bar{B}C + ABC && \text{Commutative Law} \\
 & (\bar{A} + A)B\bar{C} + A(\bar{B} + B)C && \text{Distributive Law} \\
 & B\bar{C} + AC && X + \bar{X} = 1 \text{ and } X * 1 = X
 \end{aligned}
 \tag{2}$$

3. (10pts) Show the reduced circuit.

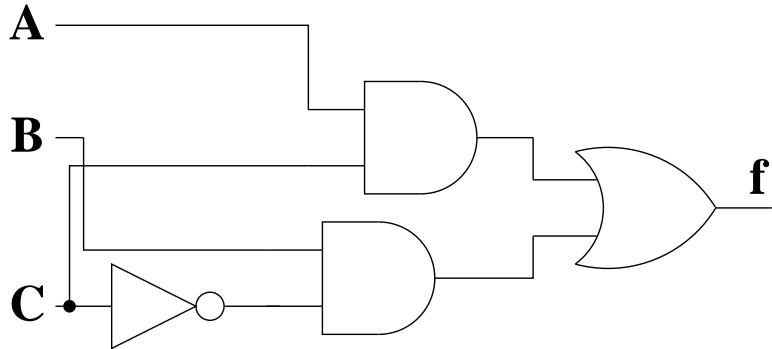

Question 4

1. (10 pts) Suppose you need a circuit to perform an AND between two inputs, but that you only have 2-input NAND gates. What would the circuit look like? Show the algebraic rules that you use.

In order to create an AND gate from a NAND, we need to invert the output of the NAND. So - the question is how to create an inverter from a NAND gate. The algebraic expression for our NAND gate is:

$$C = \overline{A * B}$$

We can wire inputs A and B to anything we like. In particular, we can choose: $B = A$. This gives us:

$$C = \overline{A * A}$$

Which simplifies to (by $X = X * X$):

$$C = \overline{A}$$



Alternatively, we can choose $B = 1$ (i.e. a constant):

$$C = \overline{A * 1}$$

Which simplifies to (by $X = X * 1$):

$$C = \overline{A}$$

The corresponding circuits are:

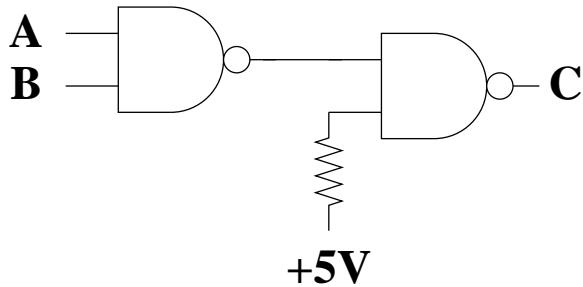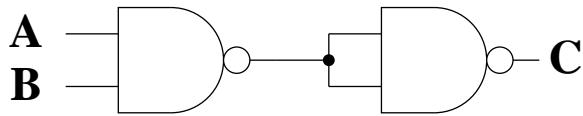

Note: it is acceptable for the latter answer to just have a logical '1' as the constant input into the 2nd NAND gate.

2. (10 pts) Suppose you need a circuit to perform an OR between two inputs, but that you only have 2-input NAND gates. What would the circuit look like? Show the algebraic rules that you use.

DeMorgan's Law gives us the relationship between AND and OR:

$$A + B = \overline{\overline{A} + \overline{B}}$$

In the previous question, we show how to use a NAND gate to implement an inverter. So - the resulting circuit is:

