

Embedded Real-Time Systems (AME 3623)

Homework 2

February 11, 2009

This homework assignment is due on Tuesday, February 24th at 5:00pm. Your work may be handed in electronically (use the **Homework 2** digital dropbox on D2L) or in hardcopy form (in person or in office).

This assignment must be done individually: do not share/discuss your answers with others or look at the answers of others.

Question 1


1. (5pts) Given the binary number: 010111010. What is the decimal equivalent? What is the hexadecimal equivalent? Show your work.
2. (5pts) Given the binary number: 110110111. What is the decimal equivalent? What is the hexadecimal equivalent? Show your work.

3. (5pts) Given the decimal number: 486. What is the binary equivalent?
Show your work (all of the steps of the algorithm that we discussed in class).

4. (5pts) Given the decimal number: 524. What is the binary equivalent?
Show your work.

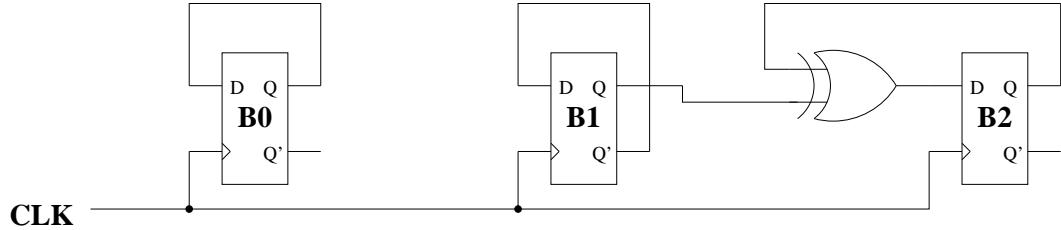Question 2

Consider the following circuit with input CLK :



1. (10pts) Assume that the initial state is: $Q0 = 0, Q1 = 0, Q2 = 0$ Show the timing diagram for $Q0, Q1$ and $Q2$ as the clock (CLK) is pulsed (show 6 transitions).
2. (10pts) Interpreting $Q2, Q1, Q0$ as a 3-bit binary number (with $Q0$ as the 1's digit), what is the sequence of values that this circuit produces?


3. (10pts) Assume that the initial state is: $Q0 = 1, Q1 = 0, Q2 = 1$ Show the timing diagram for $Q0, Q1$ and $Q2$ as the clock (CLK) is pulsed (show 6 transitions).

4. (10pts) Interpreting $Q2, Q1, Q0$ as a 3-bit binary number (with $Q0$ as the 1's digit), what is the sequence of values that this circuit produces?

5. (10pts) What is the mathematical function of this circuit?

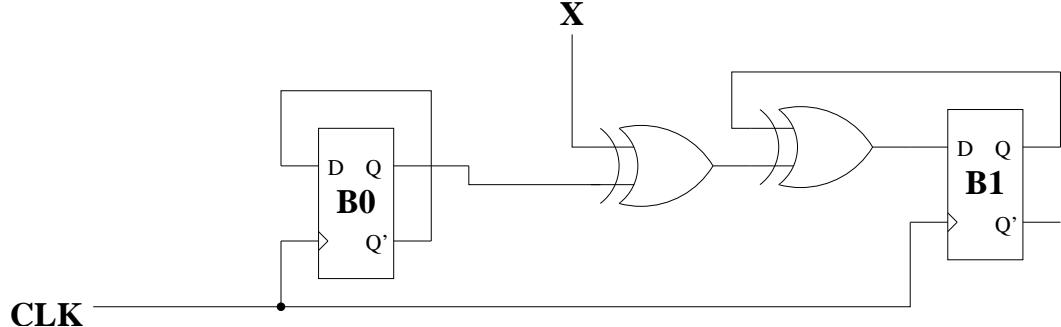Question 3

Consider the following circuit with inputs CLK and X :



1. (10pts) Assume that the initial state is: $Q0 = 1$ and $Q1 = 0$. Assume also that $X = 0$. Show the timing diagram for $Q0$ and $Q1$ as the clock (CLK) is pulsed.
2. (10pts) Interpreting $Q1, Q0$ as a 2-bit binary number (with $Q0$ as the 1's digit), what is the sequence of values that this circuit produces?

3. (10pts) What is the mathematical function of this circuit when $X = 0$?
4. (10pts) Assume the same initial state as above, and assume that $X = 1$. Show the timing diagram for $Q0$ and $Q1$ as the clock (CLK) is pulsed.
5. (10pts) What is the sequence of values that this circuit produces?

6. (10pts) What is the function of this circuit when $X = 1$?

Question 4

How much time did you spend on this homework assignment?