

# Last Time

- Circuit Reduction and Boolean Algebra
- Multiplexers
- Demultiplexers
- Tri-state buffers

# Today

- Finish circuit reduction example
- Dealing with time and memory
  
- Homework 1: due on Thursday

# Time

Until now: we have essentially ignored the issue of time


- We have assumed that our digital logic circuits perform their computations instantaneously
- Our digital logic circuits have been “stateless”
  - Once you present a new input, they forget everything about previous inputs
  - We call this type of digital system **combinatorial logic**

# Time


In reality, time is an important issue:

- Even our logic gates induce a small amount of delay (on the order of a few nanoseconds)
- For much of what we do – we actually want our circuits to have some form of memory


# Timing Notation

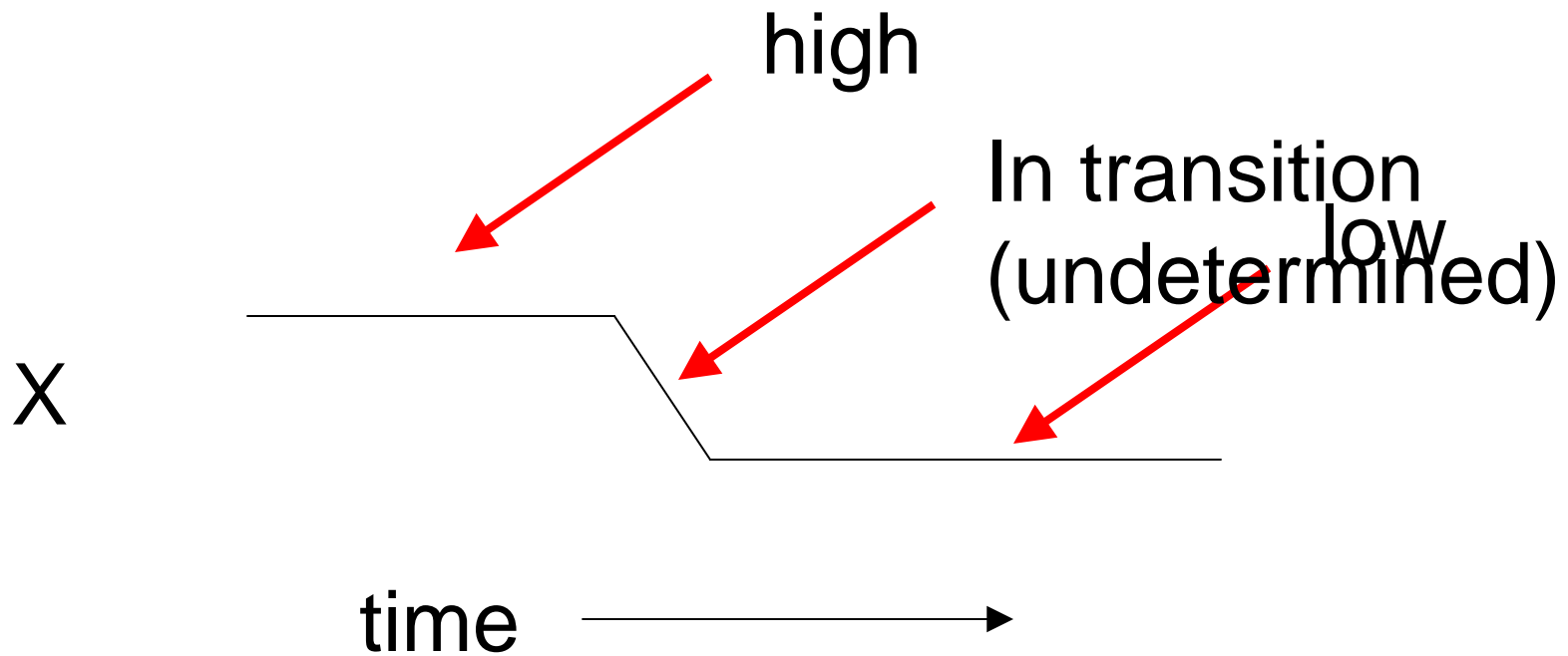


# Timing Notation

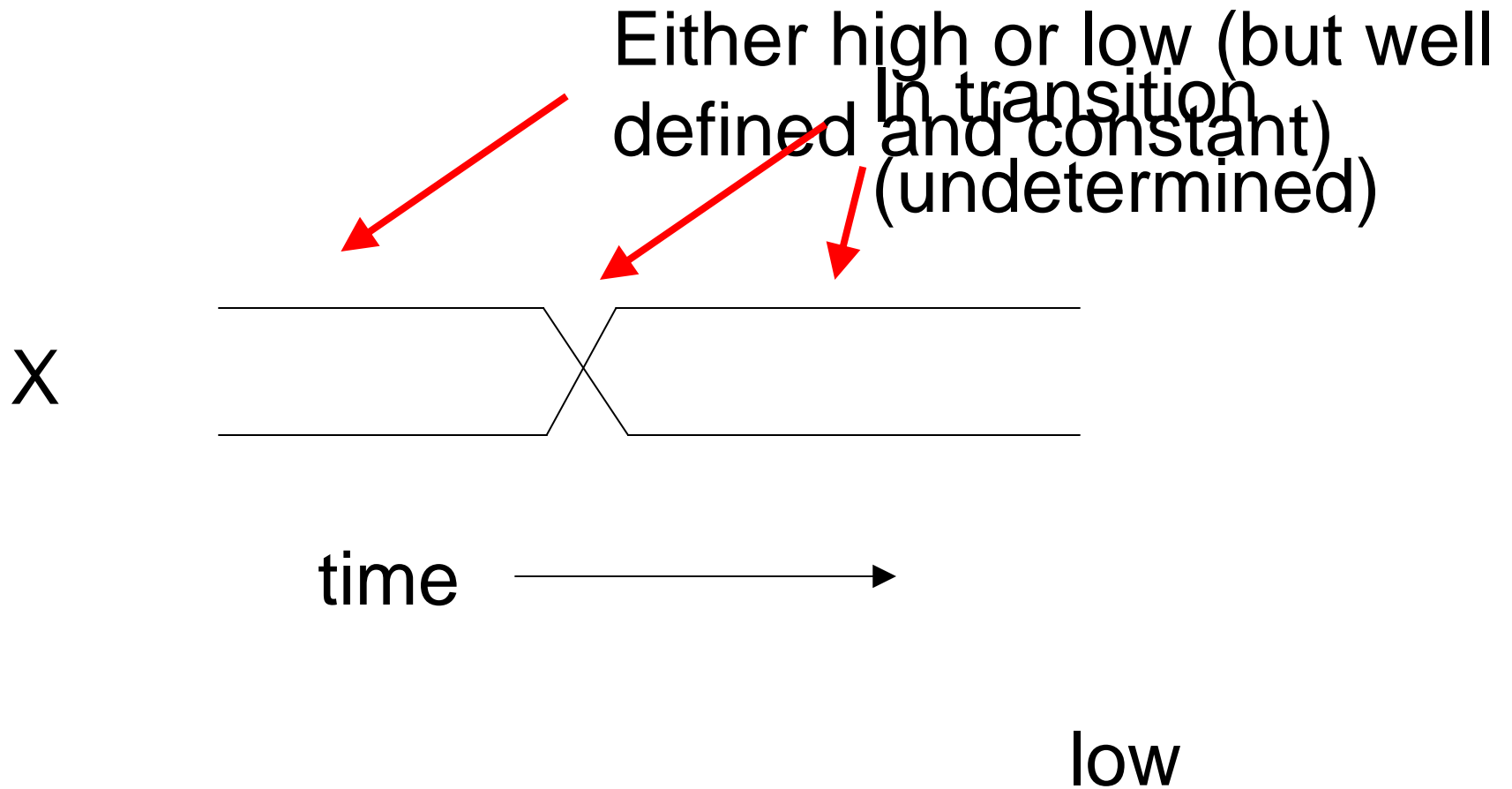

# D Flip Flops

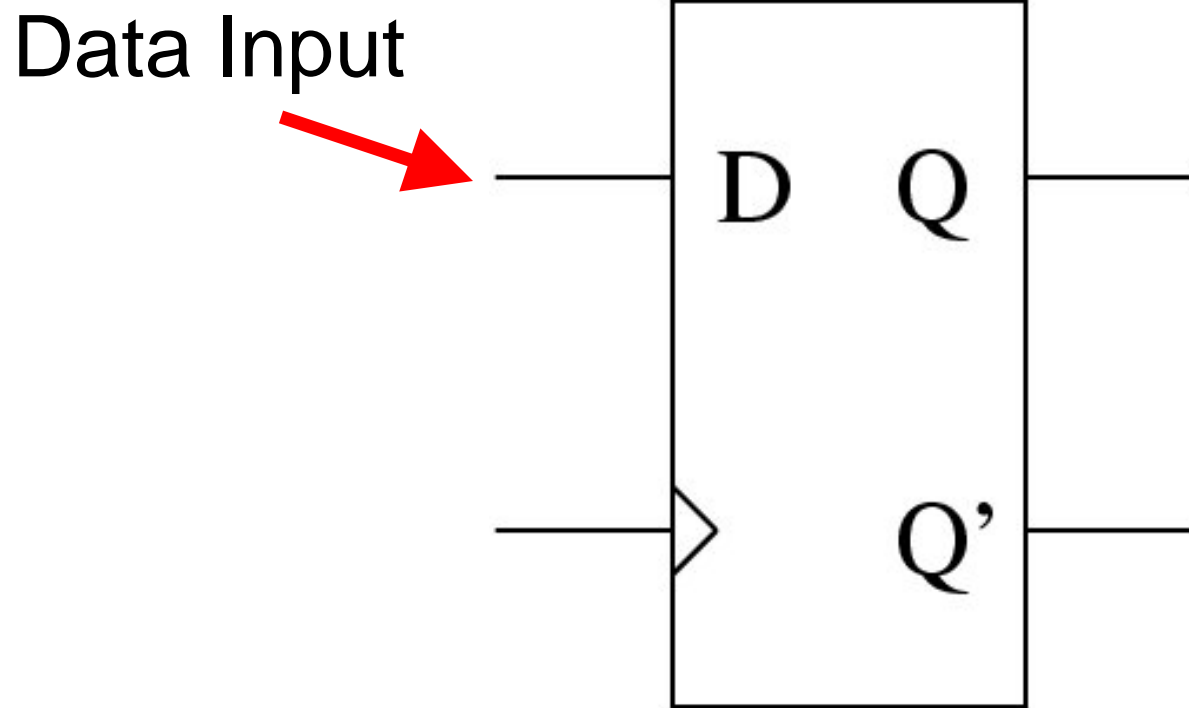


# D Flip Flops

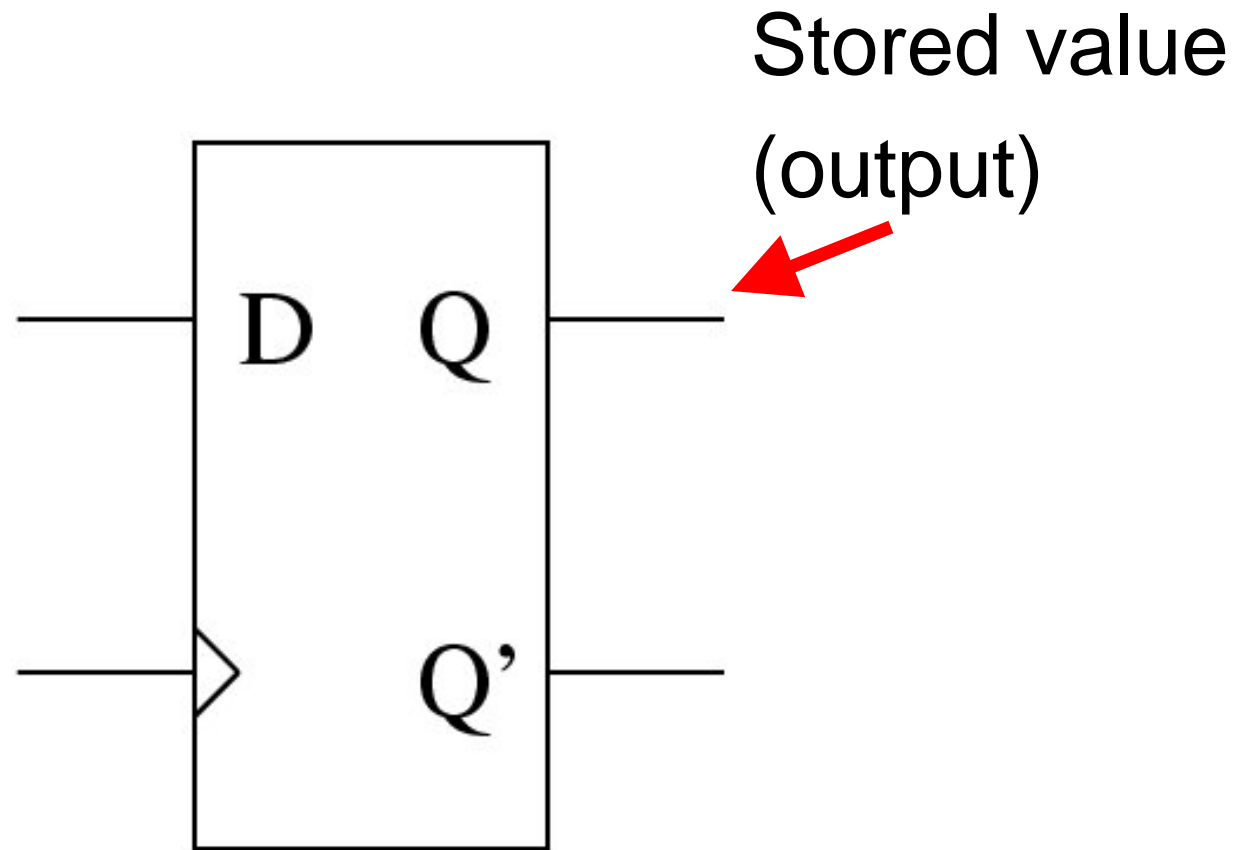





# D Flip Flops

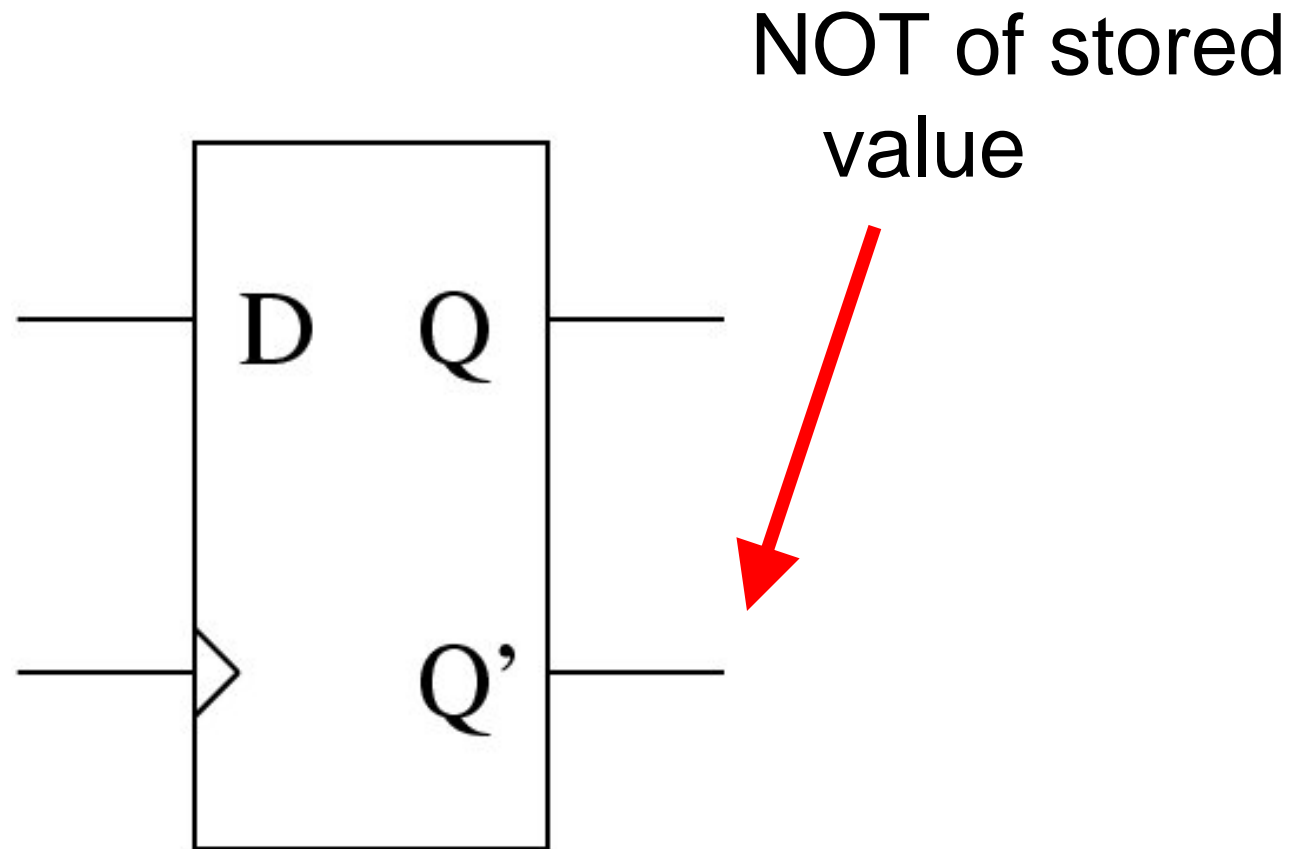

# D Flip Flops

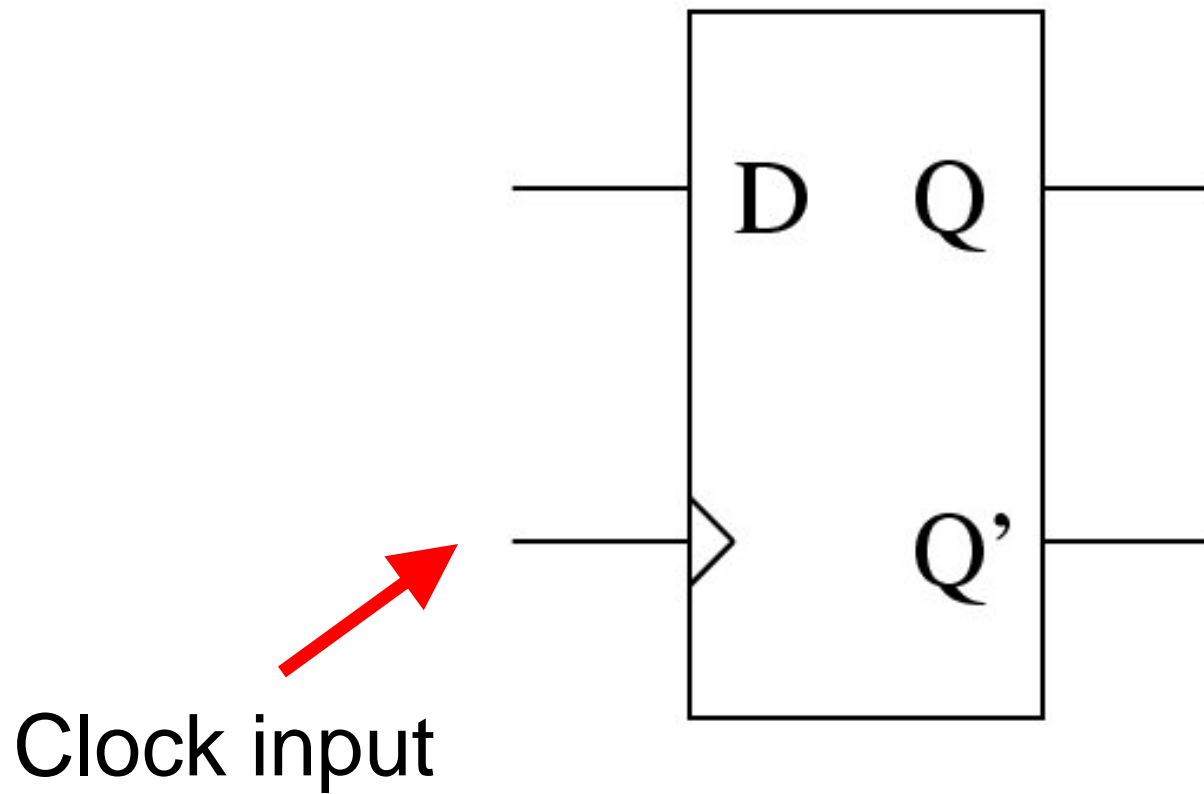


# D Flip Flops

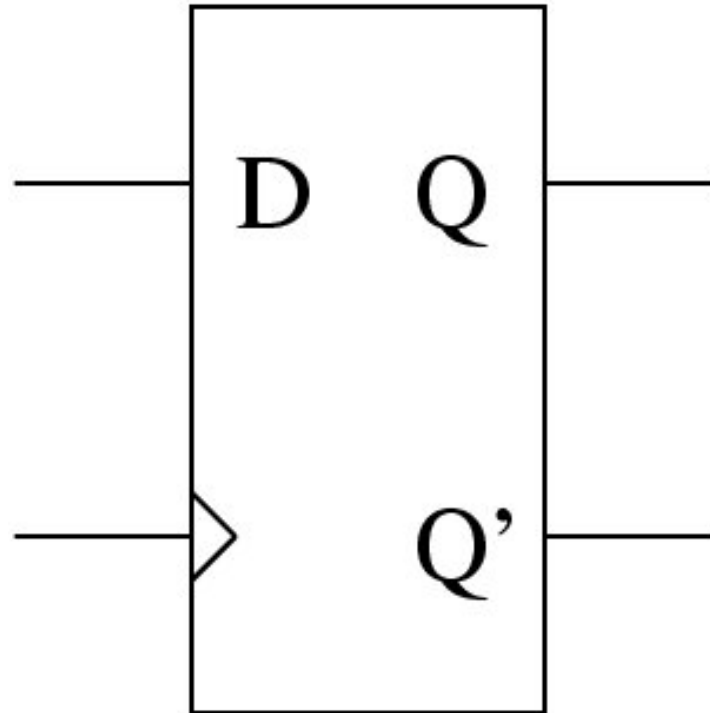


When the clock transitions from high to low:  
the value of D is stored

# D Flip Flop

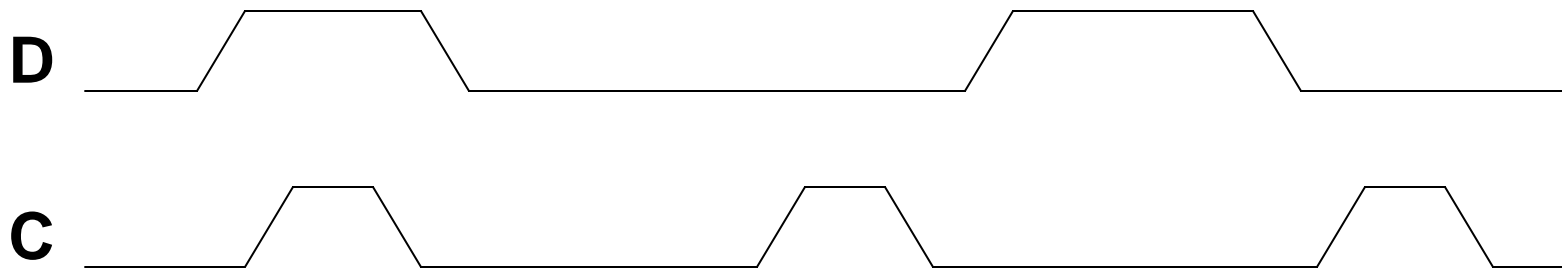


**Q** ——— What happens to  
**Q'** ——— Q and Q'?

# D Flip Flop

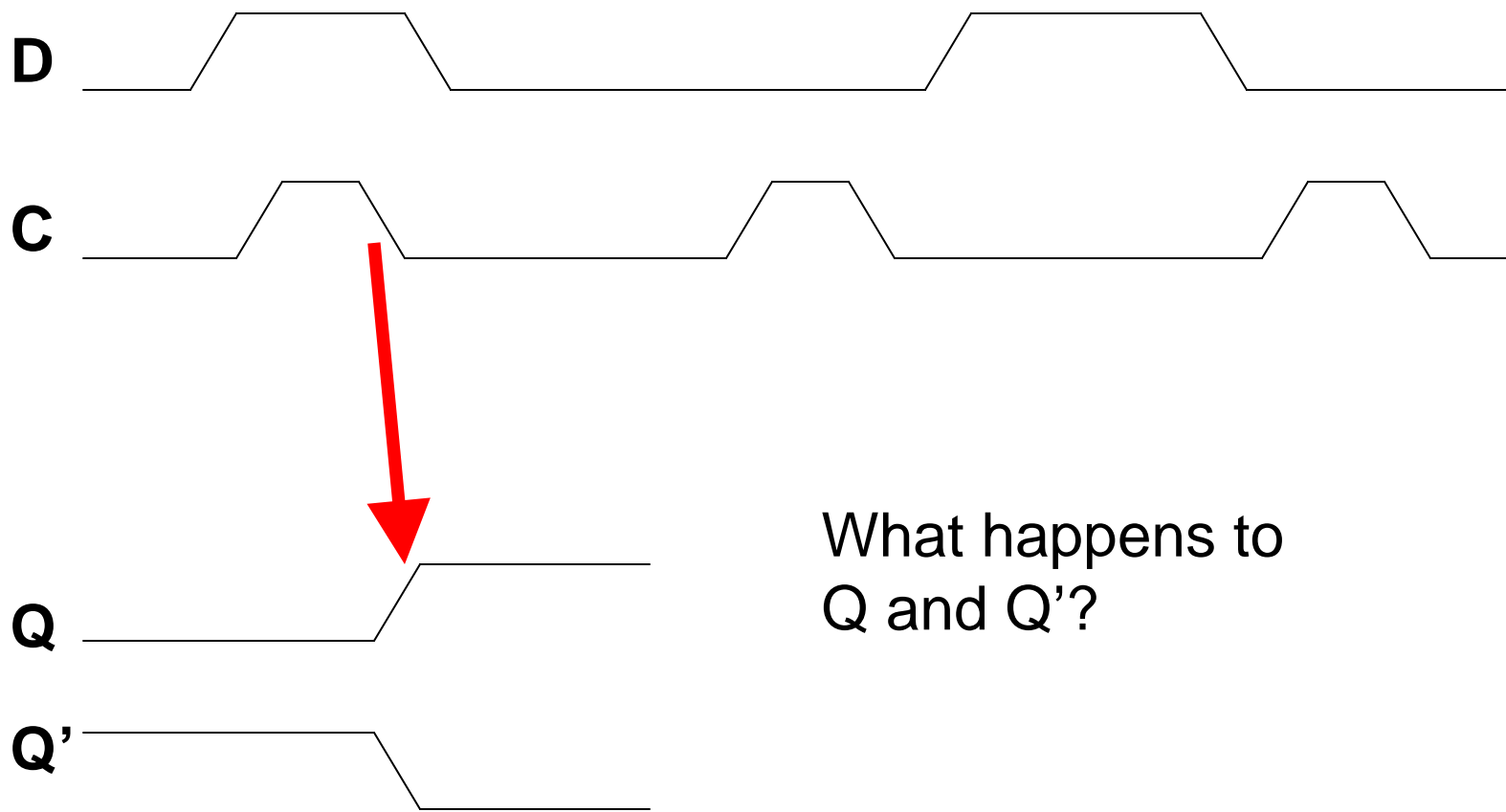


What happens to Q and Q'?

# D Flip Flop

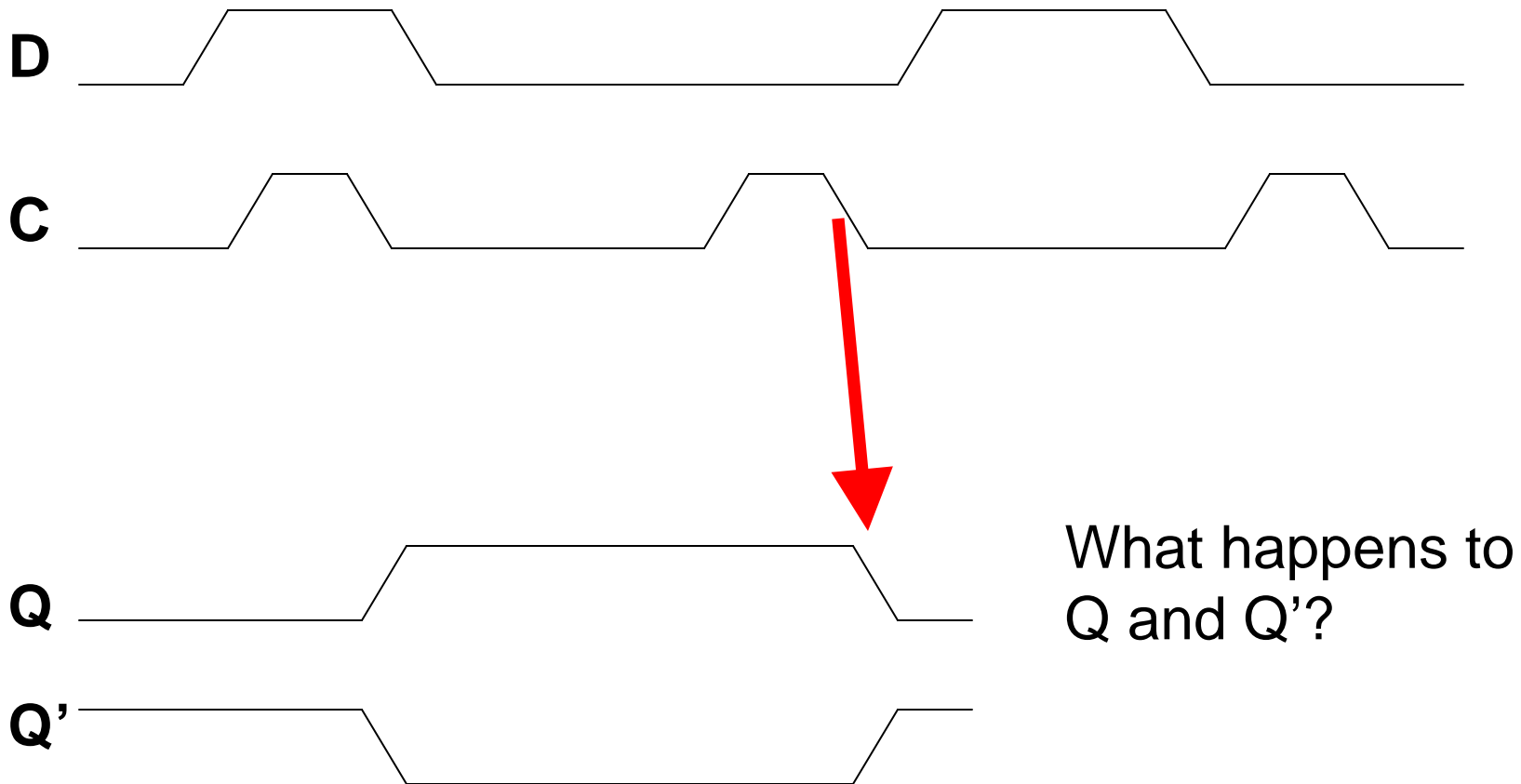


What happens to Q and Q'?

# D Flip Flop

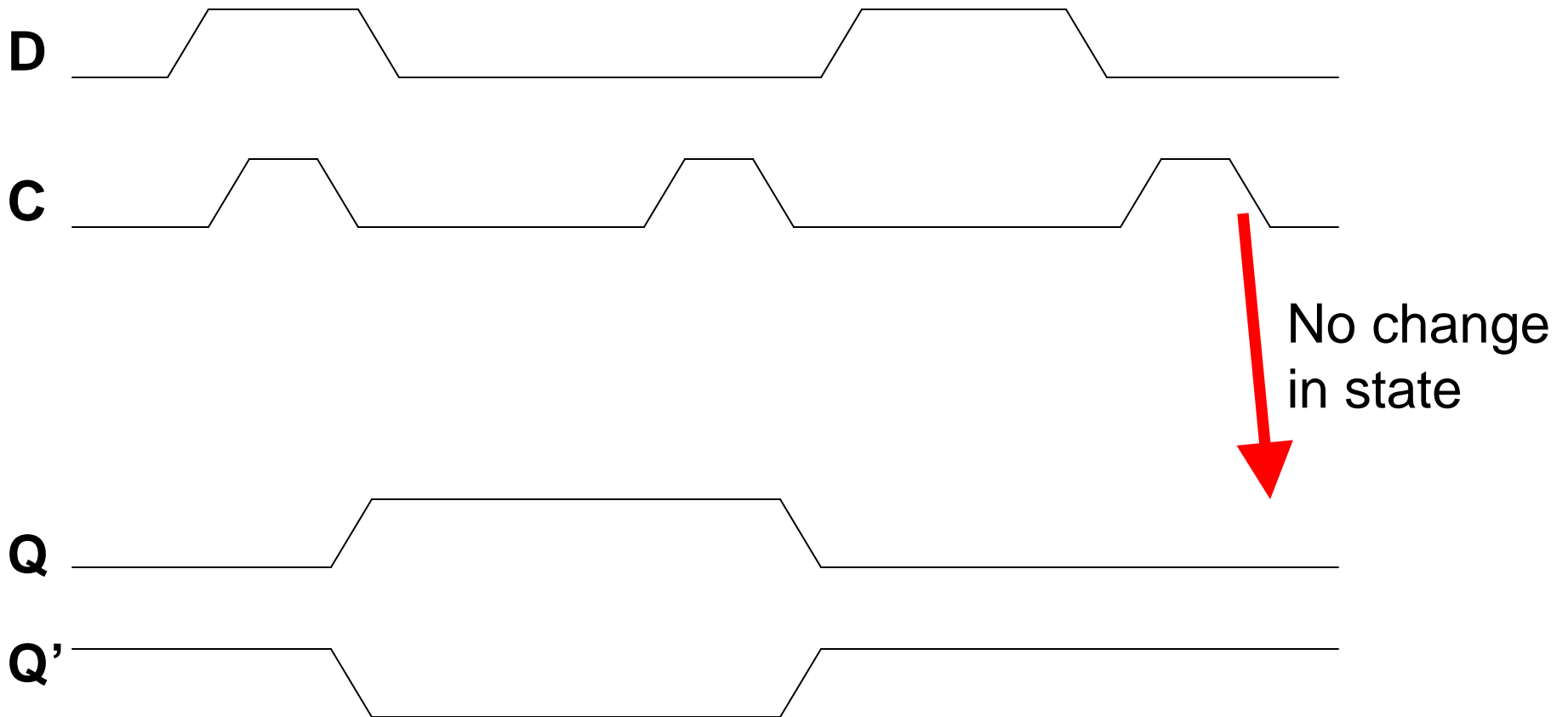

# An Application of D Flip Flops

What does this circuit do?

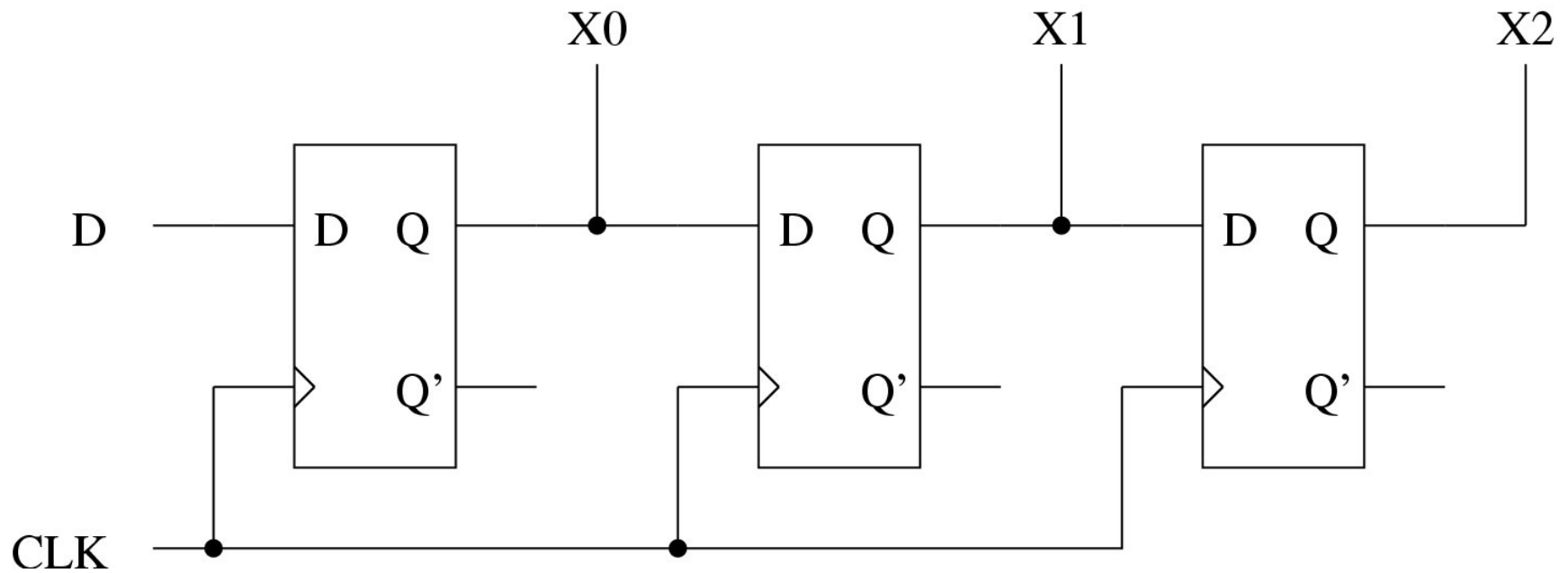



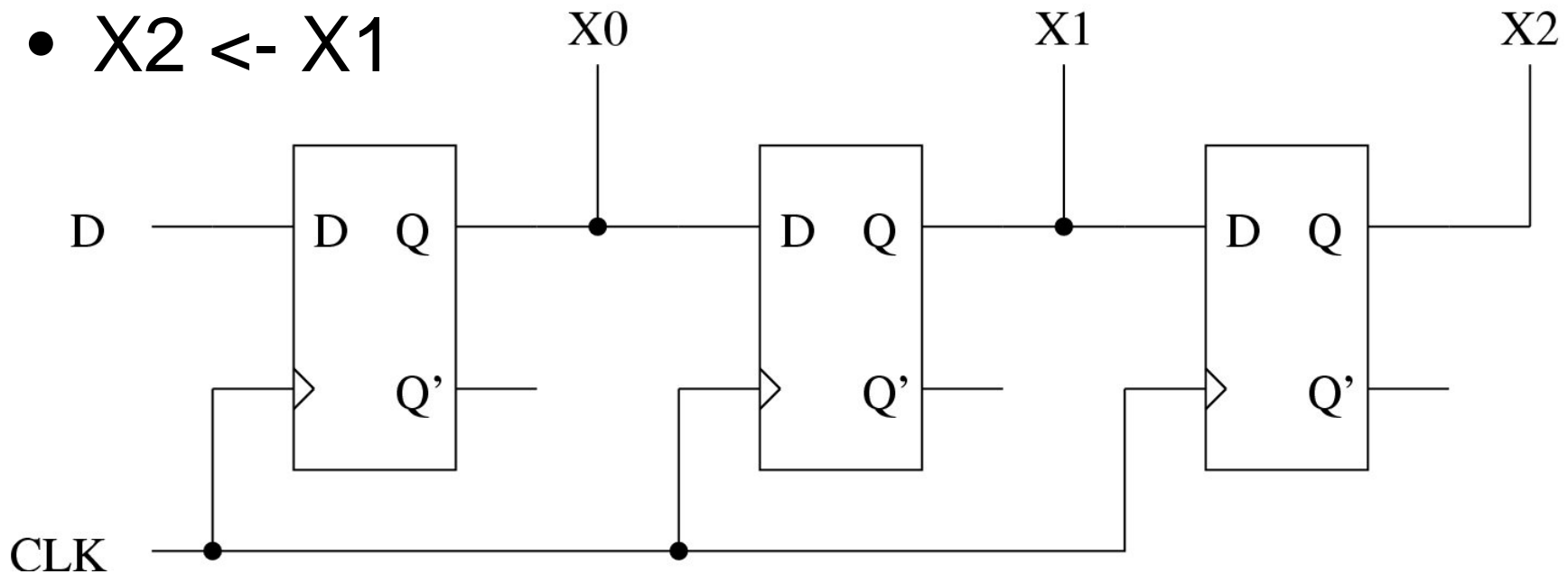
# Shift Register


On each clock transition from high to low:

- $X0$  takes on the current value of  $D$
- $X1 \leftarrow X0$
- $X2 \leftarrow X1$




# Another D Flip Flop Circuit

How does this circuit behave?

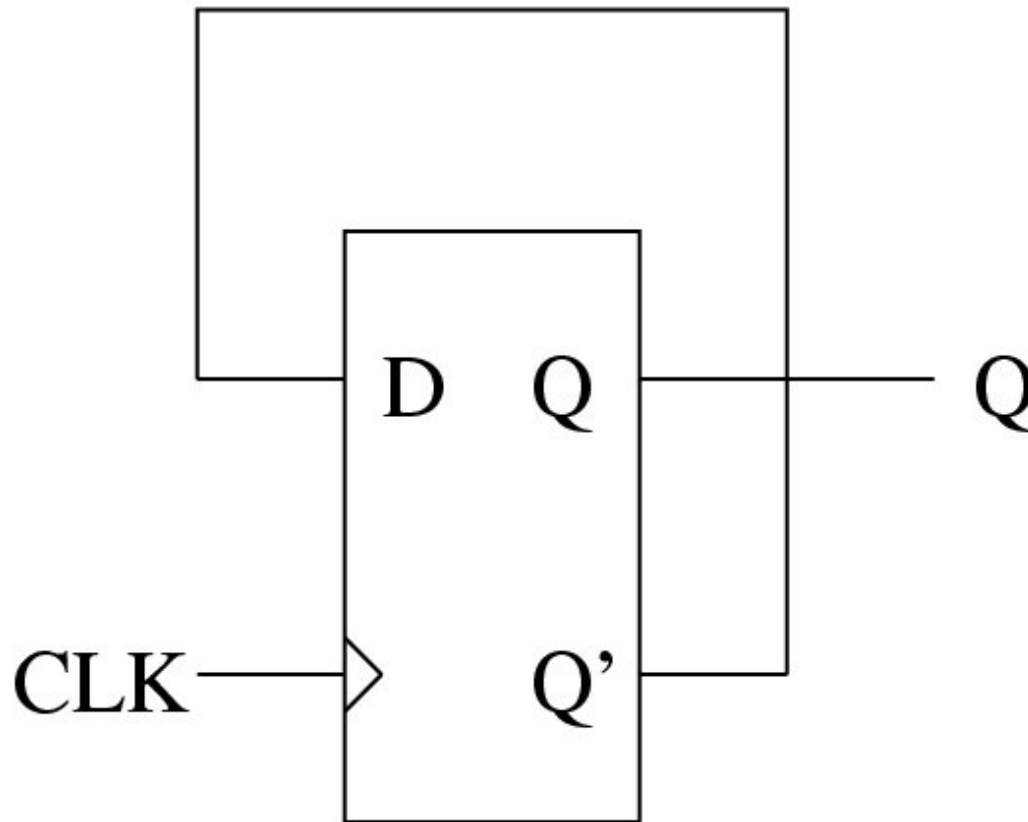


# Another D Flip Flop Circuit

How does this circuit behave?

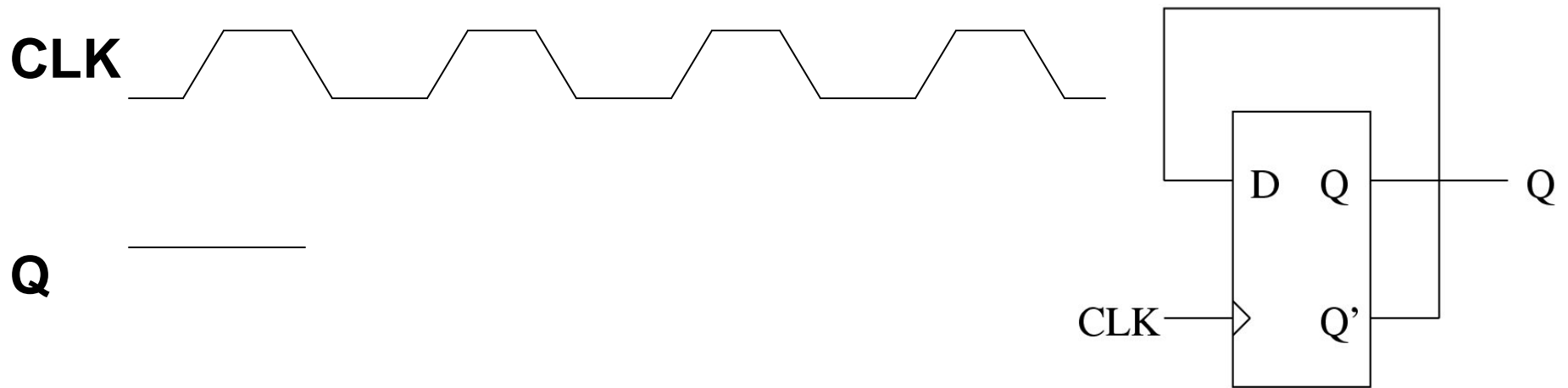
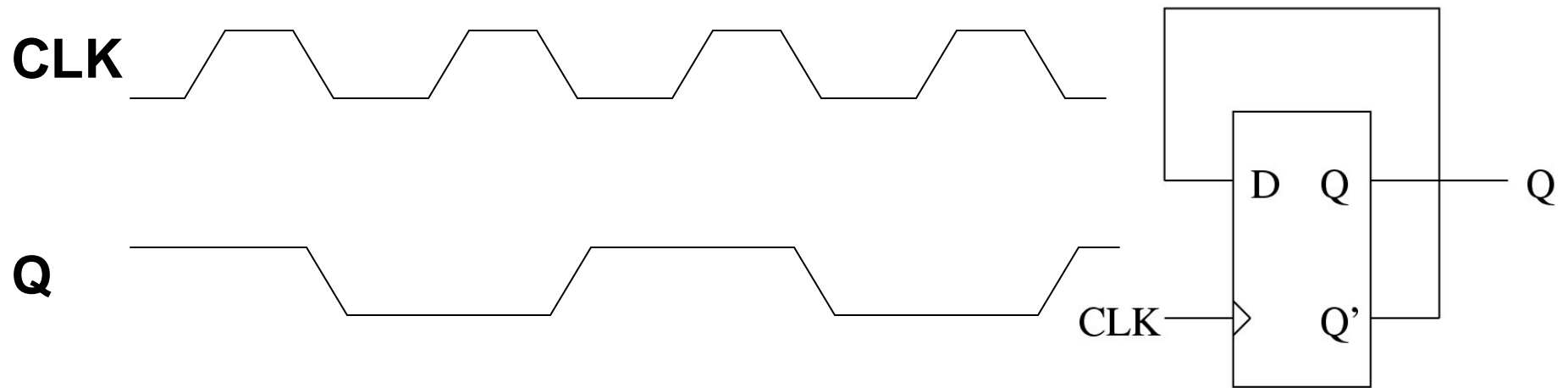
# Frequency Divider


Q flips state on every downward edge of the clock


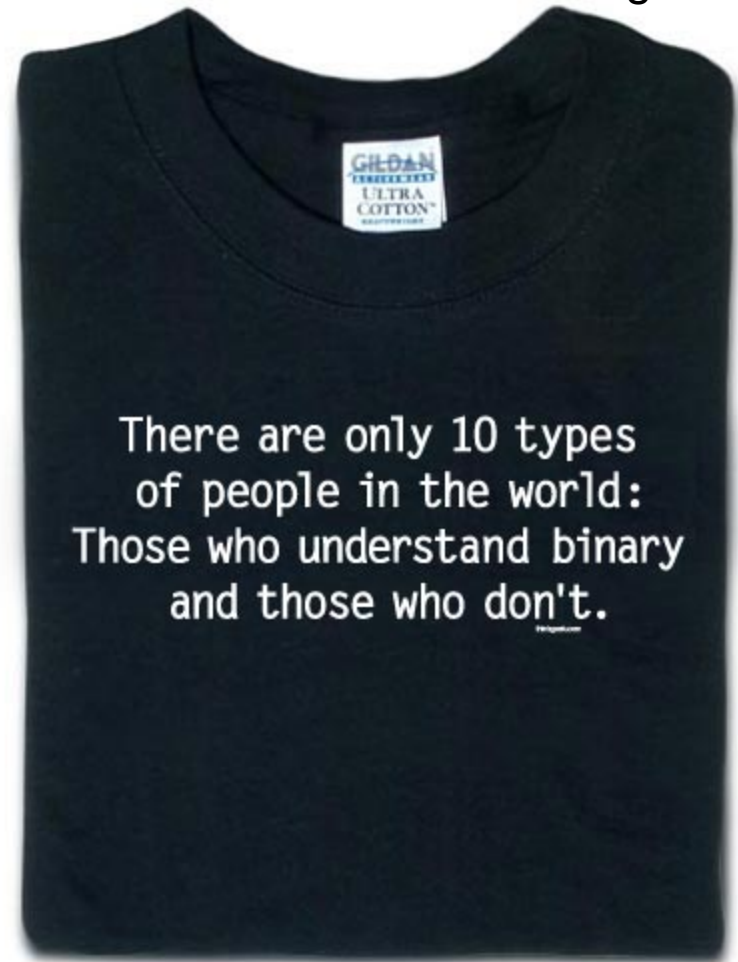
# A Bit About Binary Encoding

[www.thinkgeek.com](http://www.thinkgeek.com)

If a boolean variable can only encode two different values, how do we represent a larger number of values?



# Binary Encoding

How do we represent a larger number of values?

# Binary Encoding

How do we represent a larger number of values?

- As with our decimal number system: we concatenate binary digits (or “bits”) into strings

# Binary Encoding


- The first (rightmost) bit is the 1's digit
- The second bit is the 2's digit
- The  $i$ th bit is the  $2^{i-1}$  's digit



# Last Time
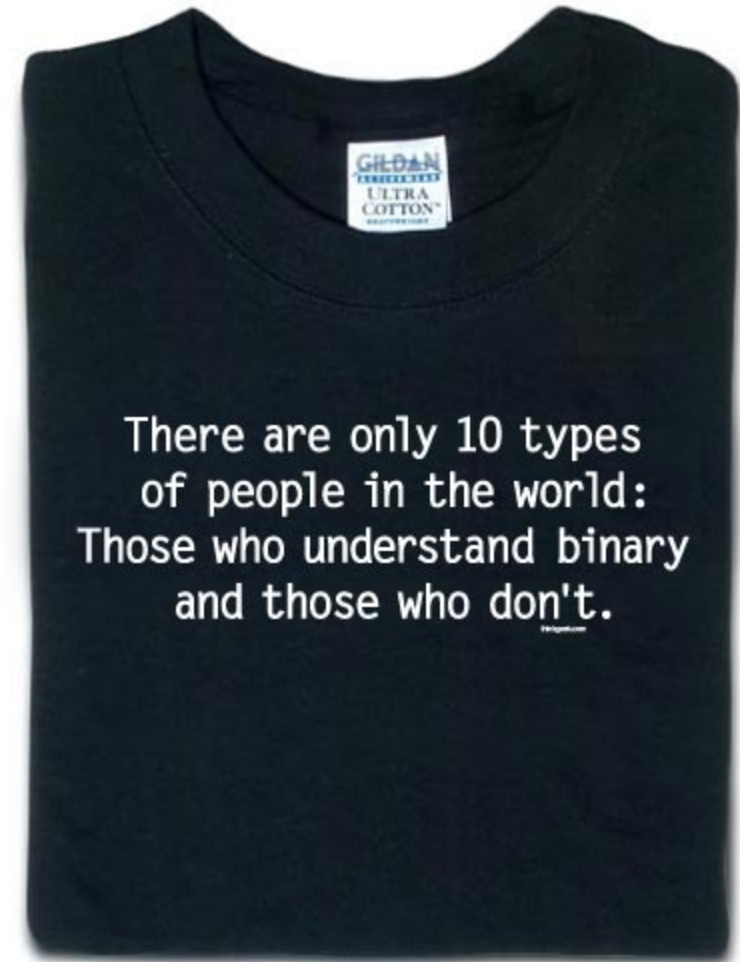
## Sequential Logic

- D Flip Flops
- Shift registers
- Binary number system



# Today

- A little more on number systems
- Use of flip-flops
- Microprocessor basics
  - Memory
  - Arithmetic Logical Units
  - Instructions and execution

# Administrivia

- Homework 1 due today at 5:00
- Homework 2 available tonight

# Binary Encoding

How do we  
convert from  
binary to  
decimal in  
general?

B2	B1	B0		decimal
0	0	0		0
0	0	1		1
0	1	0		2
0	1	1		3
1	0	0		4
1	0	1		5
1	1	0		6
1	1	1		7

# Binary to Decimal Conversion

$$value = B_0 + B_1 * 2^1 + B_2 * 2^2 + B_3 * 2^3 + \dots$$

$$value = \sum_{i=0}^{N-1} B_i * 2^i$$

How do we convert from decimal to binary?

# Decimal to Binary Conversion

$\forall i : B_i \leftarrow 0$

*while*(*value*  $\neq$  0)

{

*Find i such that*  $2^{i+1} > \text{value} \geq 2^i$

$B_i \leftarrow 1$

*value*  $\leftarrow$  *value*  $- 2^i$

}

# Binary Counter

How would we build a circuit that counts the number of clock ticks that have gone by?

B2	B1	B0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

# Binary Counter

How would we build a circuit that counts the number of clock ticks that have gone by?

Insight:


- B1 changes state at half the frequency that B0 does
- B2 changes state at half the frequency of B1

B2	B1	B0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



# Ripple Counter

The carry “ripples” down the chain ...

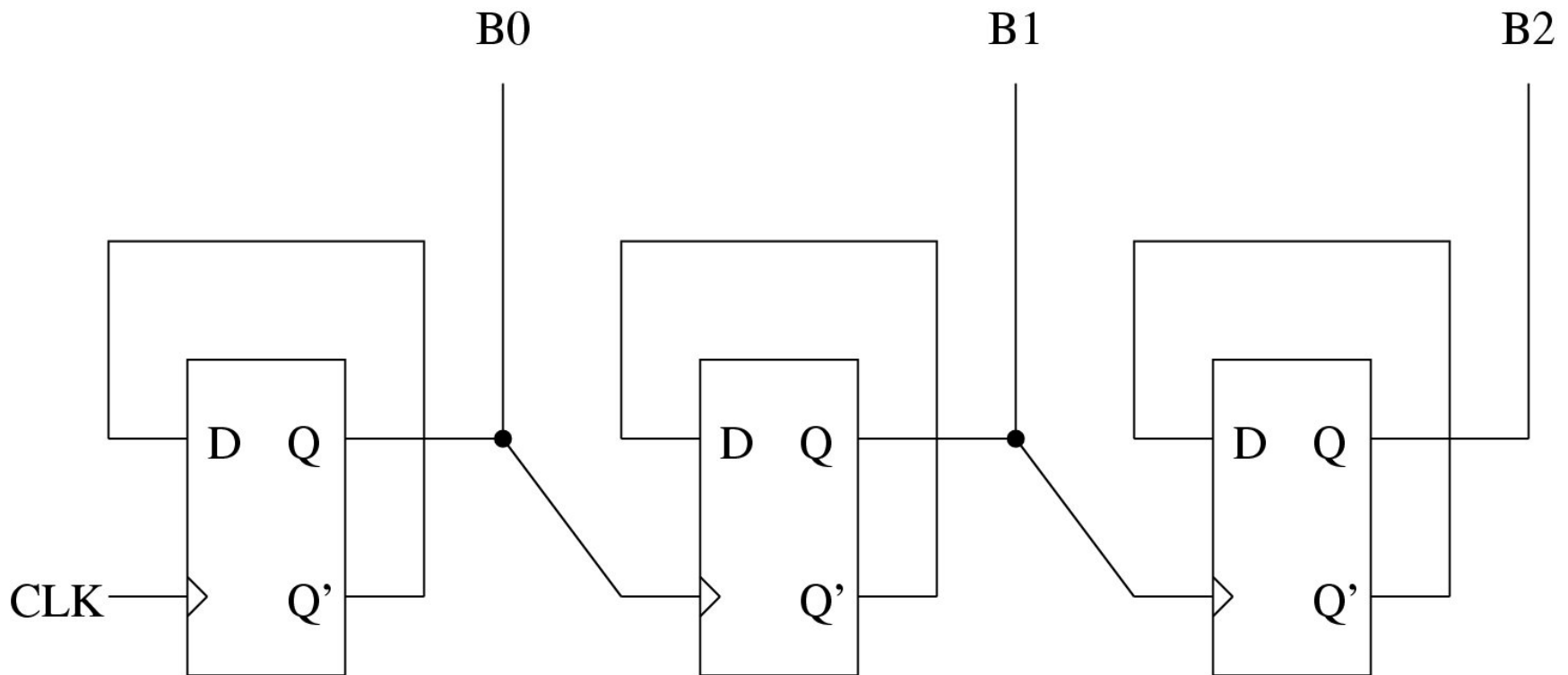

# Ripple Counter Notes

- The bits do not change state at the same time
- This can be repaired with a more sophisticated circuit design
  - We will experiment with this in hw2

# Flip-Flop Notes

- Means of storing ‘bits’ of data
- Have now seen two circuits that operate on sets of ‘bits’ (or binary numbers)
  - Counter
  - Shift register
    - What arithmetic operation does shifting perform?
- These are examples of operations that are performed by the “Arithmetic Logical Unit”