

# Embedded Real-Time Systems (AME 3623)

## Homework 1

February 13, 2010

This homework assignment is due on Tuesday, February 9th at 5:00pm. Your work may be handed in electronically (use the **Homework 1** digital dropbox on D2L) or in hardcopy form (in person or in office).

This assignment must be done individually: do not share/discuss your answers with others or look at the answers of others.

### Question 1


1. (5pts) Given the binary number: 110100101. What is the decimal equivalent? Show your work.
2. (5pts) Given the binary number: 011011111. What is the decimal equivalent? Show your work.

3. (5pts) Given the decimal number: 45. What is the binary equivalent?  
Show your work (all of the steps of the algorithm that we discussed in class).

4. (5pts) Given the decimal number: 567. What is the binary equivalent?  
Show your work.
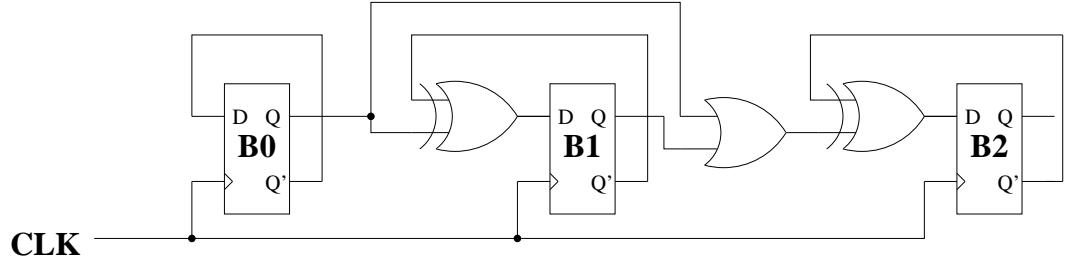
## Question 2


Consider the following circuit with input  $CLK$ :



1. (10pts) Assume that the initial state is:  $Q_0 = 0, Q_1 = 0, Q_2 = 1$ . Show the timing diagram for  $Q_0, Q_1$  and  $Q_2$  as the clock ( $CLK$ ) is pulsed (show 6 transitions).
2. (10pts) Interpreting  $Q_2, Q_1, Q_0$  as a 3-bit binary number (with  $Q_0$  as the 1's digit), what is the sequence of values that this circuit produces?
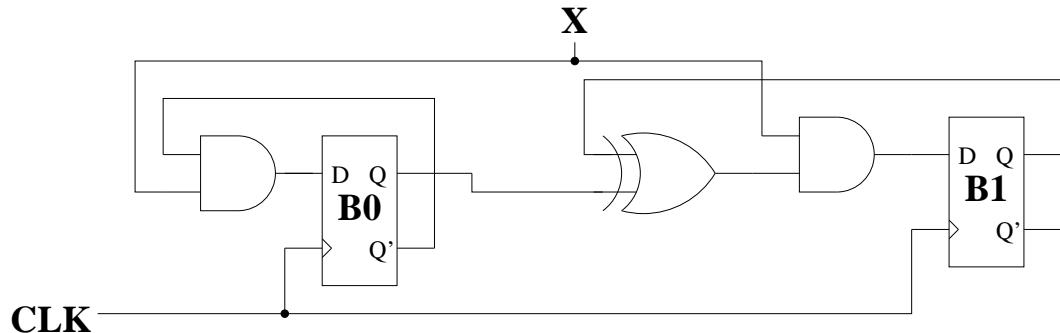
## Question 3

Consider the following circuit with inputs  $CLK$  and  $X$ :



1. (10pts) Assume that the initial state is:  $Q0 = 1$  and  $Q1 = 0$ . Assume also that  $X = 1$ . Show the timing diagram for  $Q0$  and  $Q1$  as the clock ( $CLK$ ) is pulsed (for 6 transitions).
2. (10pts) Interpreting  $Q1$ ,  $Q0$  as a 2-bit binary number (with  $Q0$  as the 1's digit), what is the sequence of values that this circuit produces?

3. (10pts) What is the mathematical function of this circuit when  $X = 1$ ?
4. (10pts) Assume the same initial state as above, and assume that  $X = 0$ . Show the timing diagram for  $Q0$  and  $Q1$  as the clock ( $CLK$ ) is pulsed (for 6 transitions).
5. (10pts) What is the sequence of values that this circuit produces?

6. (10pts) What is the function of this circuit when  $X = 0$ ?

## Question 4

How much time did you spend on this homework assignment?