

# Binary Encoding

How do we  
convert from  
binary to  
decimal in  
general?

B2	B1	B0		decimal
0	0	0		0
0	0	1		1
0	1	0		2
0	1	1		3
1	0	0		4
1	0	1		5
1	1	0		6
1	1	1		7

# Binary to Decimal Conversion

$$value = B_0 + B_1 * 2^1 + B_2 * 2^2 + B_3 * 2^3 + \dots$$

$$value = \sum_{i=0}^{N-1} B_i * 2^i$$

How do we convert from decimal to binary?

# Decimal to Binary Conversion

```
int value;
```

```
For each i: B[i] = 0
```

```
while(value > 0) {  
    if(remainder of value / 2 is 1) {  
        B[i] = 1;  
    }  
    value = value / 2;  
}
```

# Time

Until now: we have ignored the issue of time


- We assumed that our digital logic circuits perform their computations instantaneously
- Our digital logic circuits have been “stateless”
  - Once you present a new input, they forget everything about previous inputs
  - We call this type of digital system **combinatorial logic**

# Time


In reality, time is an important issue:

- Even our logic gates induce a small amount of delay (on the order of a few nanoseconds)
- For much of what we do – we actually want our circuits to have some form of memory


# Timing Notation

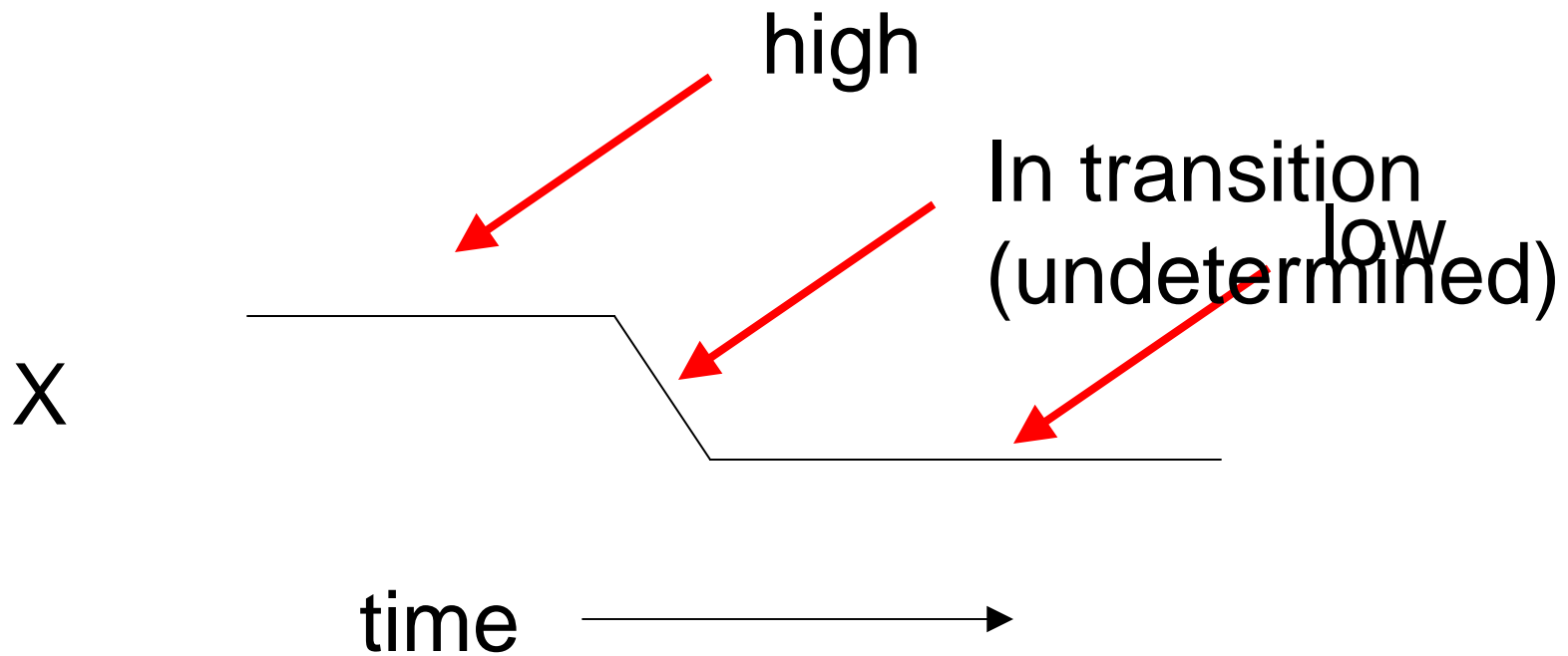

# Timing Notation

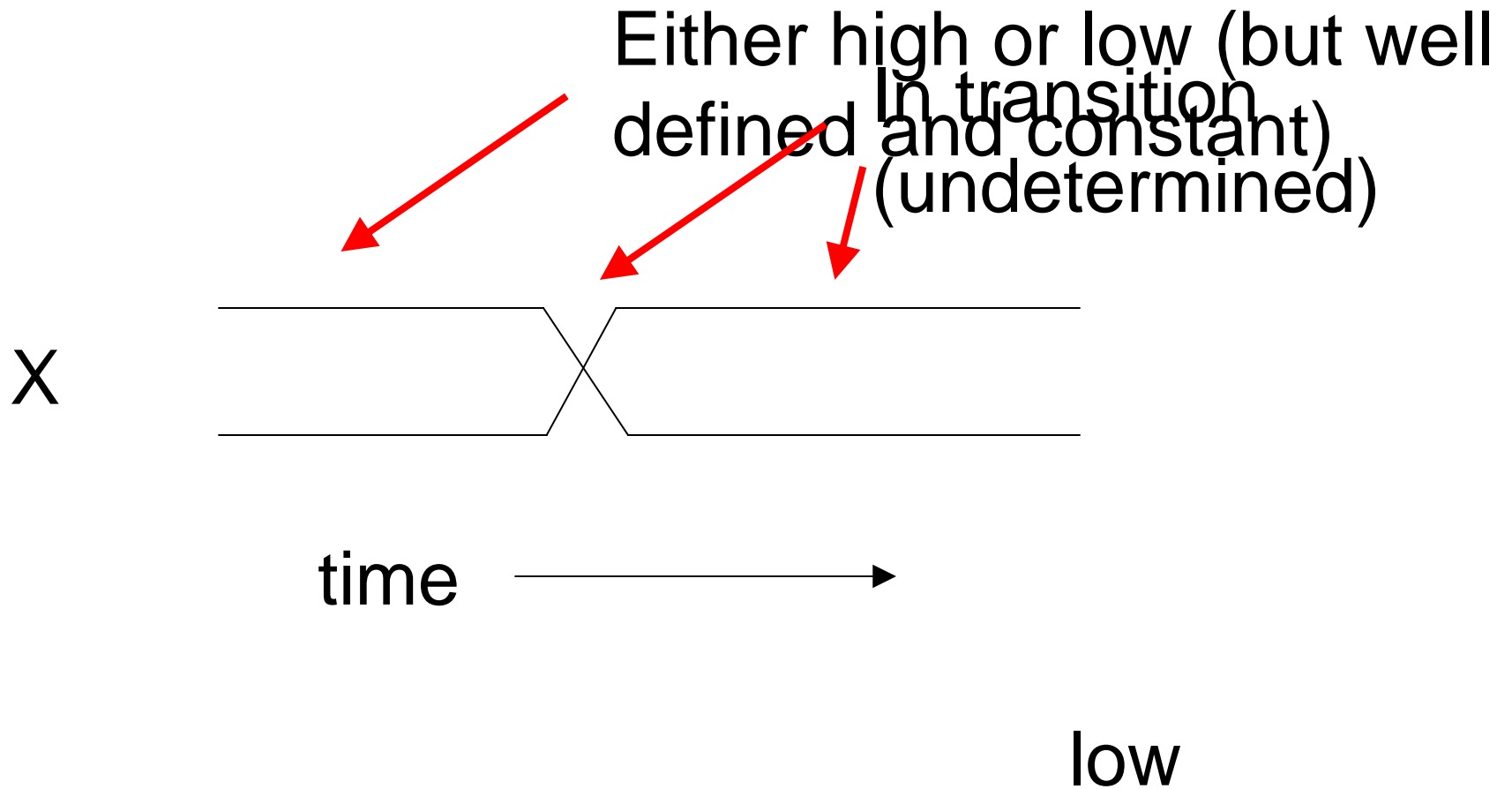


# D Flip Flops

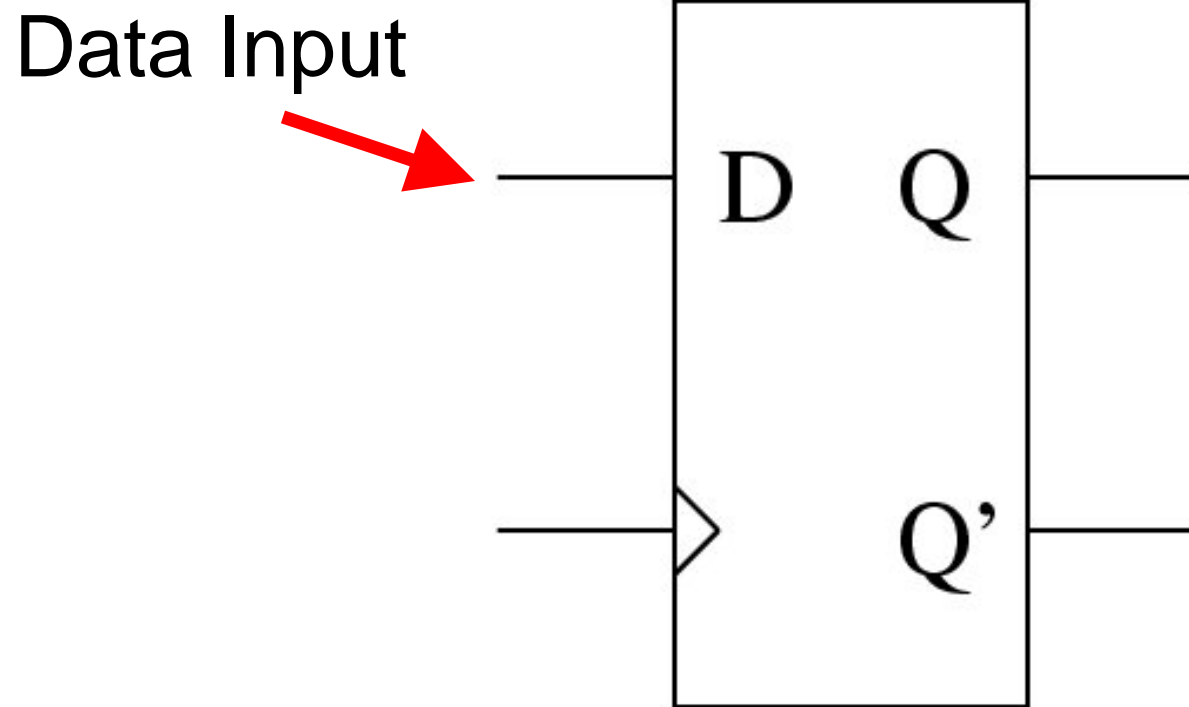





# D Flip Flops

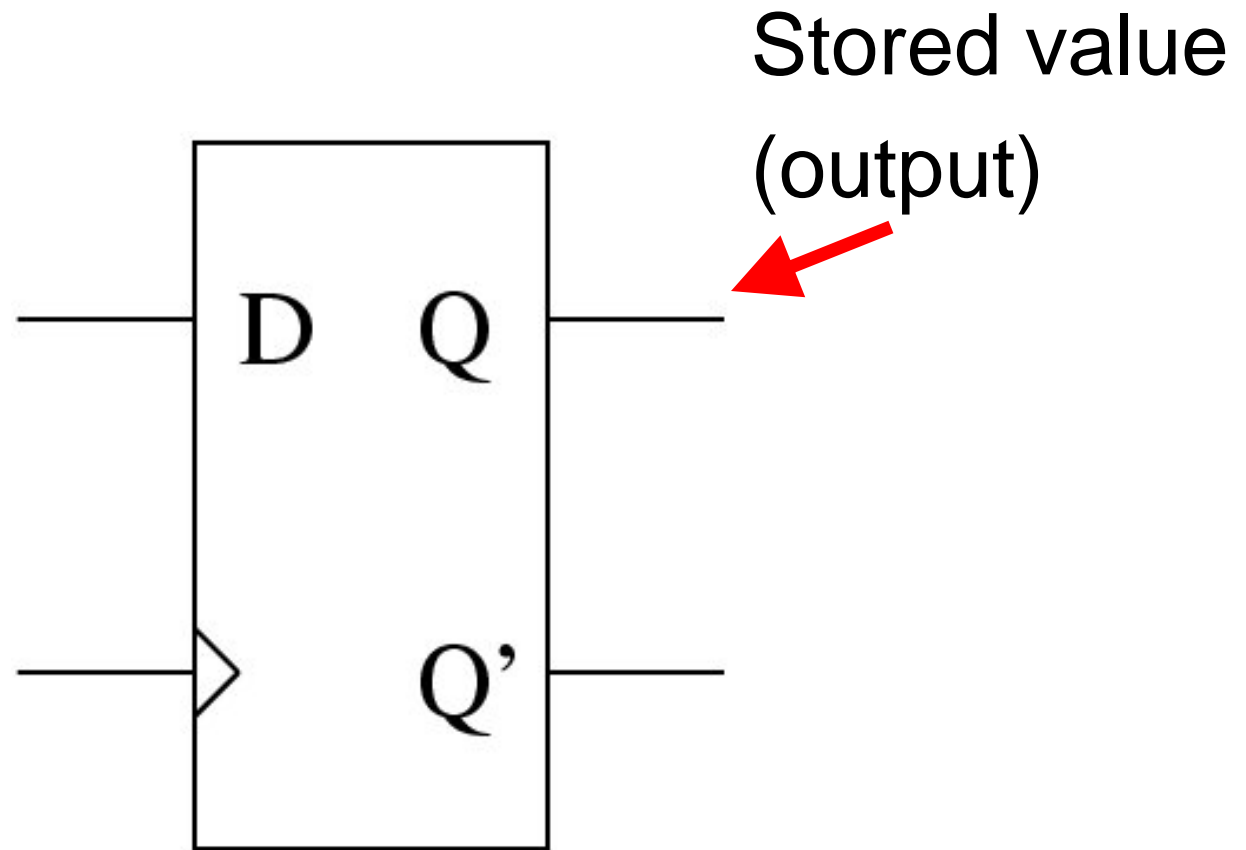


# D Flip Flops

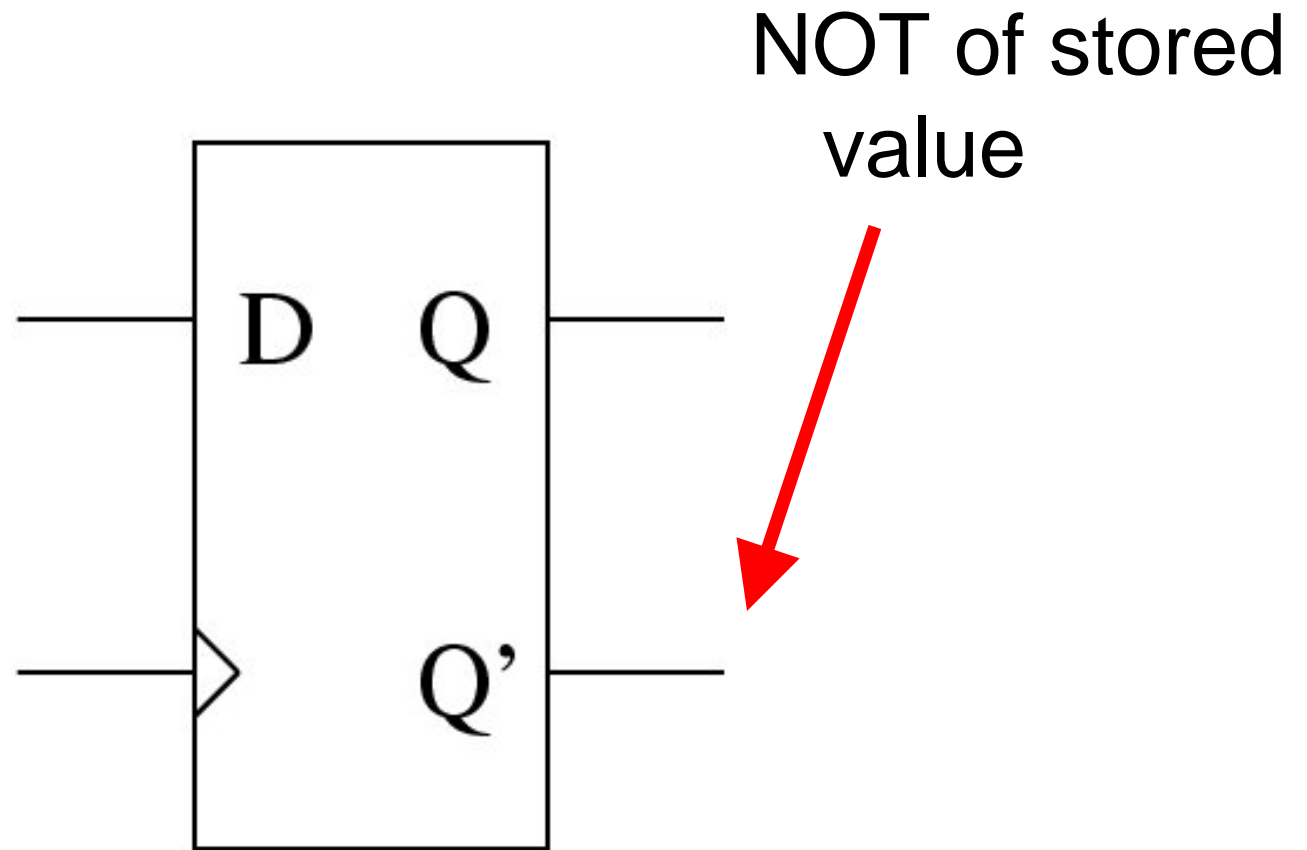

# D Flip Flops

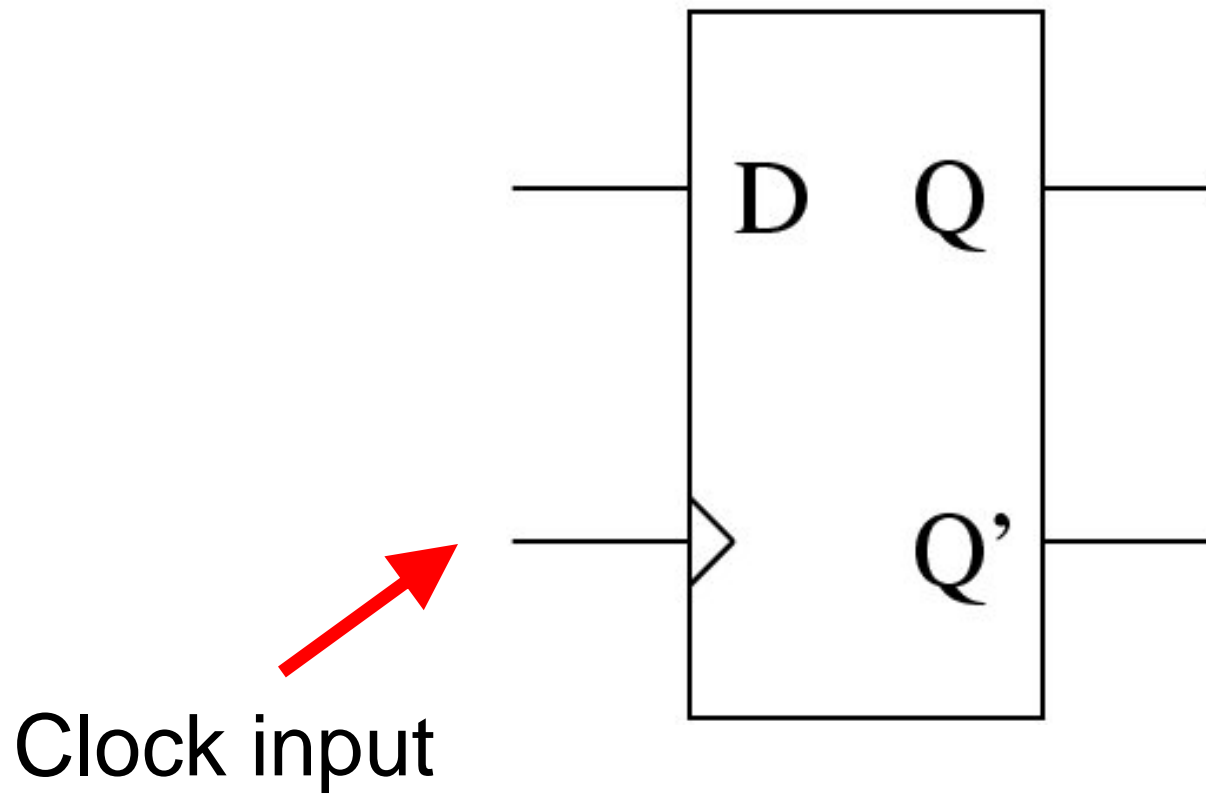


# D Flip Flops

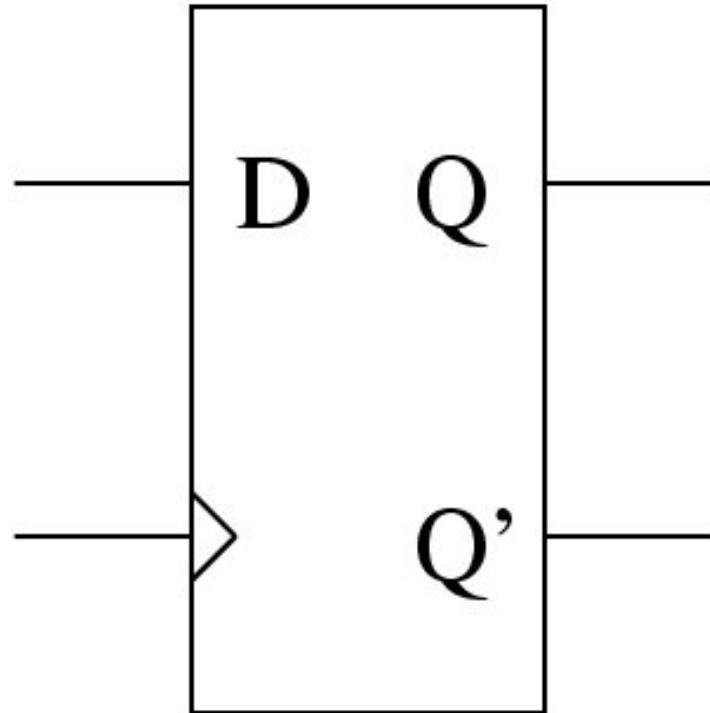


When the clock transitions from high to low:  
the value of D is stored

# D Flip Flop

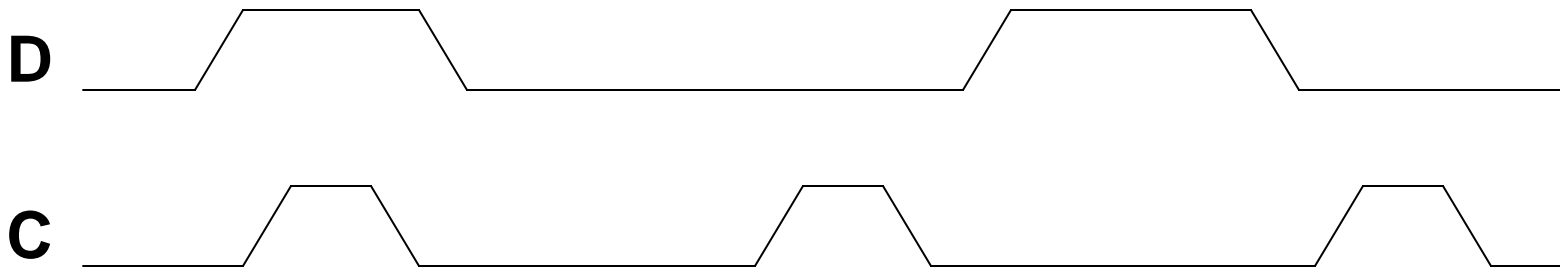


**Q** ——— What happens to  
**Q'** ——— Q and Q'?

# D Flip Flop

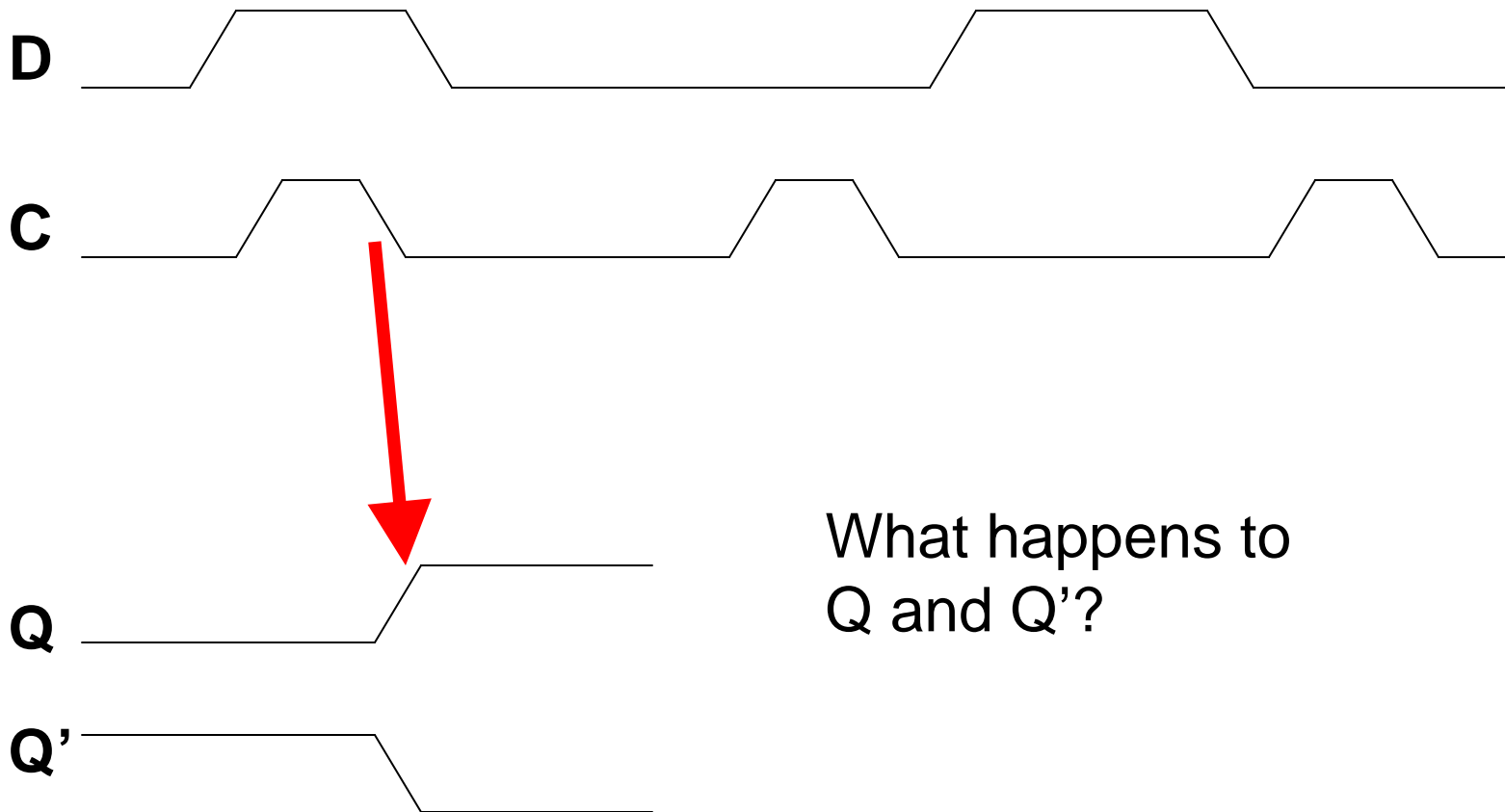


What happens to  
Q and Q'?

# D Flip Flop

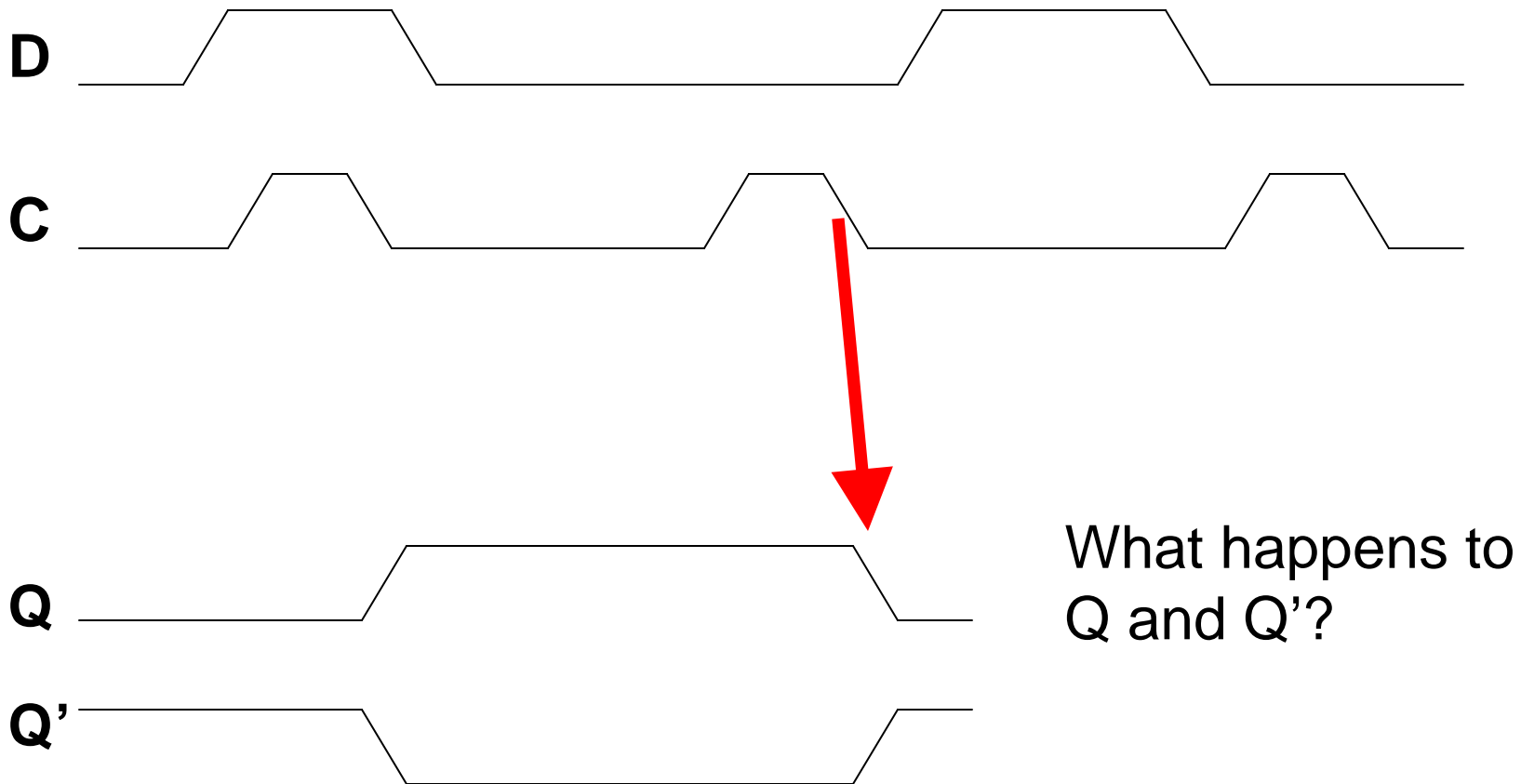

What happens to  
Q and Q'?


# D Flip Flop

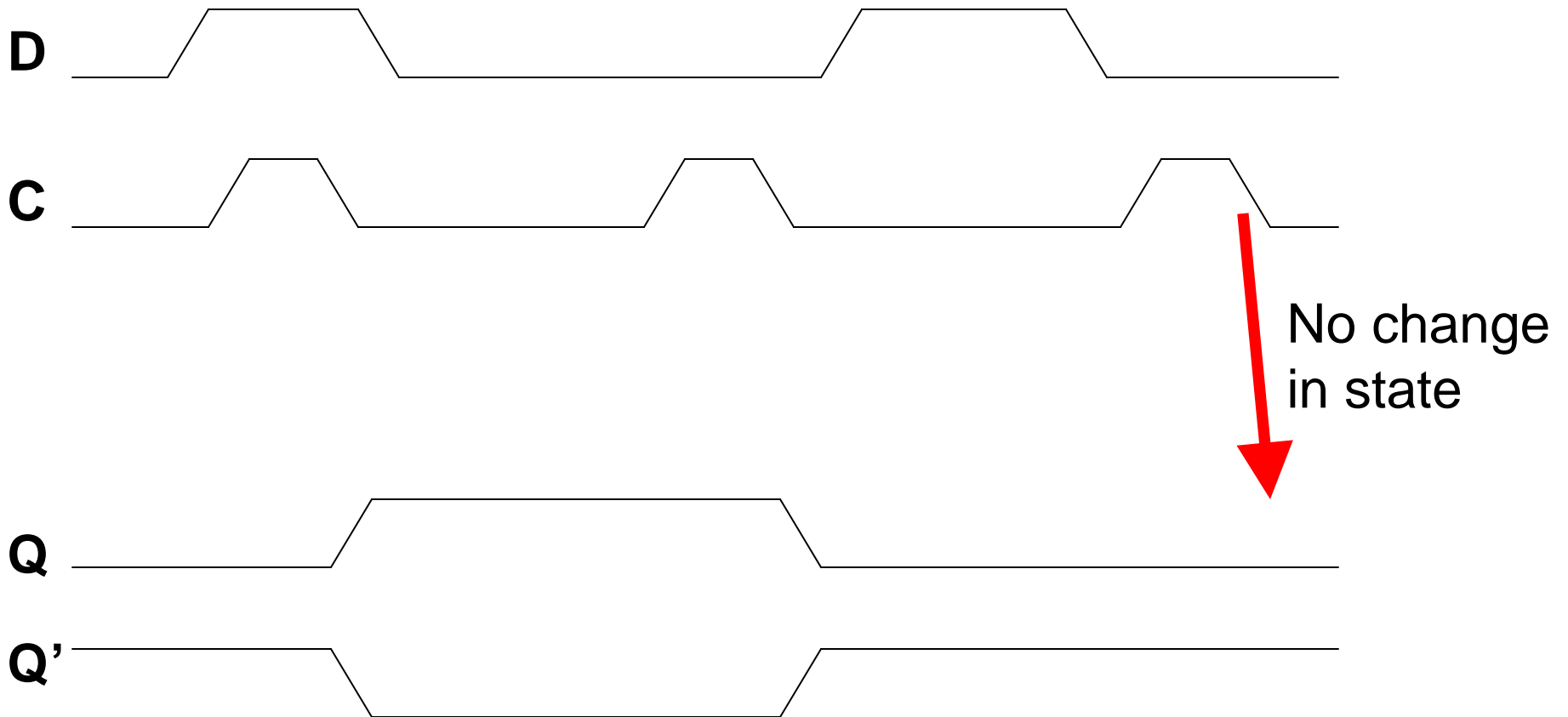



# An Application of D Flip Flops


What does this circuit do?

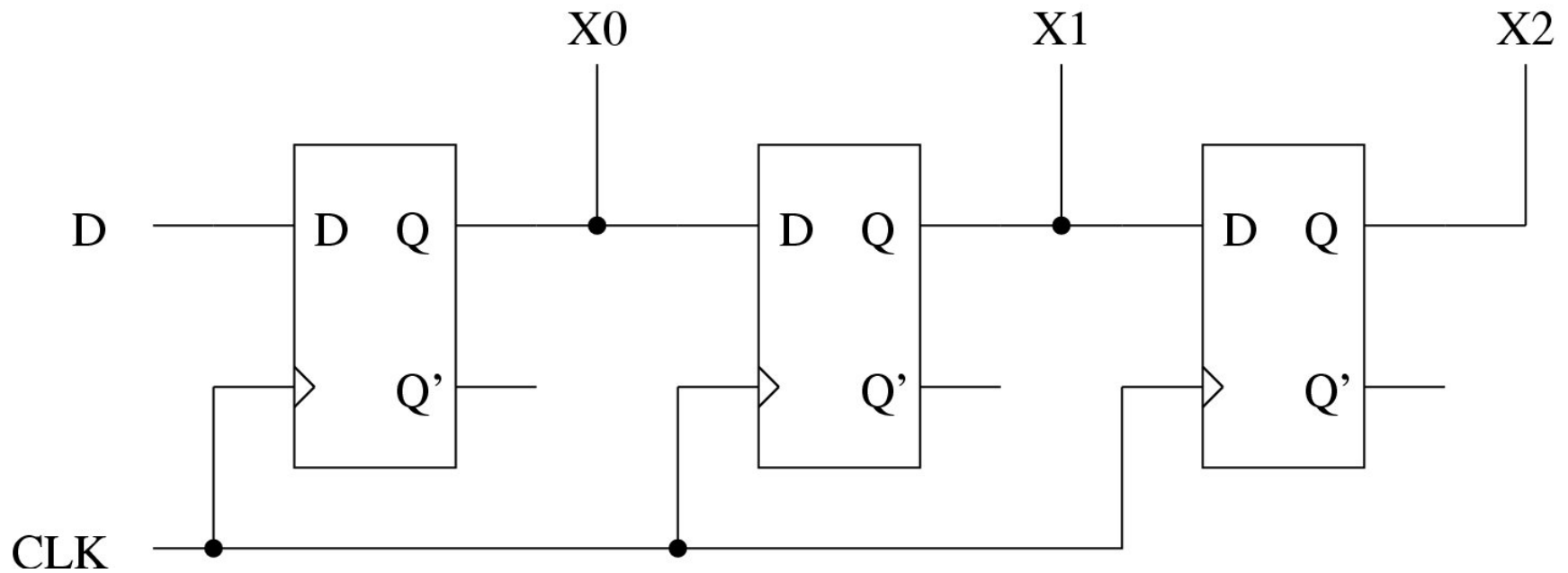
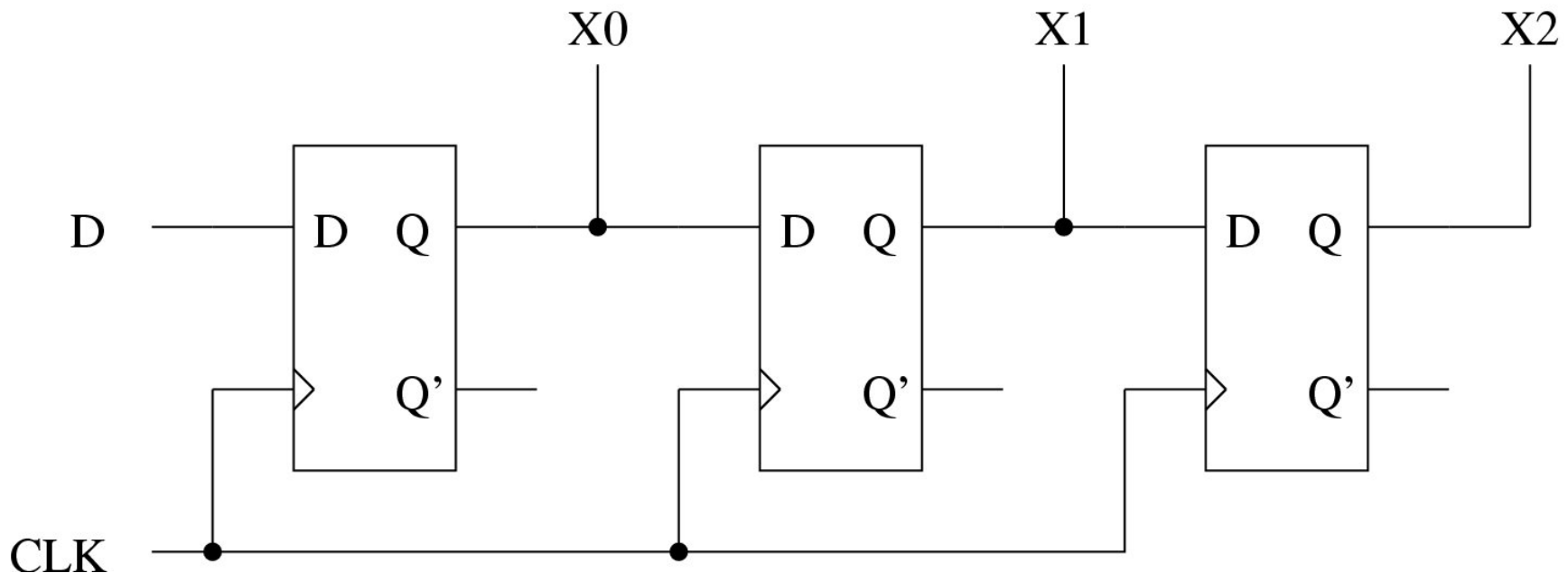
# Shift Register


On each clock transition from high to low:

- X0 takes on the current value of D
- X1 becomes the old value of X0
- X2 becomes the old value of X1




# Another D Flip Flop Circuit

How does this circuit behave?

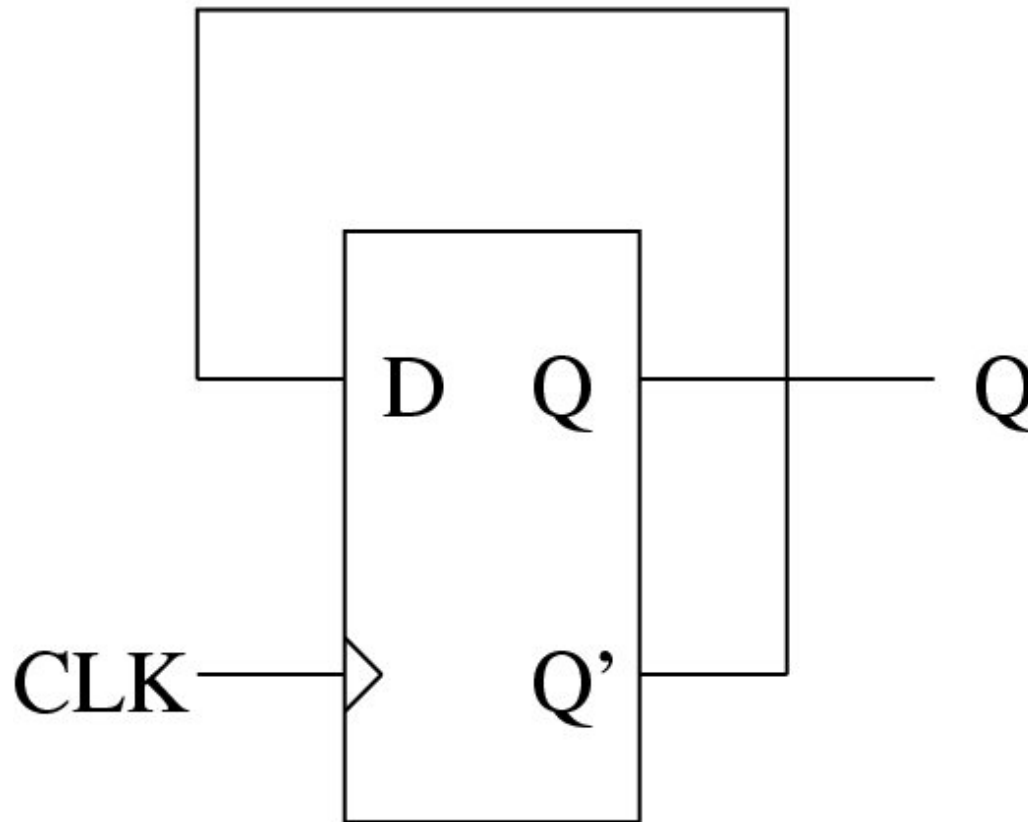


# Another D Flip Flop Circuit

How does this circuit behave?

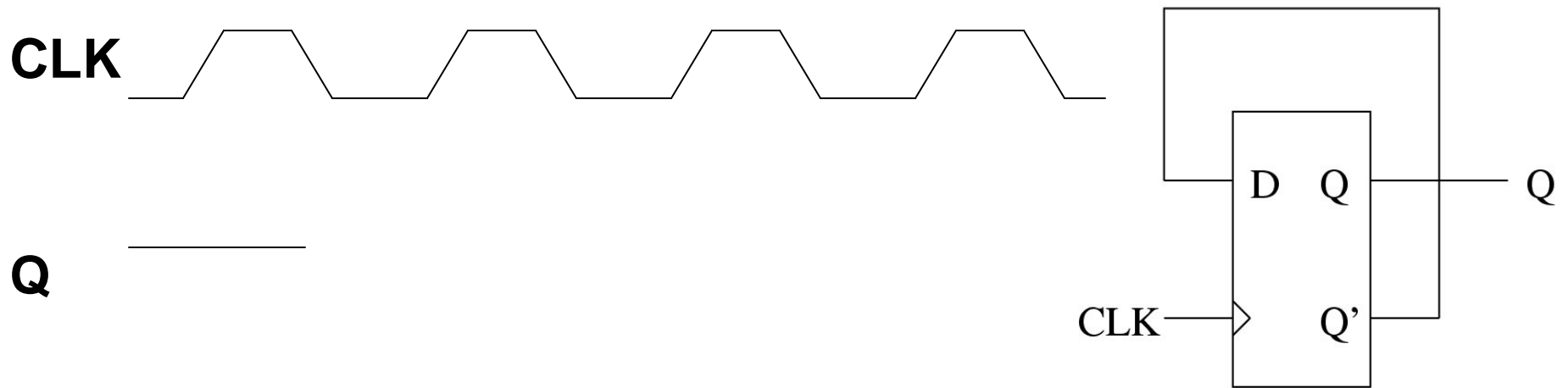
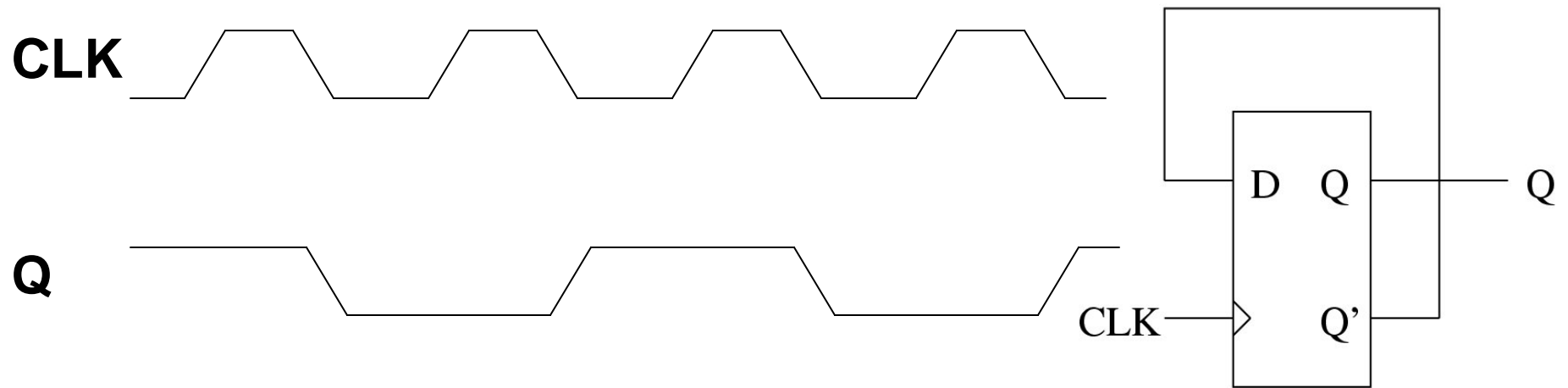
# Frequency Divider

Q flips state on every downward edge of the clock



# Binary Counter

How would we build a circuit that counts the number of clock ticks that have gone by?

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

# Binary Counter

How would we build a circuit that counts the number of clock ticks that have gone by?

Combinatorial circuit design: for a given set of input Q values, output the D's for the next number in the sequence

Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1