

Direct Current (DC) Motors

- Rotating shaft
- Fixed pair of magnets


www.pcgadgets.com



Direct Current (DC) Motors



Wire placed within a magnetic field:

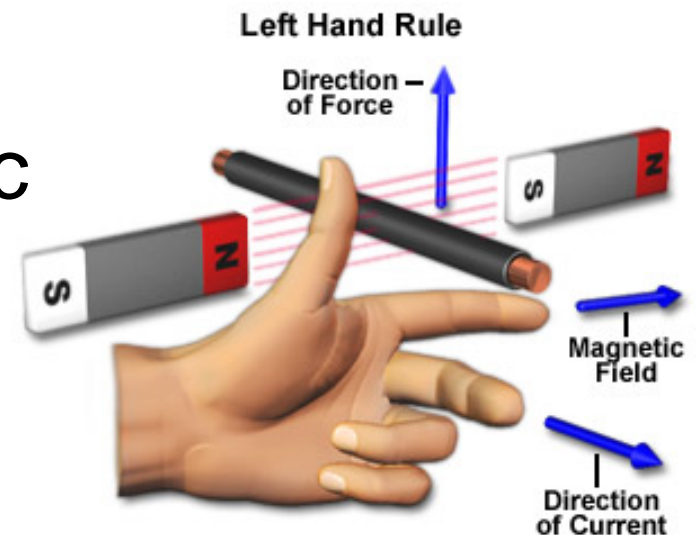- Force on the wire is perpendicular the magnetic field and to the direction of current through the wire
- Direction of force: determined by the left-hand rule




Direct Current (DC) Motors

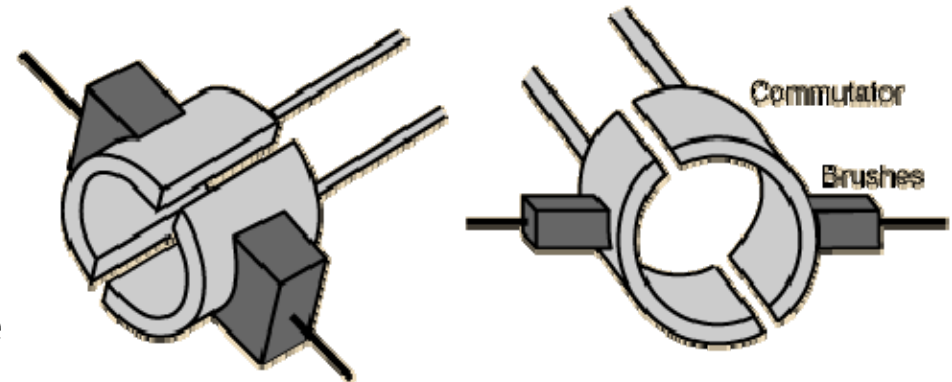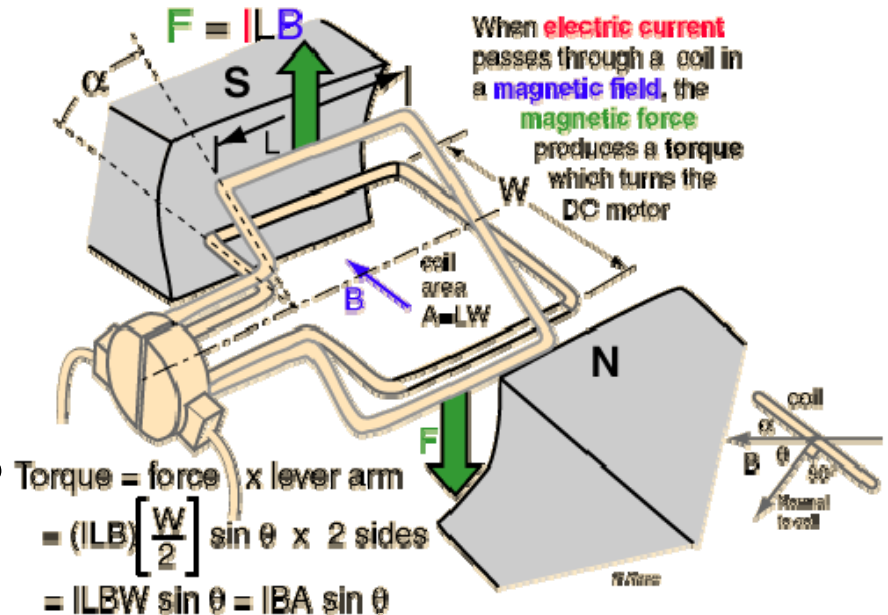- Force on the wire induces a torque about the motor shaft
- Commutator switches direction of current every half cycle
- Direction of torque remains the same throughout the cycle



DC Motors

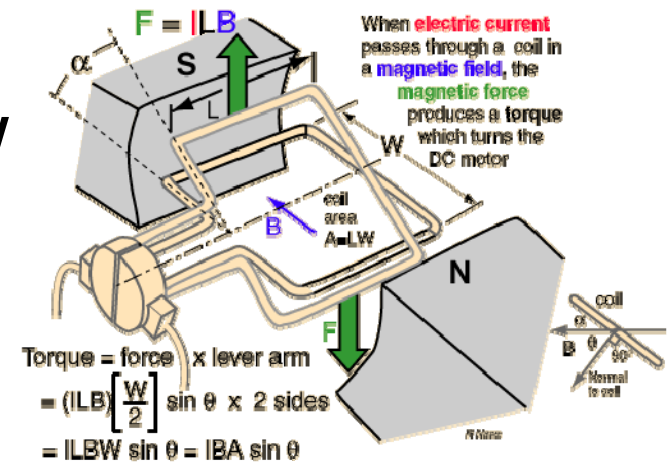- Average motor torque is proportional to current flow through the wire
 - Wire has some resistance




- Direction of current flow determines torque direction

How can a digital input control torque magnitude?

DC Motors

How can a digital input control torque magnitude?

- Use Pulse Width Modulation (PWM)!

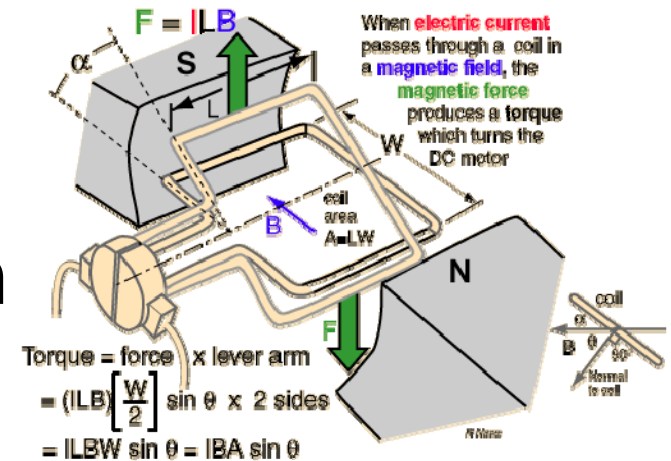


How do we handle torque direction?

DC Motors

How do we handle torque direction?

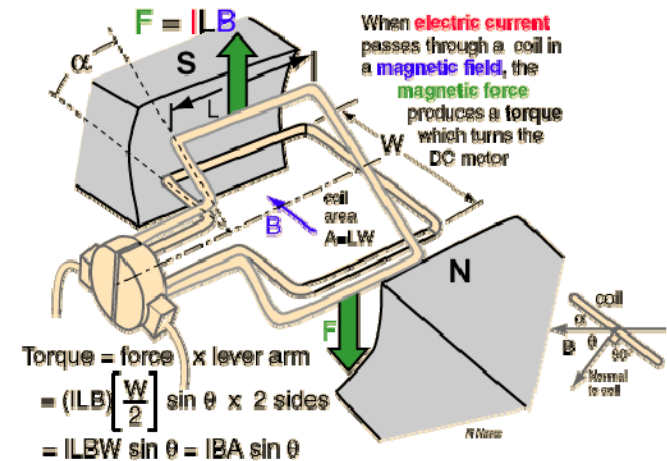- +5V to north 0V to south
- 0V to north +5V to south



How would we implement this with our microcontroller?


DC Motor Control

One possibility...

- Connect motor directly to the I/O pins

Two directions:

- PD2: 1; PD3: 0
- PD2: 0; PD3: 1

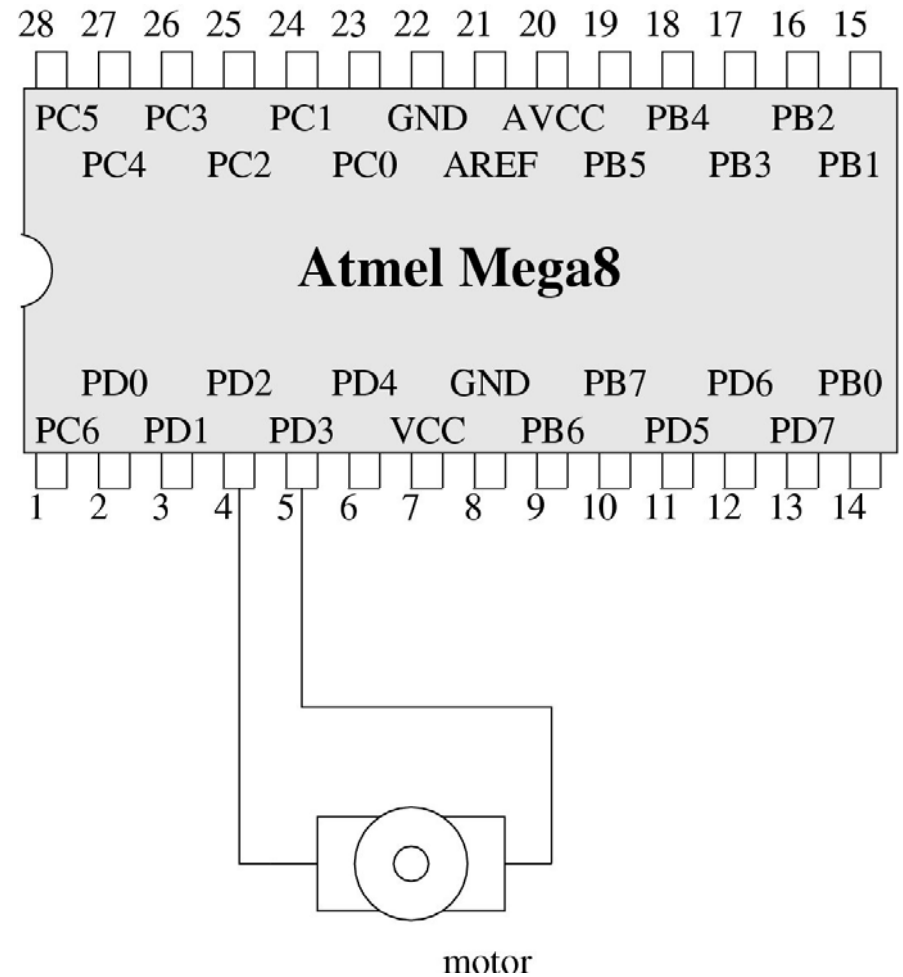


DC Motor Control

One possibility...

- Connect motor directly to the I/O pins

What is wrong with this implementation?

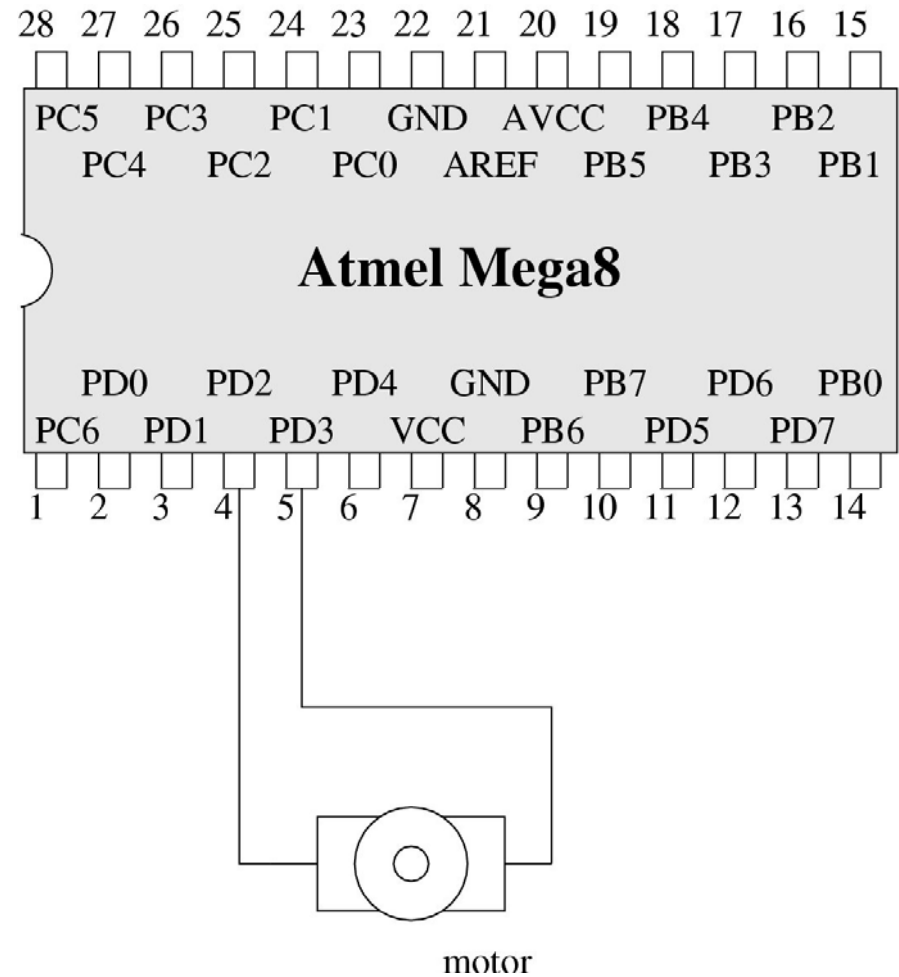


DC Motor Control


What is wrong with this implementation?

- Our I/O pins can source/sink at most 20 mA of current
- This is not very much when it comes to motors...

How do we fix this?

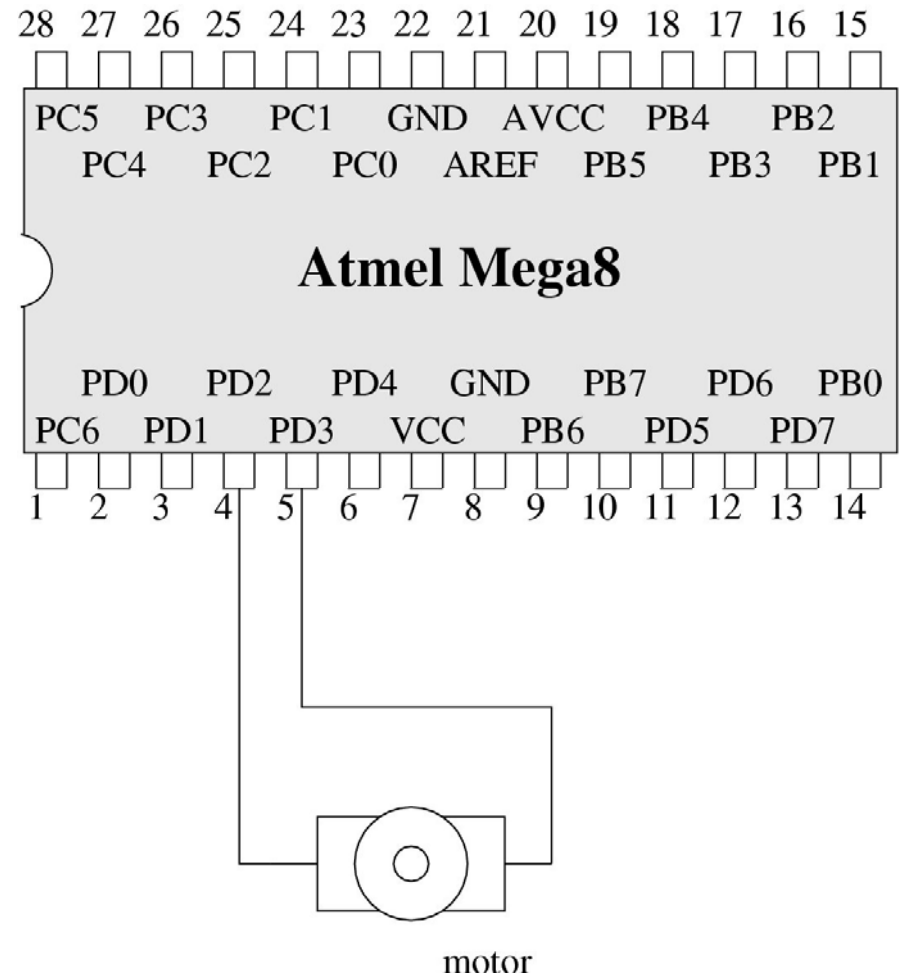

NPN Transistors

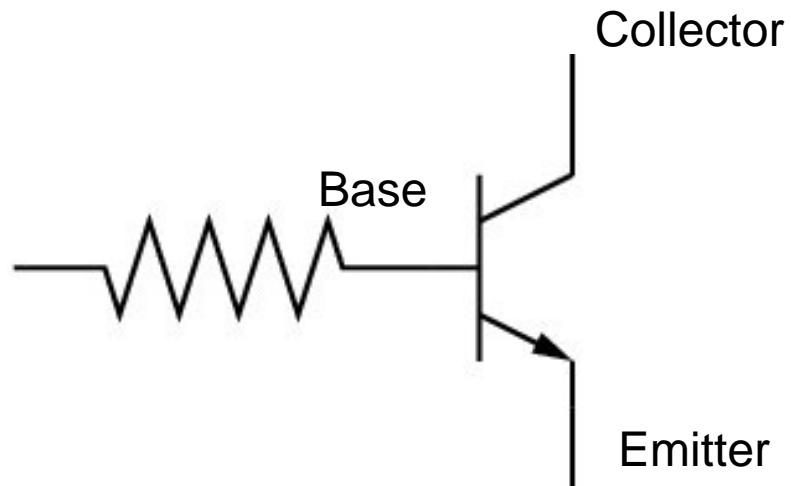


If there is current flow:

- Base to emitter, and
- (possibly) collector to emitter

Transistors as Switches

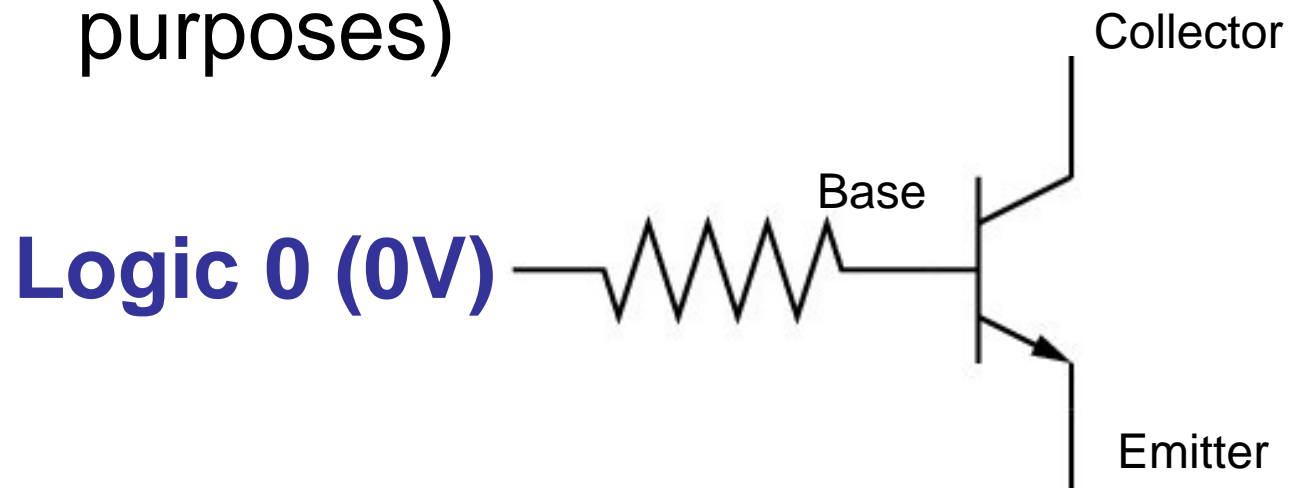
(what we need to understand for our purposes)



0 -> no current flow

Transistors as Switches

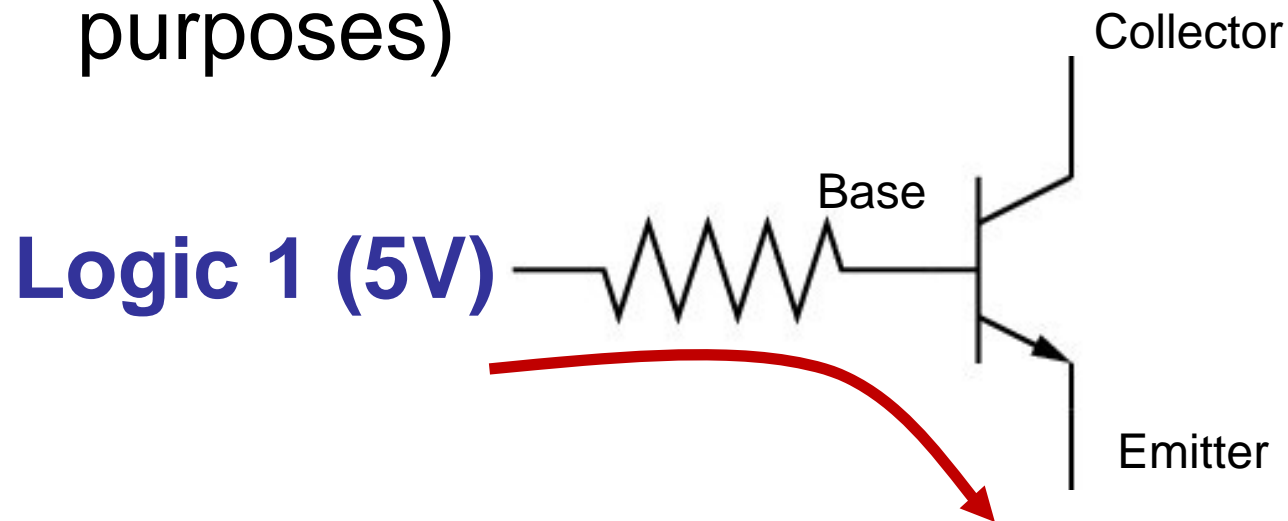
(what we need to understand for our purposes)



1 -> small amount of current flow from base to emitter


Transistors as Switches

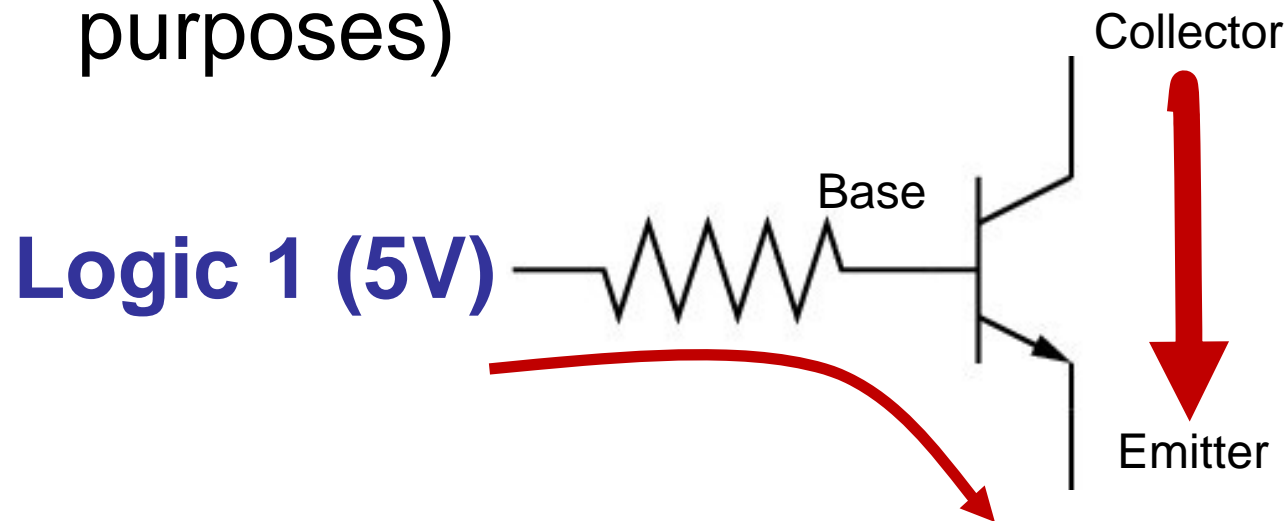(what we need to understand for our purposes)




1 -> small amount of current flow from base to emitter
also allows (possibly large) current to flow from
collector to emitter

Simple H-Bridge

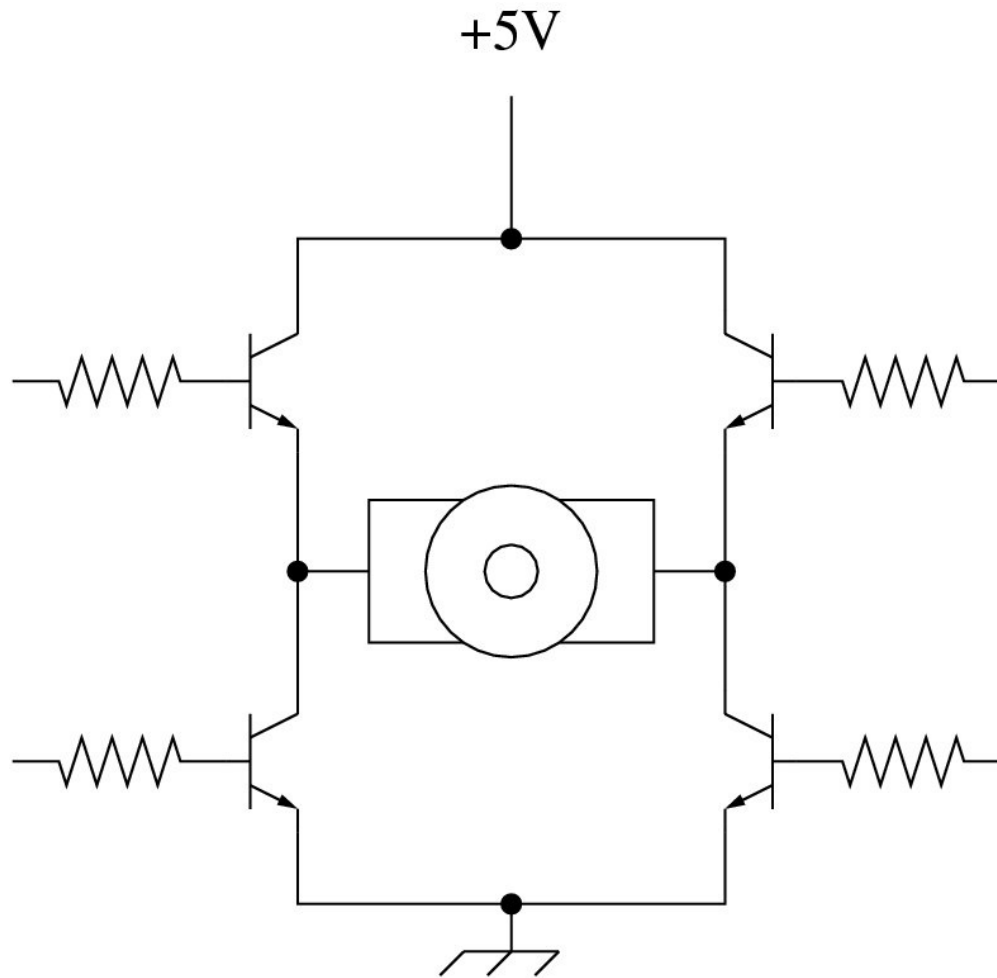

Simple H-Bridge


What happens with these inputs?

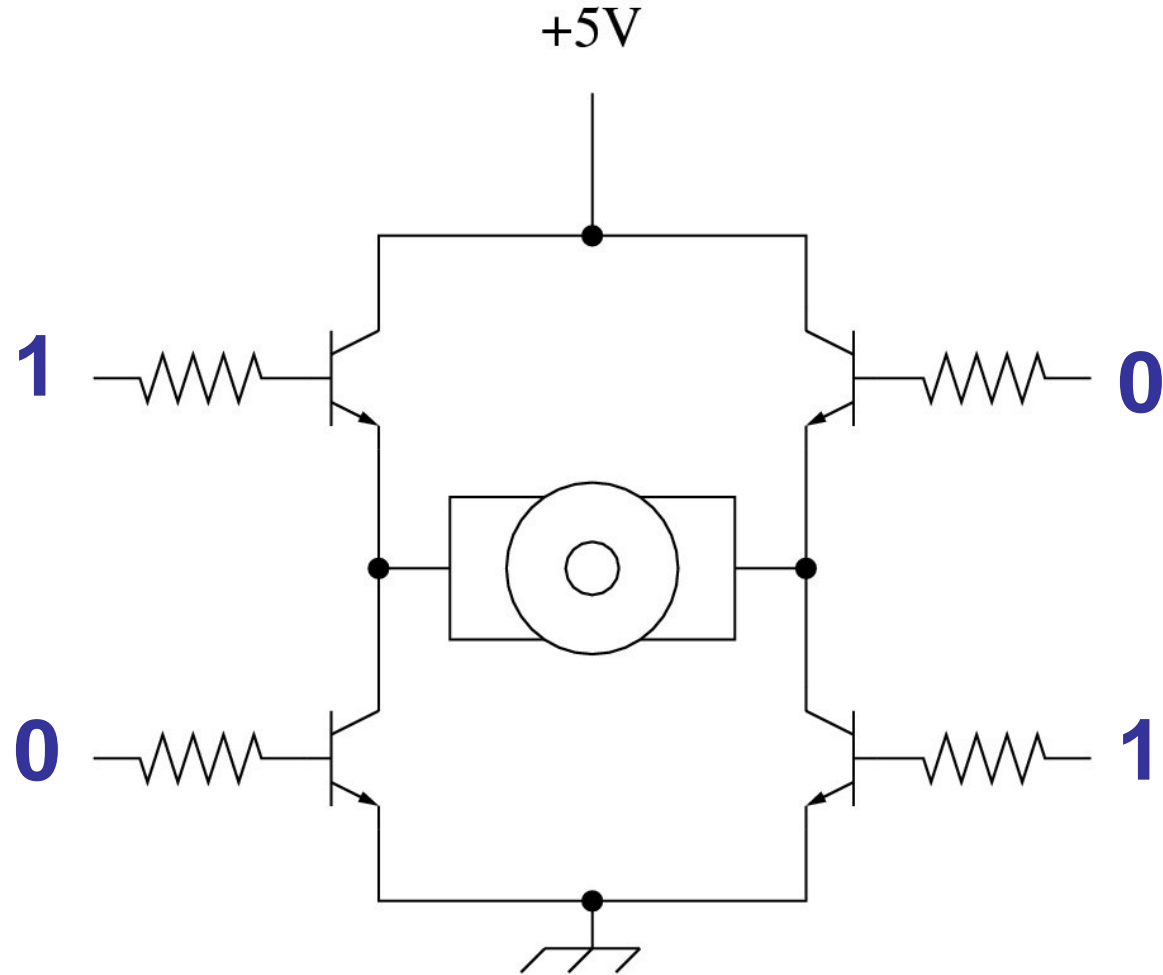

Simple H-Bridge


What happens with these inputs?

- Motor turns in one direction

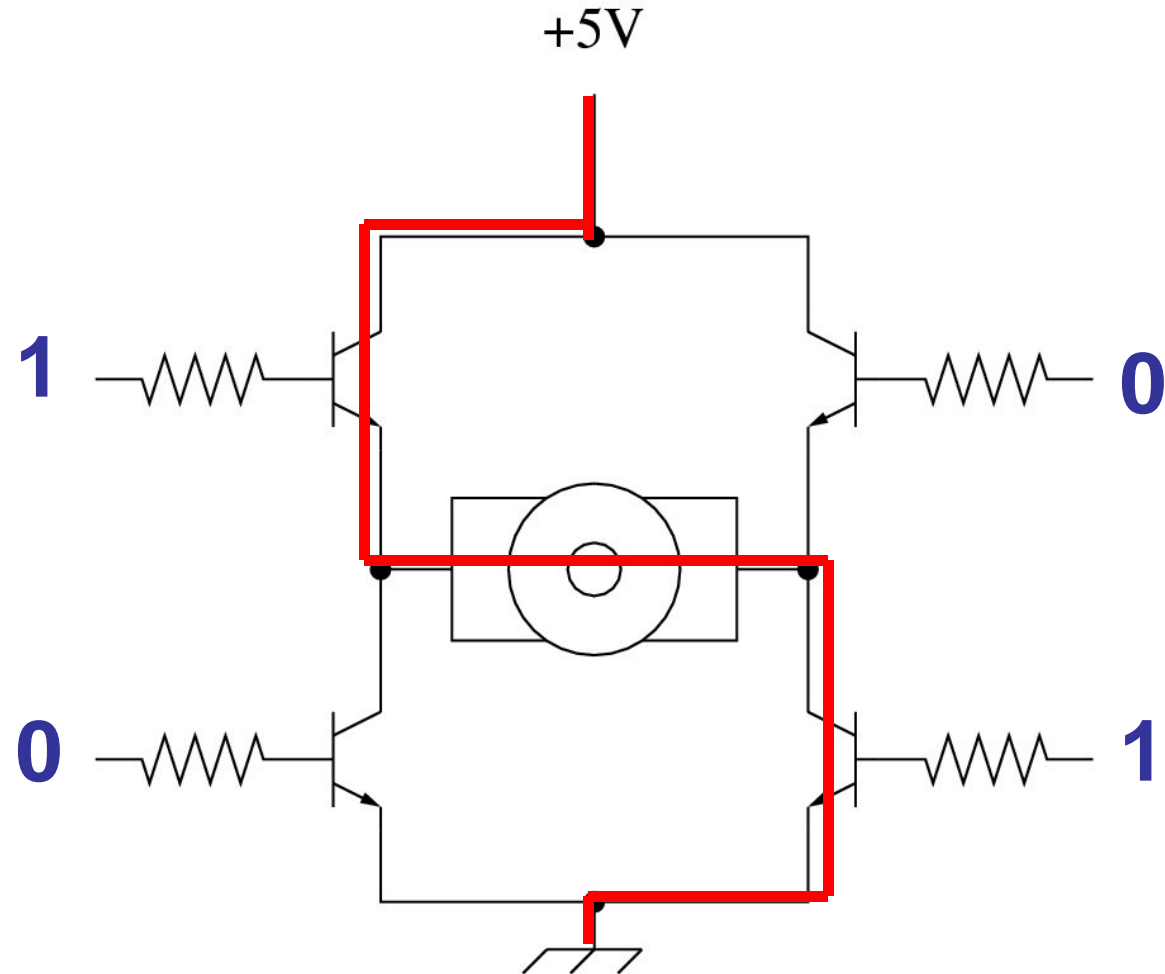

Simple H-Bridge


How about these inputs?

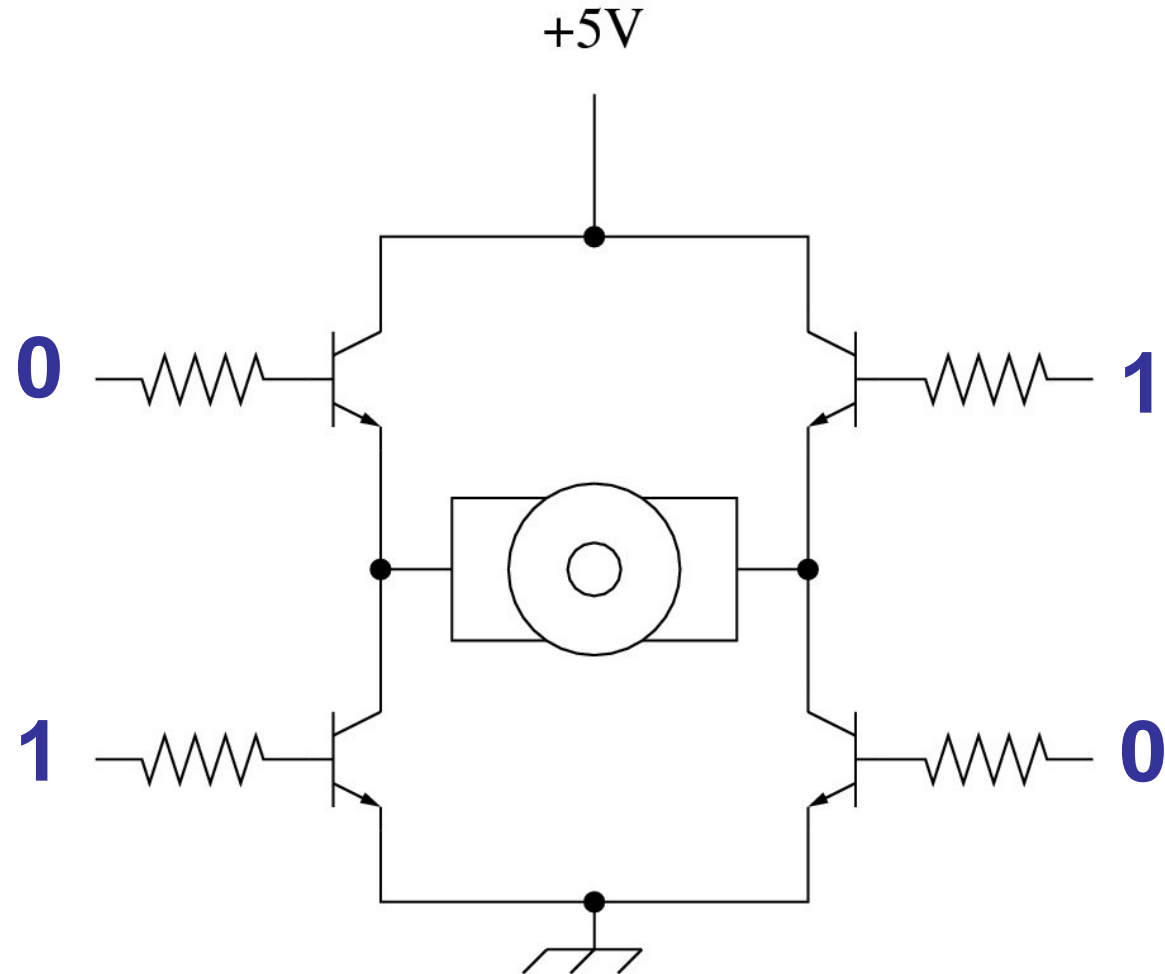

Simple H-Bridge


What happens with these inputs?

- Motor turns in the other direction!

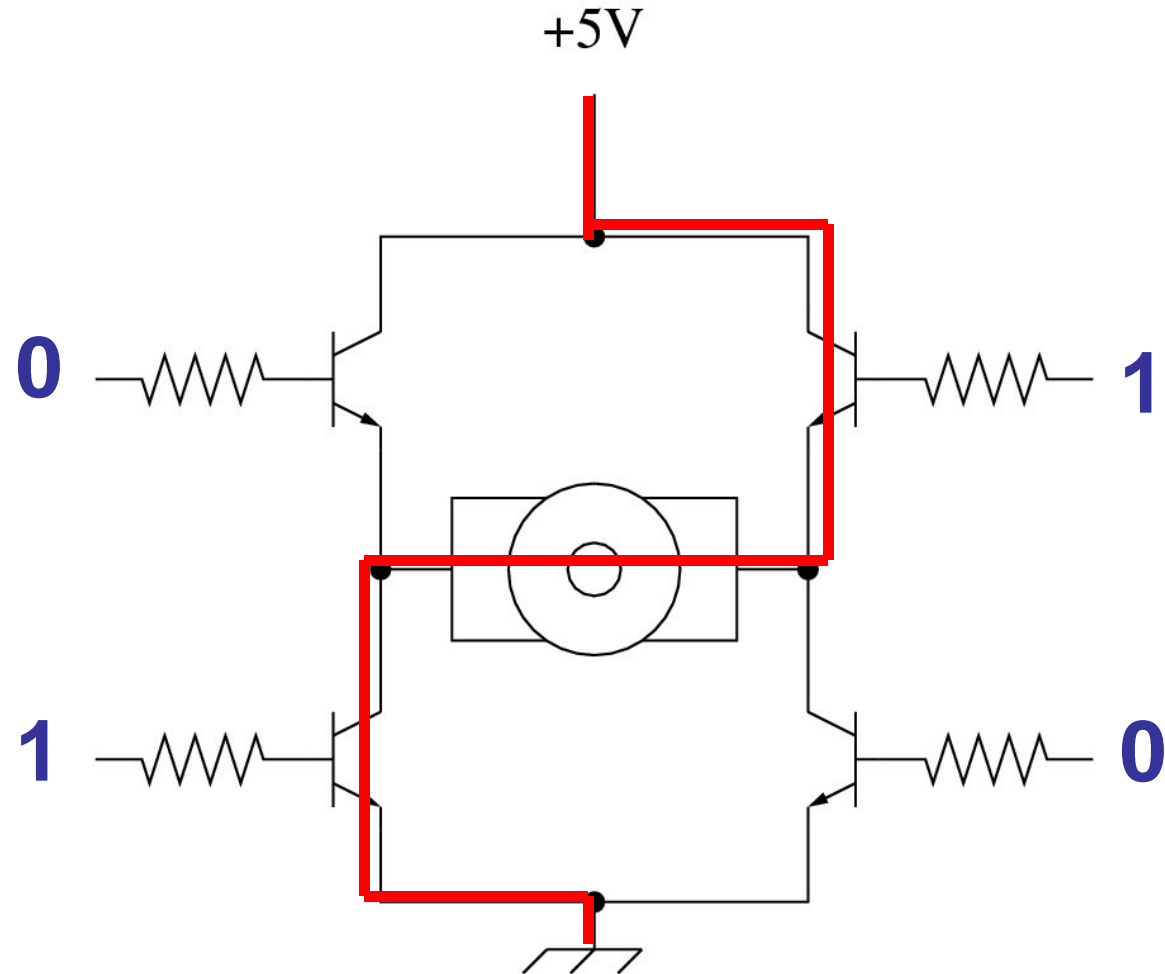

Simple H-Bridge


How about
these
inputs?

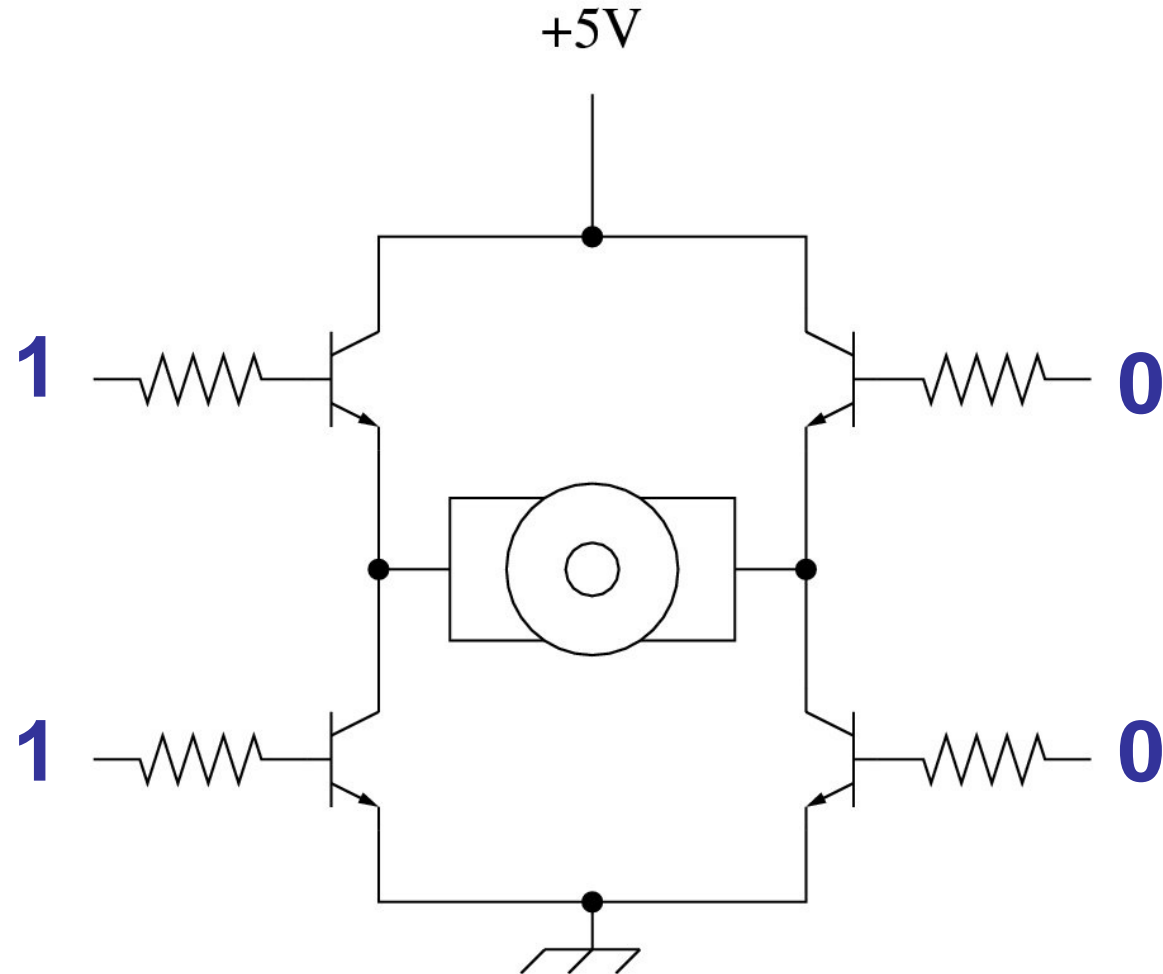

Simple H-Bridge


What happens with these inputs?

- We short power to ground ... very bad

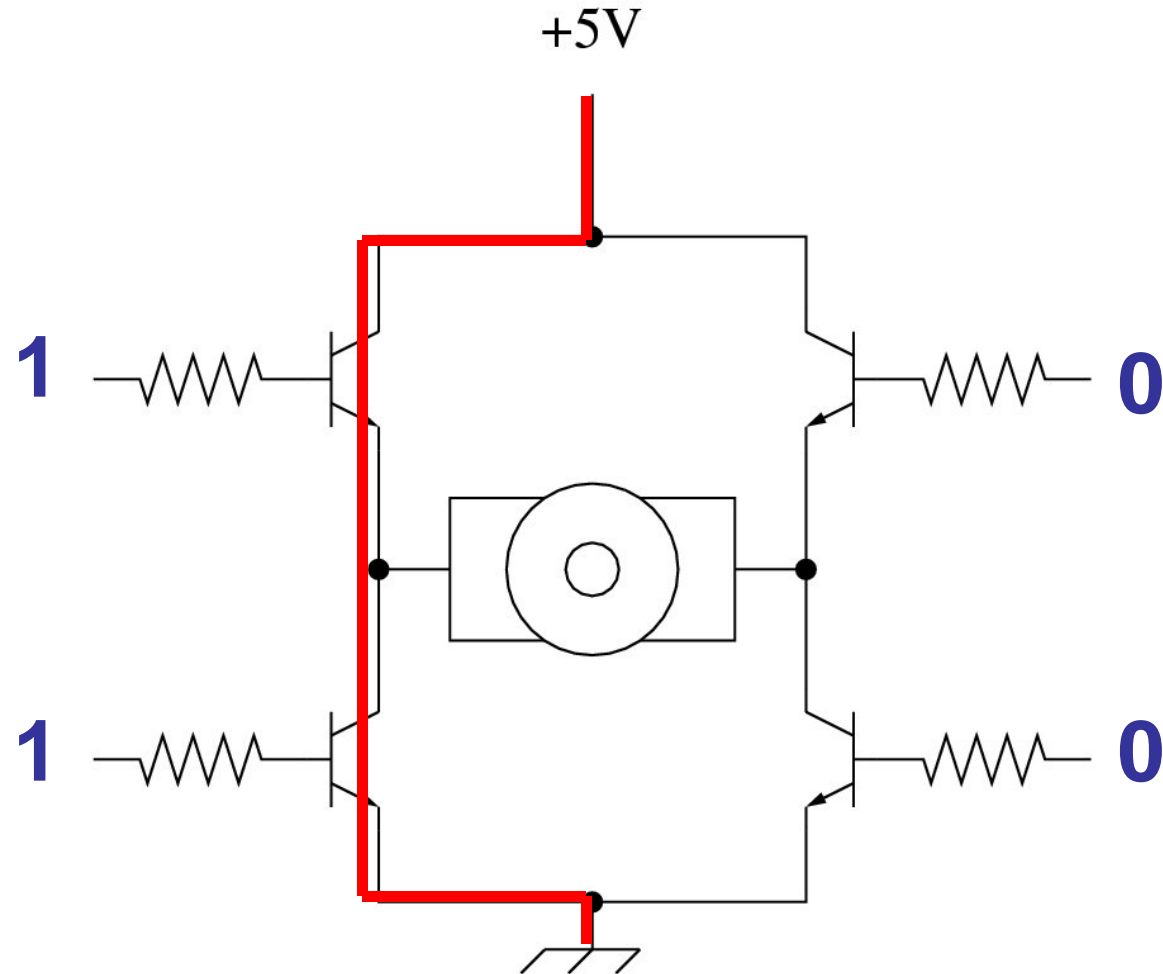


Simple H-Bridge

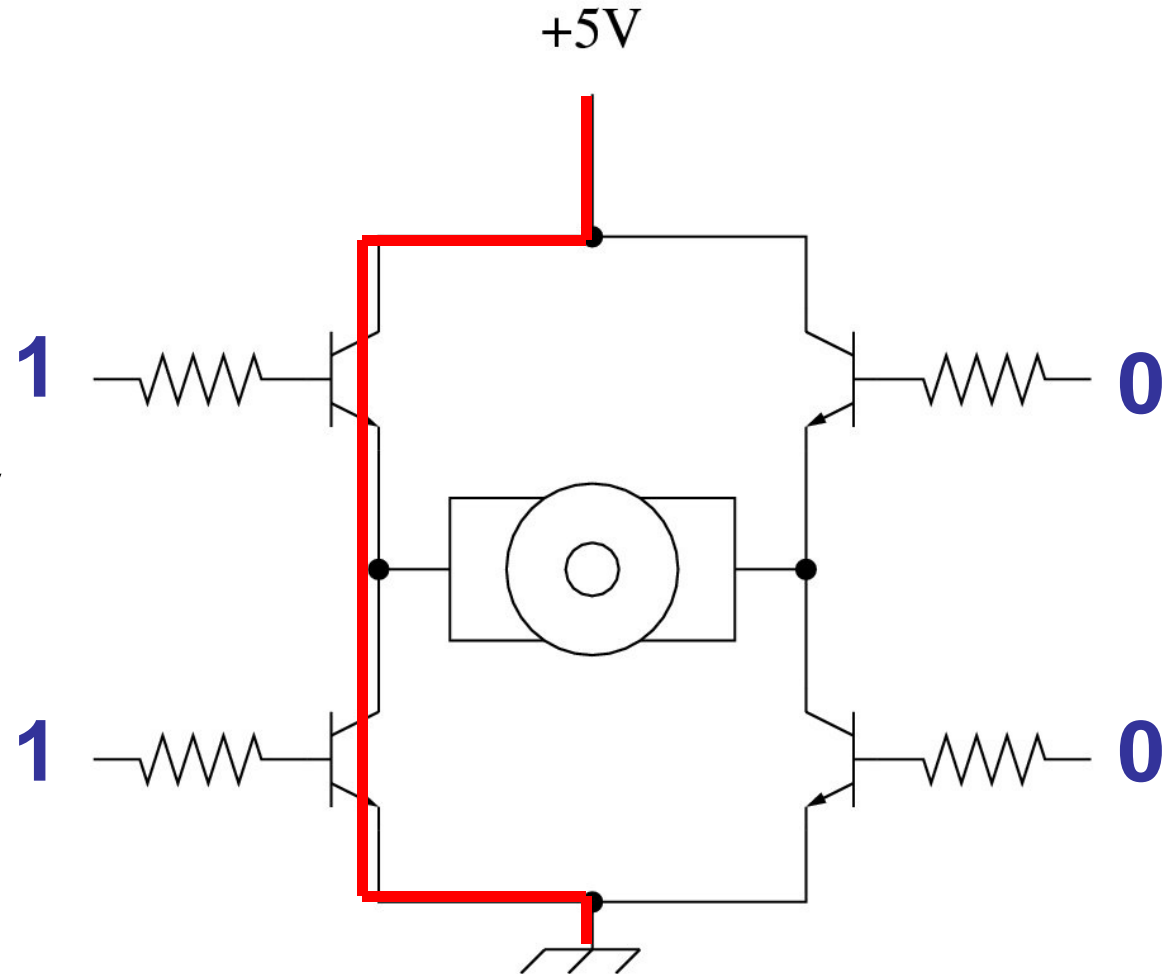How can we prevent a processor from accidentally producing this case?




Modified H-Bridge

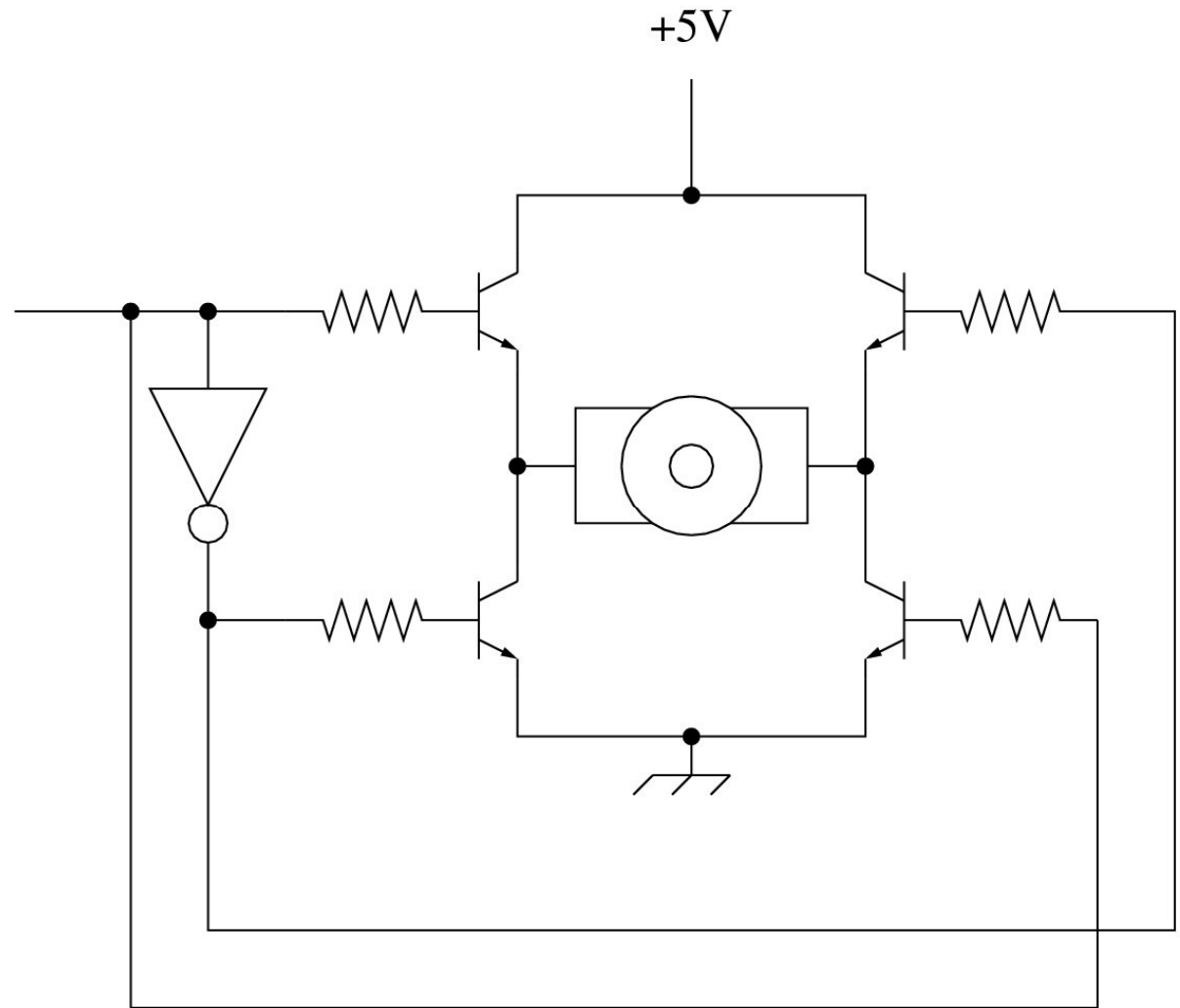We introduce a little logic to ensure the short never occurs




Modified H-Bridge

What happens
with this
input?

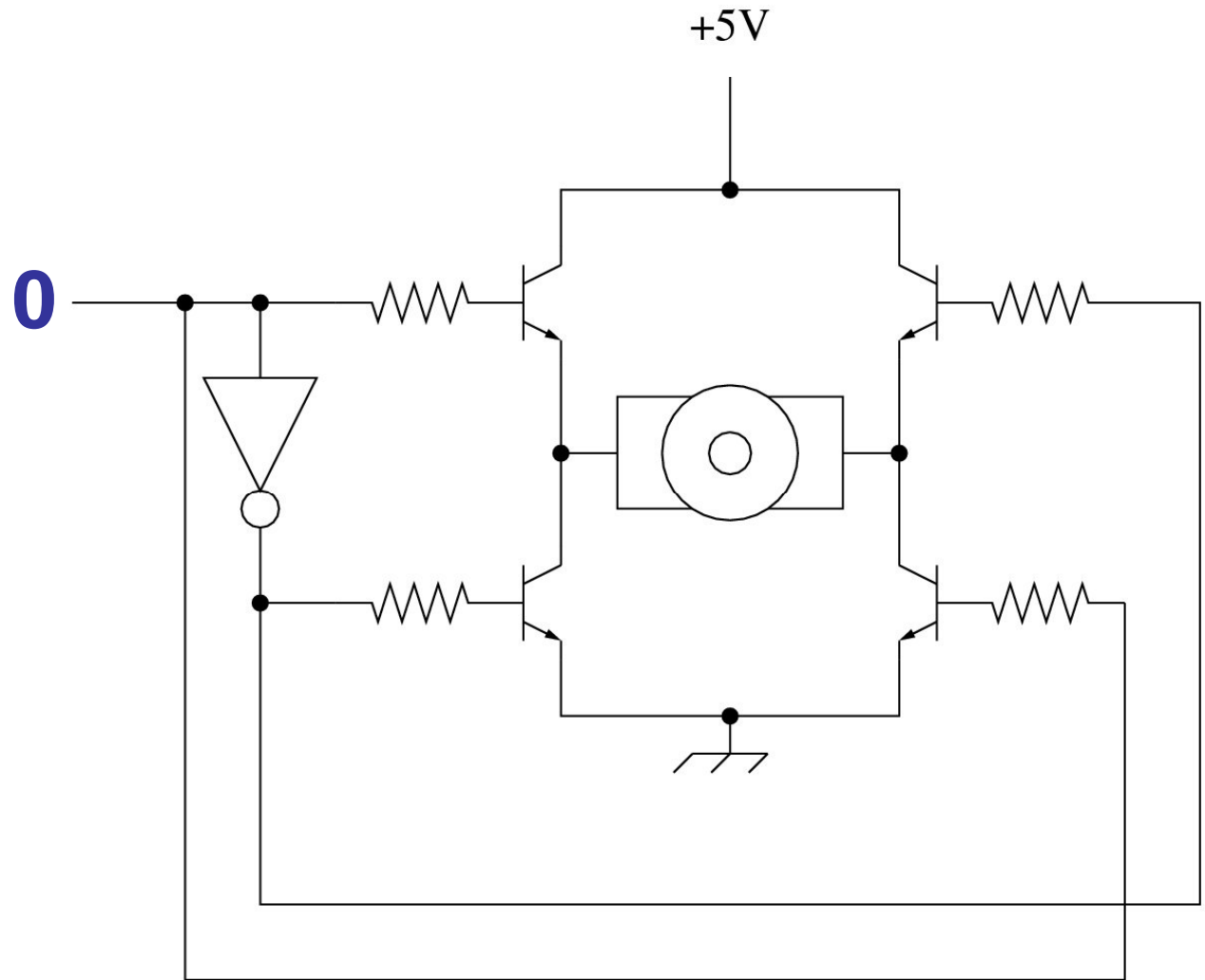

Modified H-Bridge


What happens with this input?

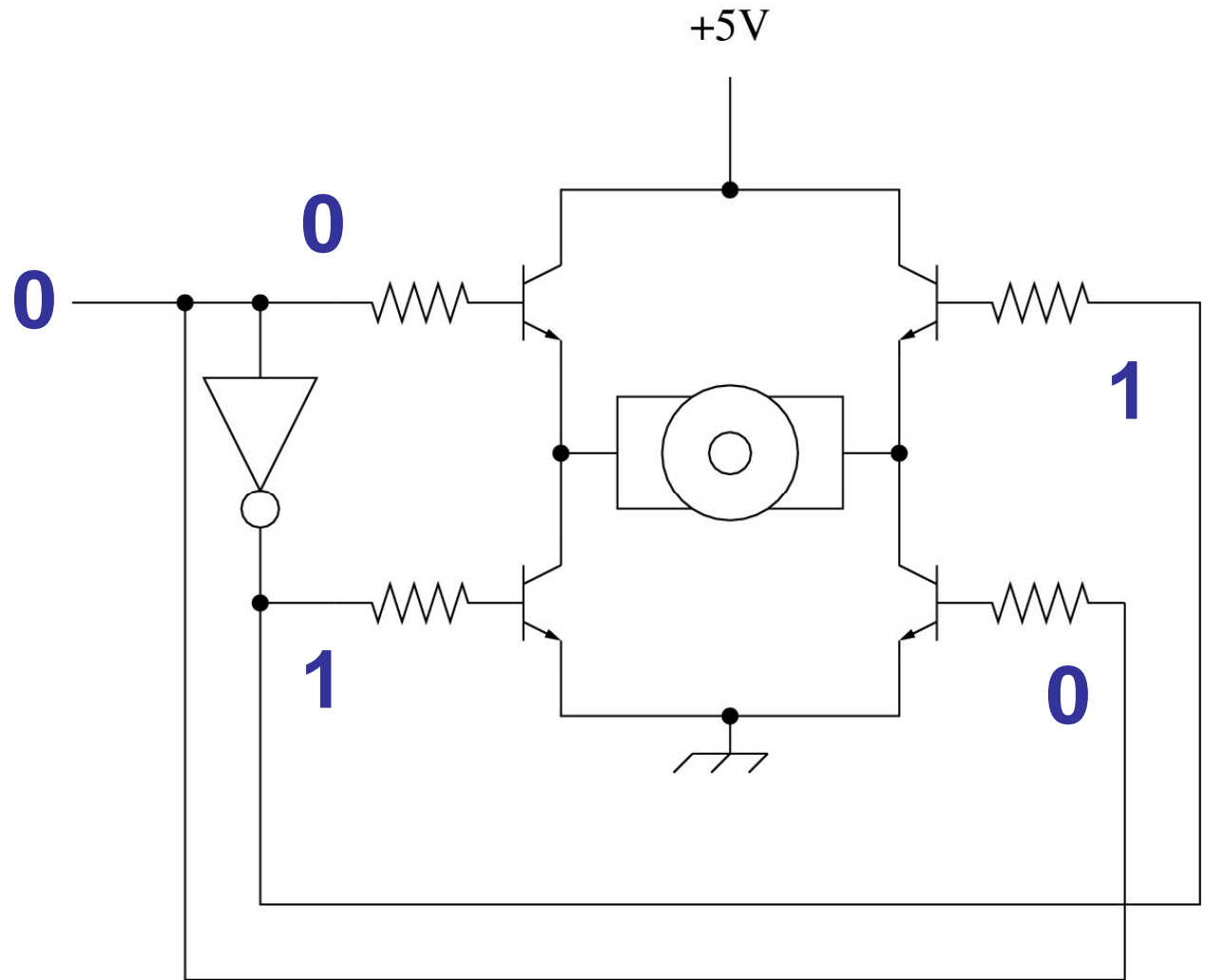

Modified H-Bridge


What happens with this input?

- Motor turns in one direction

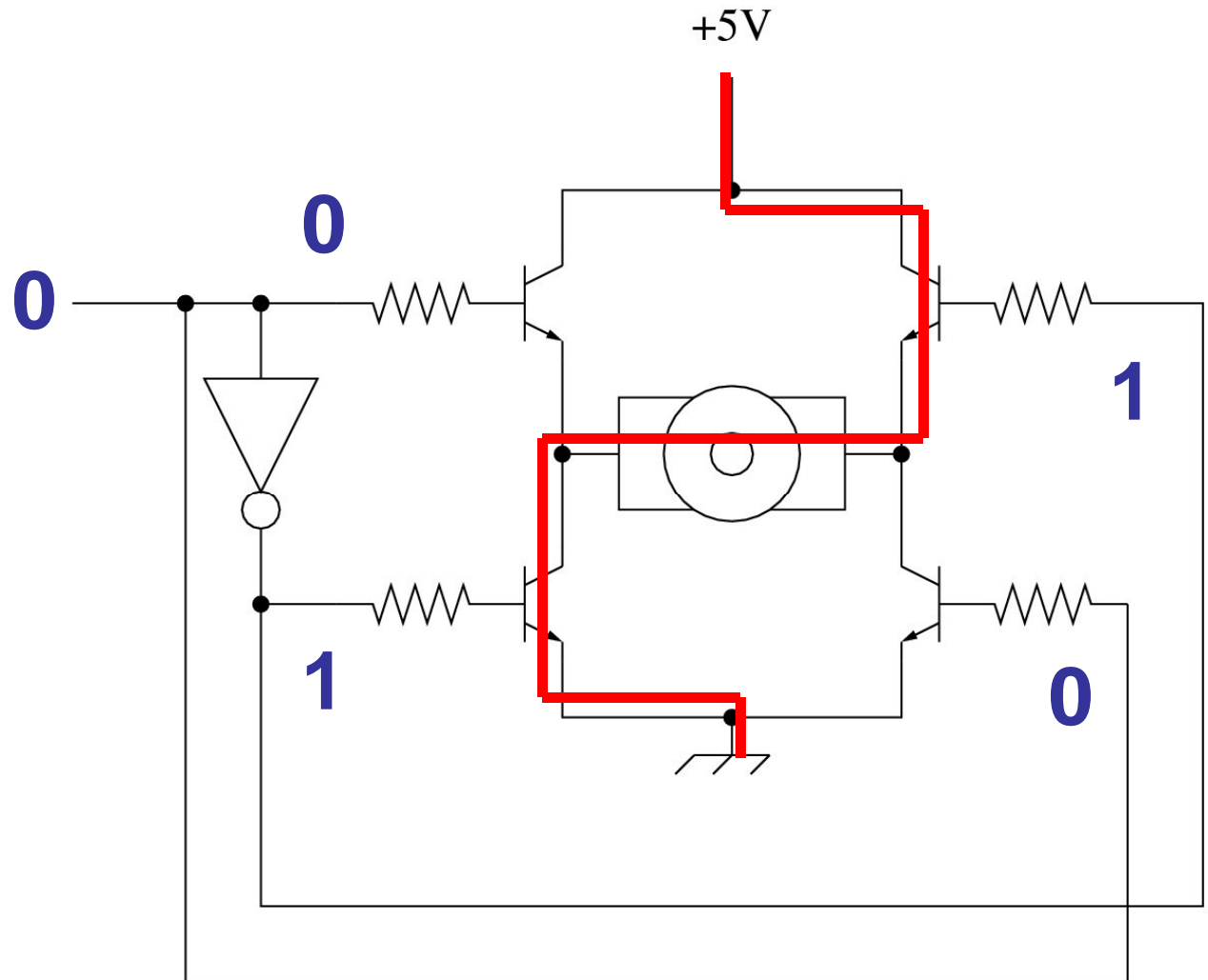


Modified H-Bridge

How about this
input?

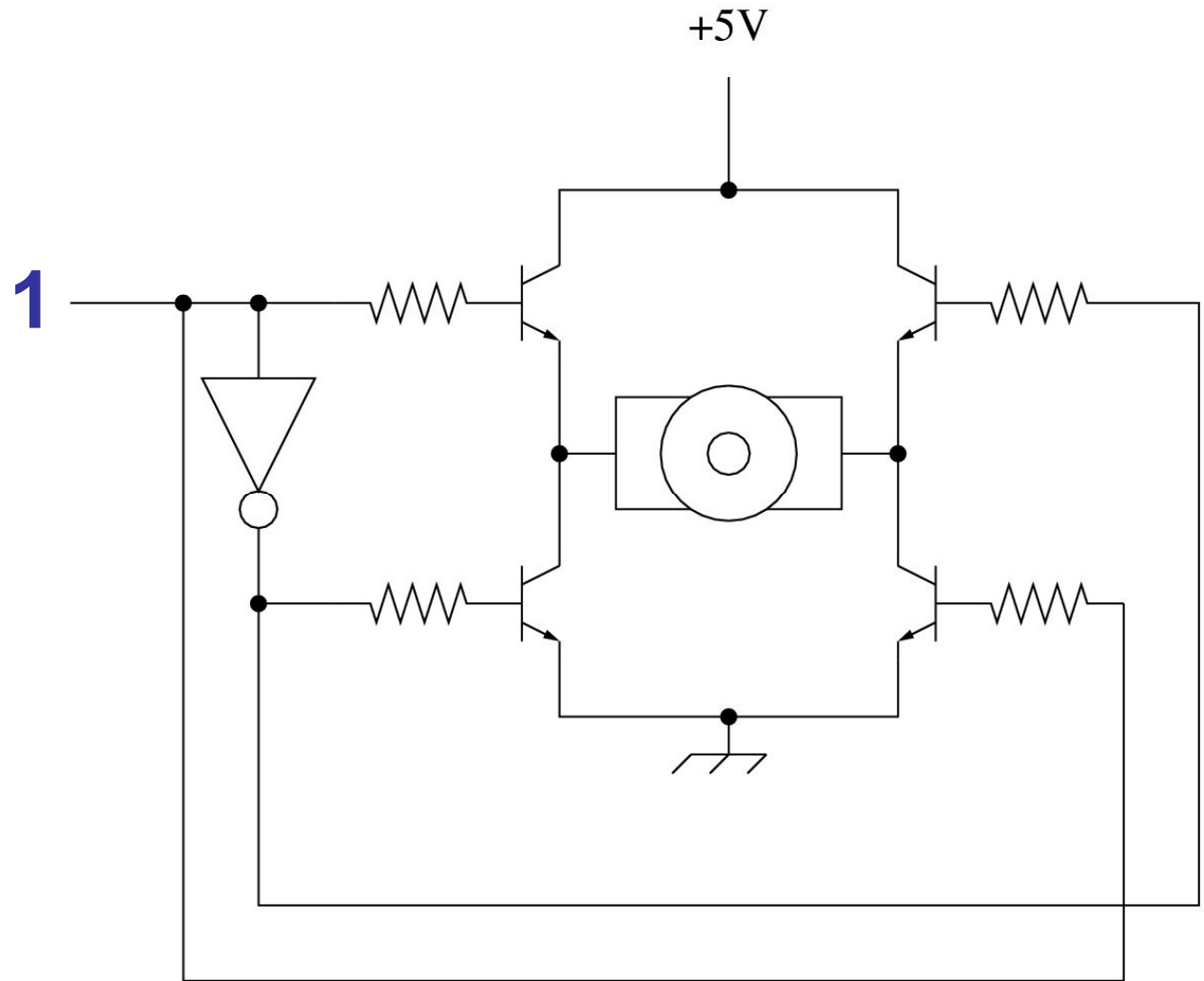

Modified H-Bridge


What happens with this input?

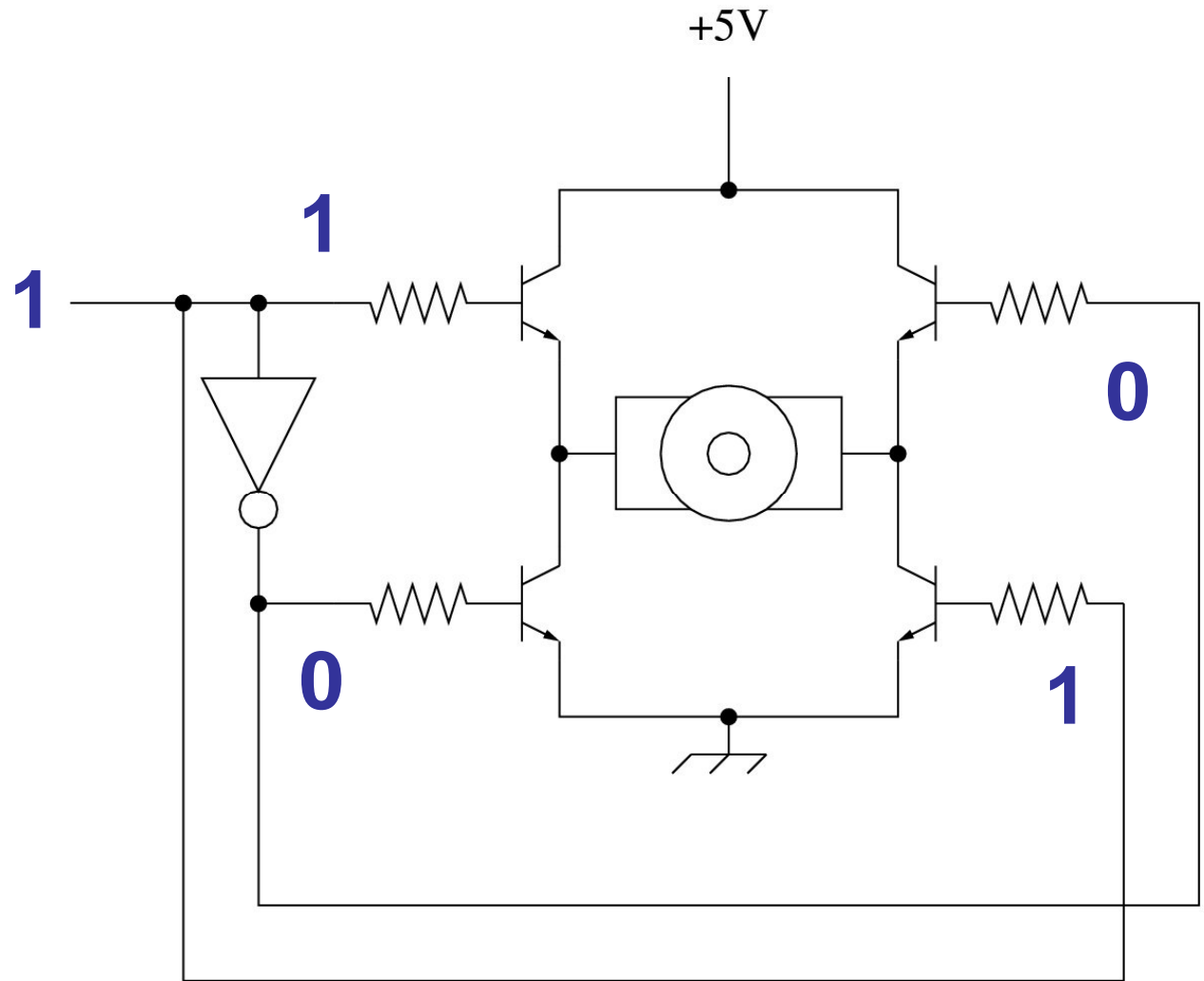

Modified H-Bridge


How about this input?

- Motor turns in the other direction

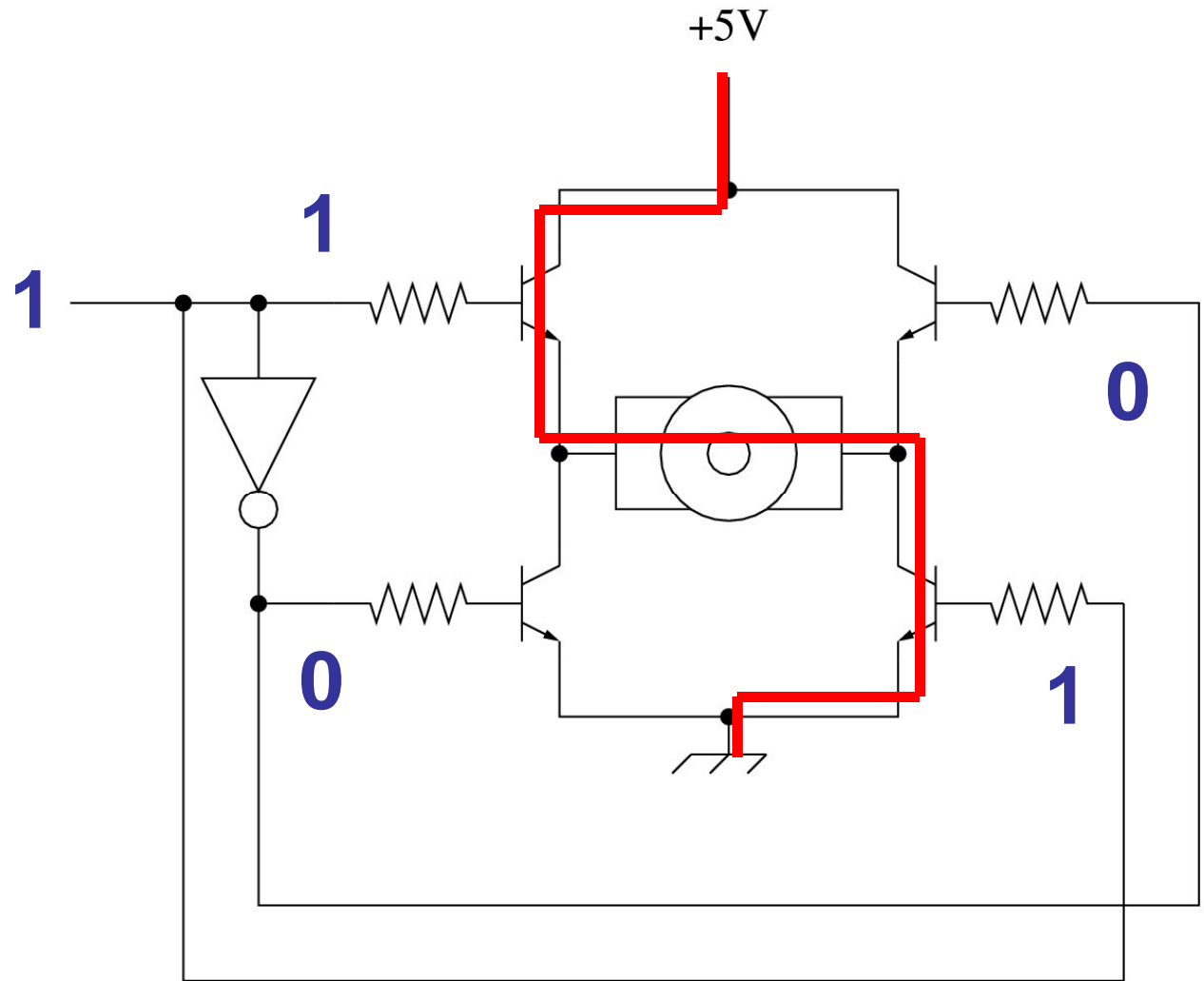

Modified H-Bridge

+5V

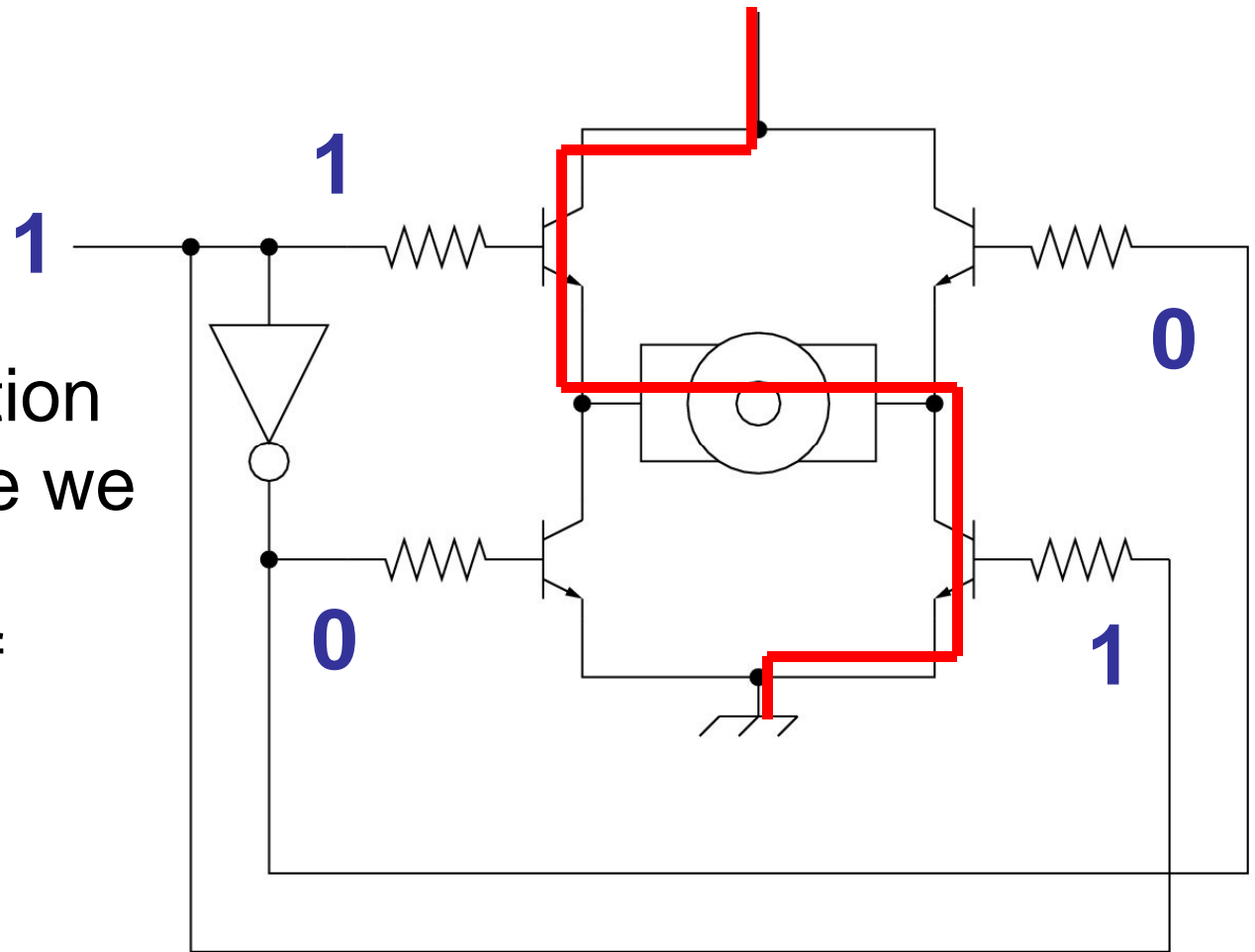

This implementation is nice because we only need one **direction** bit of control


- What are we missing?

Modified H-Bridge


What are we missing?

- Control of torque magnitude
- Let's introduce a second PWM input

What would this look like?

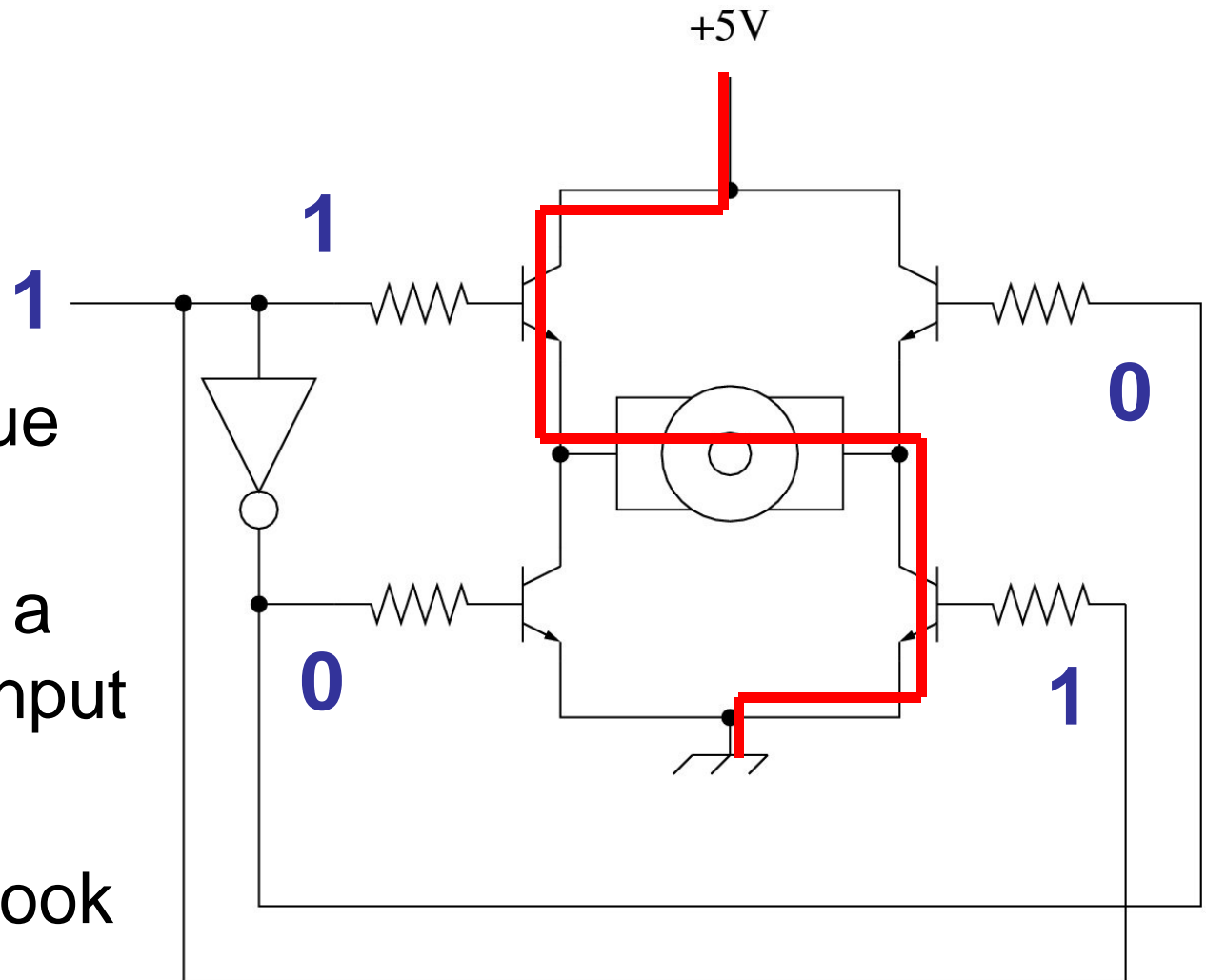


PWM and Direction Control

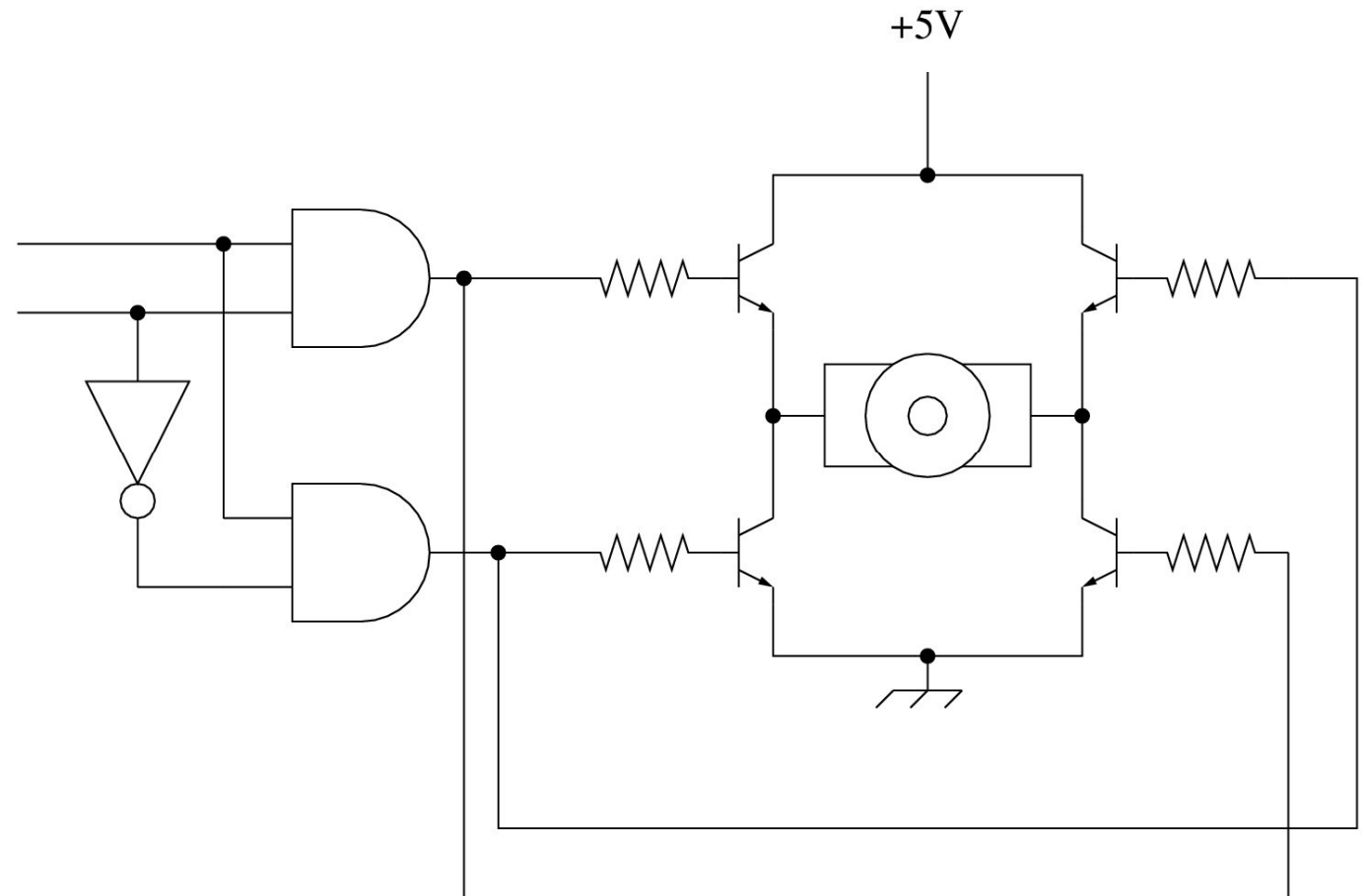


PWM and Direction Control

What happens with this input?

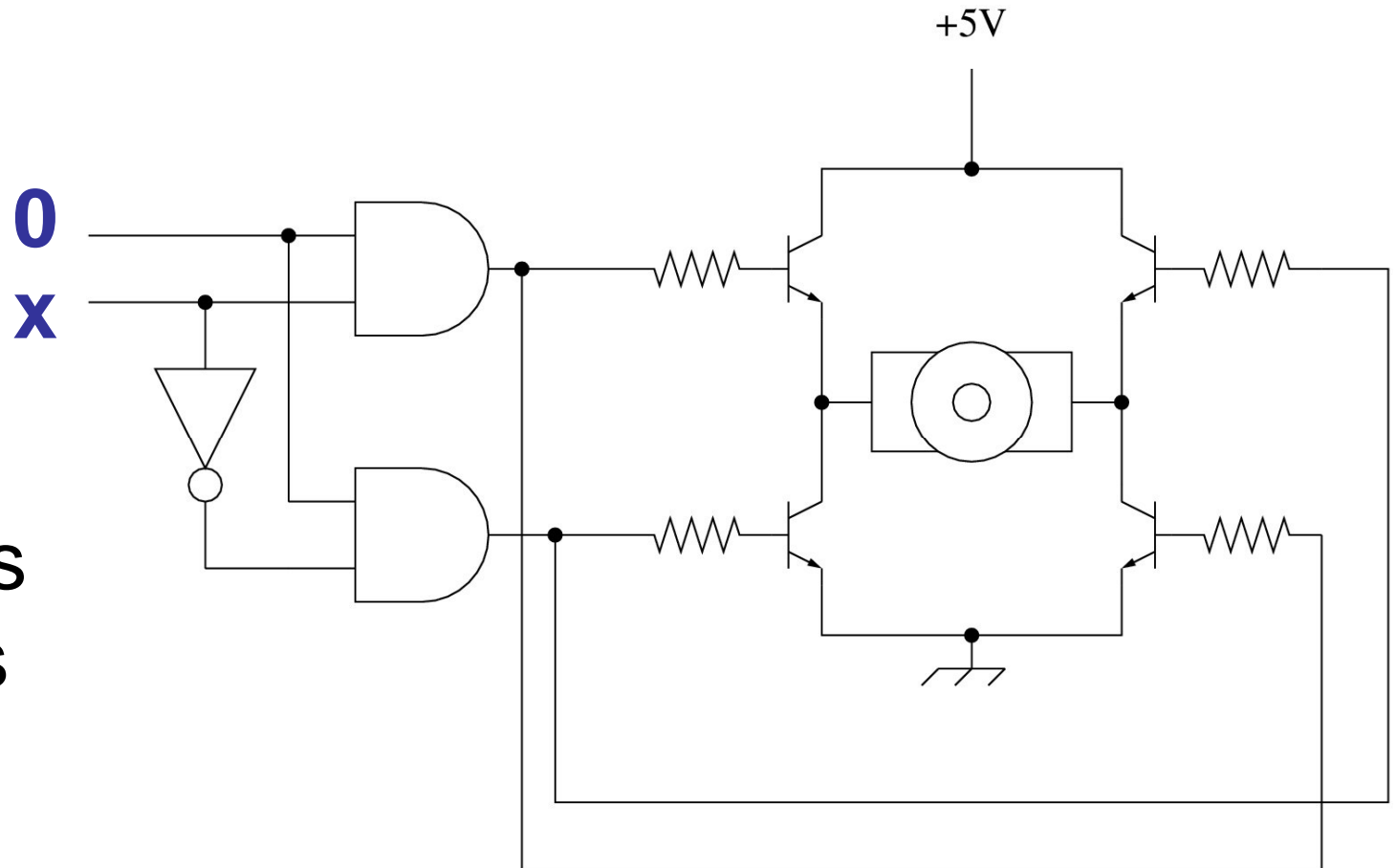


PWM and Direction Control

- What happens?
- No current flow

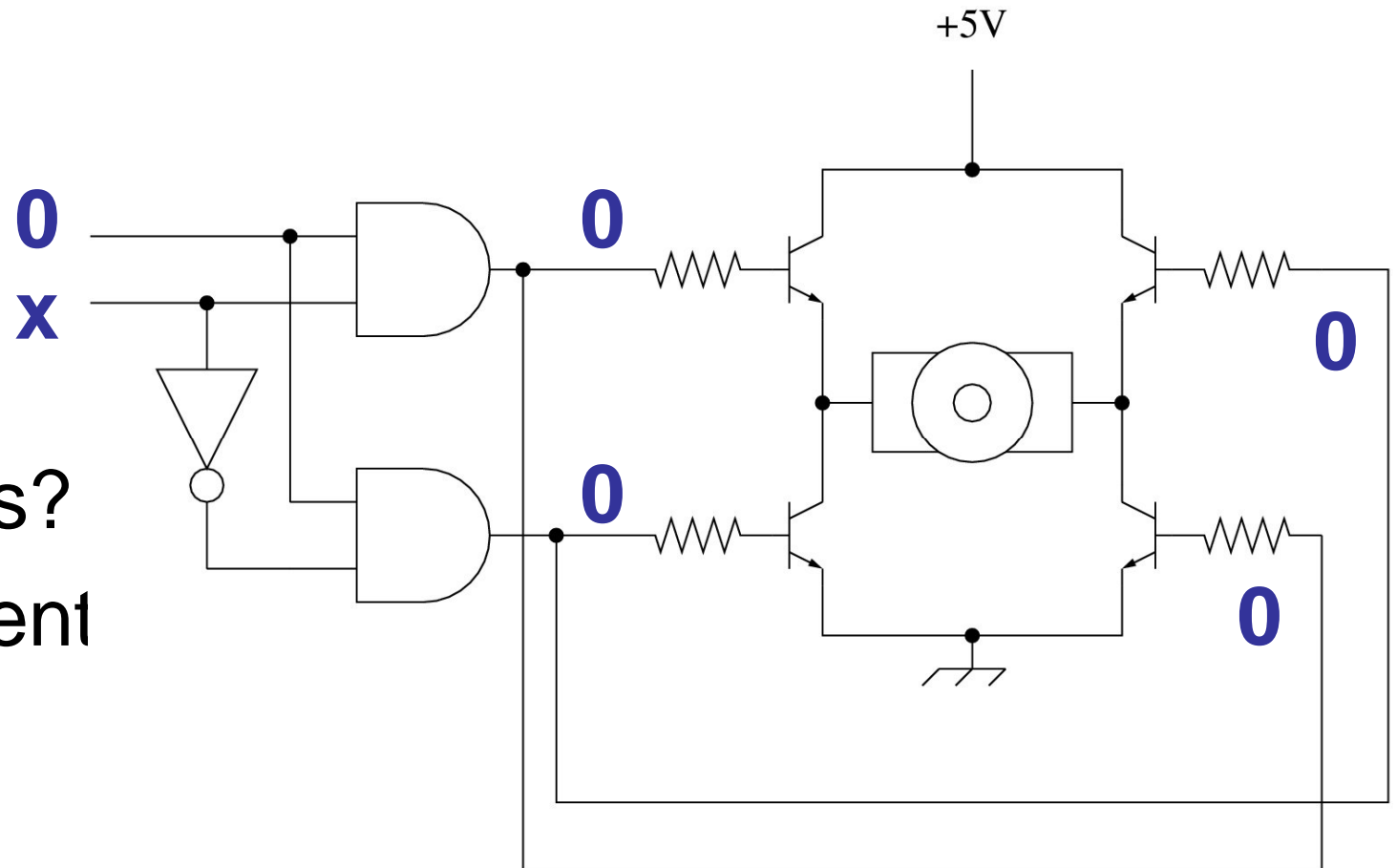


PWM and Direction Control

What happens now?

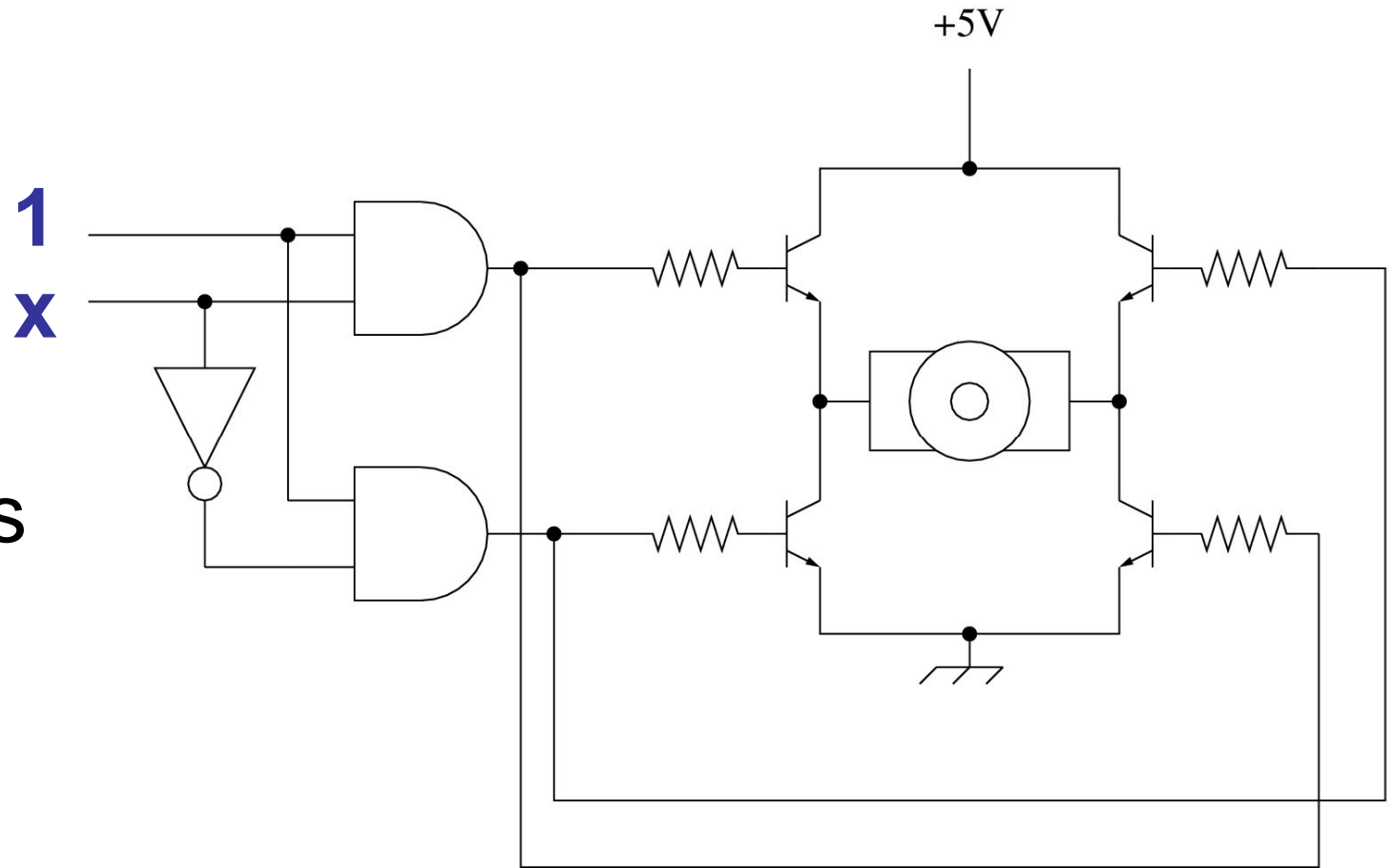

PWM and Direction Control

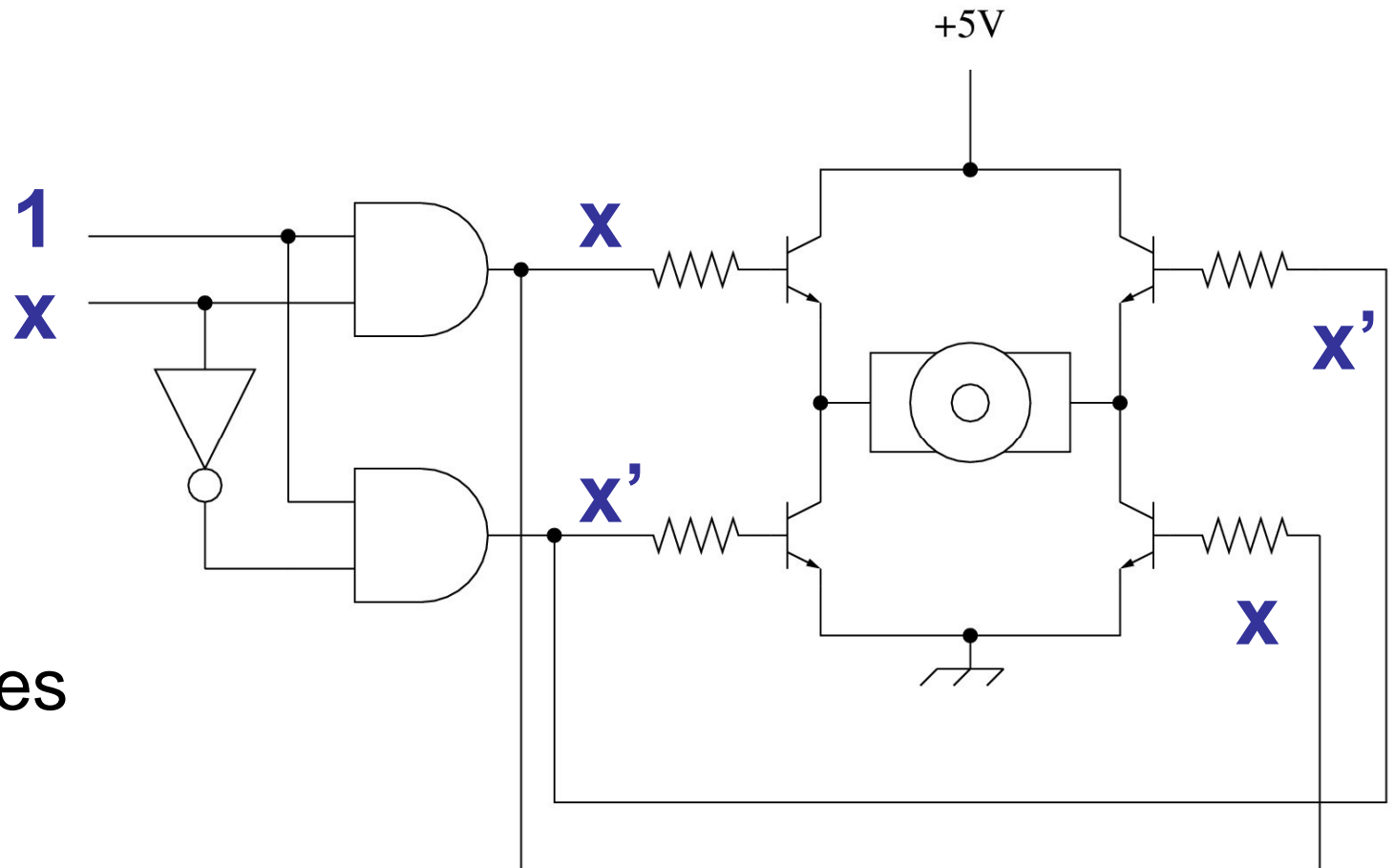- What happens now?
- 'x' determines motor direction




PWM and Direction Control




Direction

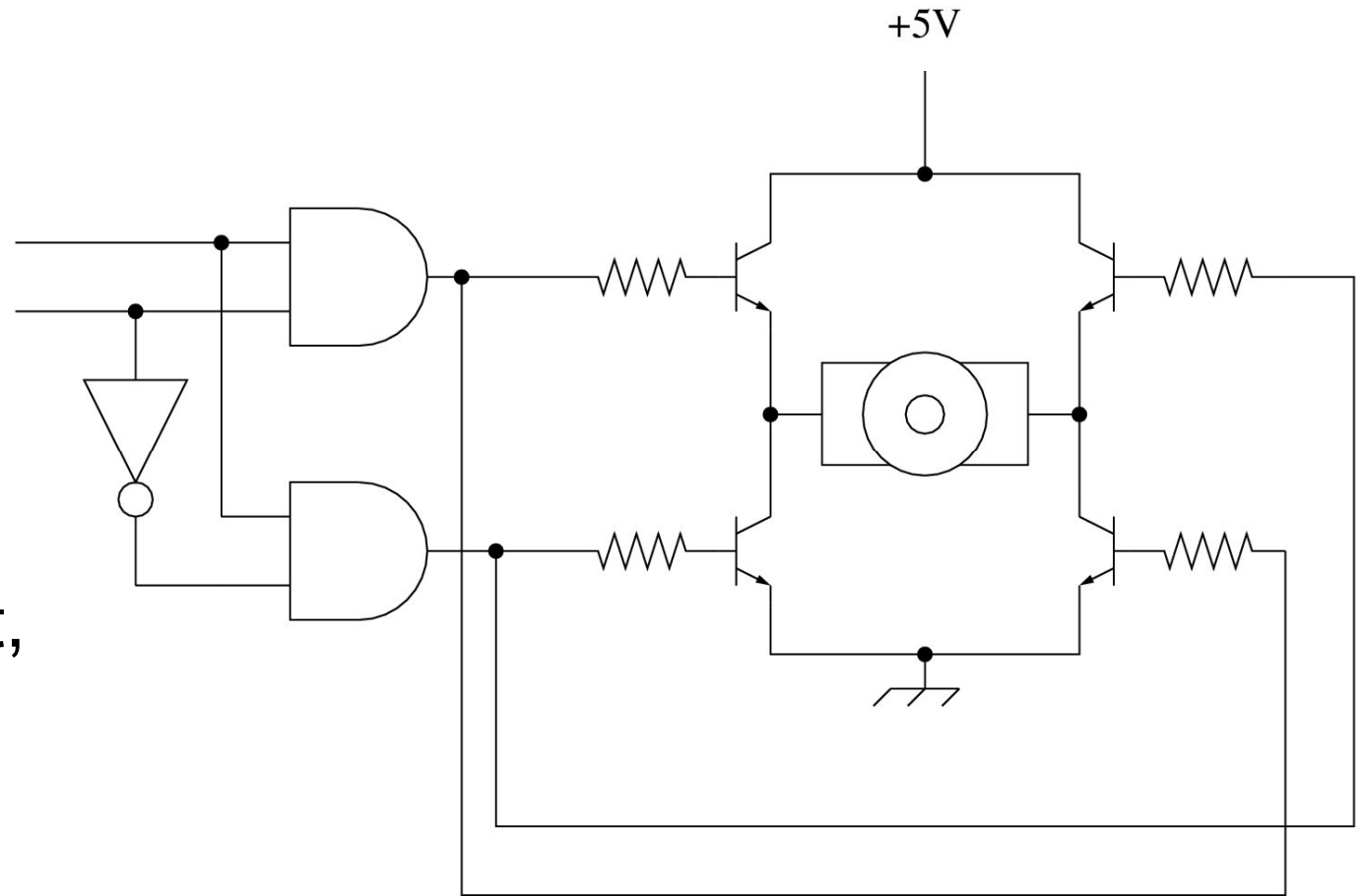With the
PWM input,
we can
control the
magnitude
of torque



Dual H-Bridge for Project 3

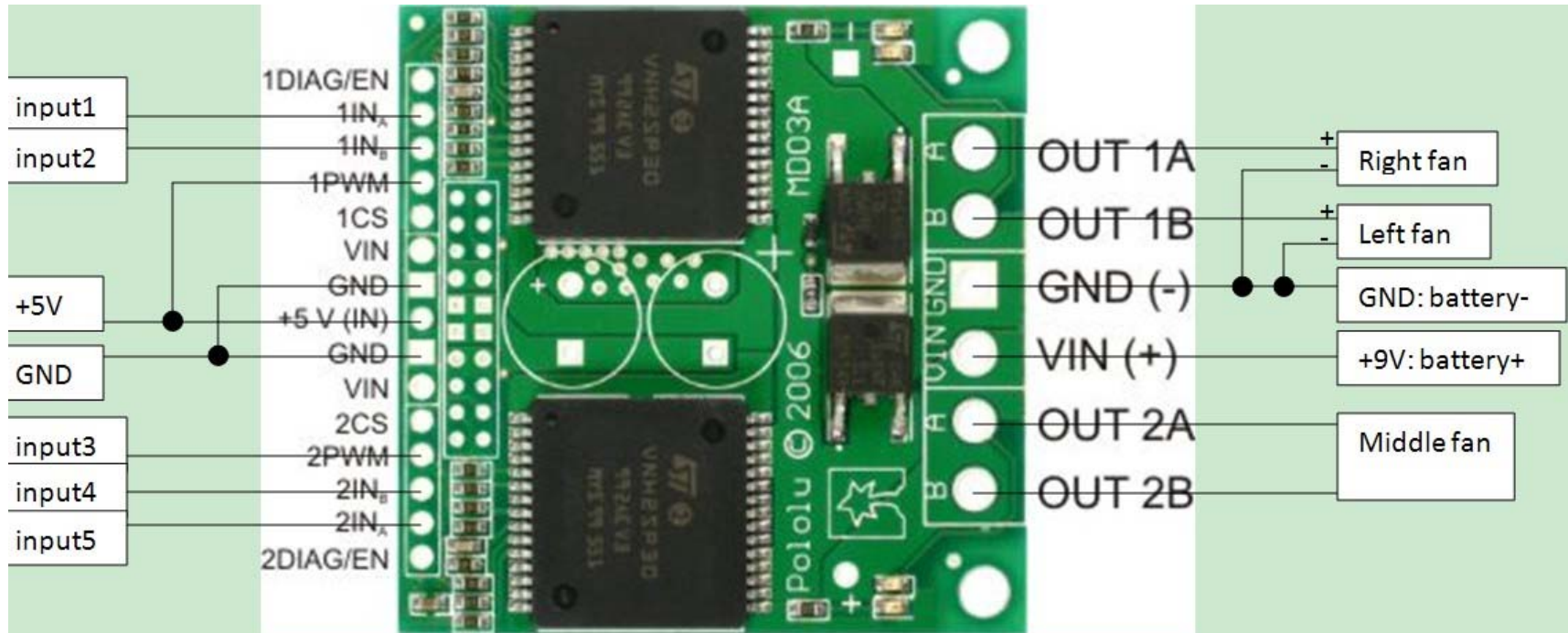

Note: Input1 to input5 should be connected to 5 output pins on Atmega8 and these are the control signals. Particularly, sending a PWM signal to input1 controls the rotational speed of the right fan; sending a PWM signal to input2 controls the rotational speed of the left fan; sending a PWM signal to input3 controls the rotational speed of the middle fan; input4 and input5 control the rotation direction of the middle fan. Specifically, input4=1 & input5=0, one rotation direction; input4=0 & input5=1, the other rotation direction.