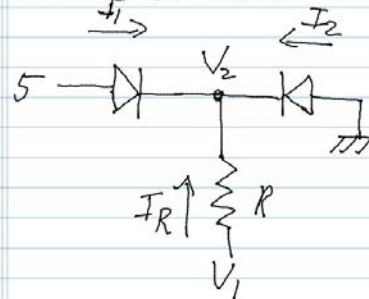


AME 3623 Quiz #3 1/24/13



Knowns:

$$V_{f1}$$

$$V_{f2}$$

$$R$$

$$\text{Assume } V_{f1} = V_{f2} = 0.7$$

(A) What is always true?

$$I_1 + I_2 + I_R = 0$$

$$V_1 - V_2 = I_R R$$

(B) What is I_R as a function of V_1 ? (Draw)

4 cases

Case 1: Both on

$$I_1 > 0$$

$$I_2 > 0$$

$$5 - V_2 = V_{f1}$$

$$0 - V_2 = V_{f2}$$

$$V_2 = -V_{f2}$$

$$5 + V_{f2} = V_{f1}$$

Can't happen given Assumption!

Case 2: Both off

$$\begin{aligned} I_1 &= 0 & 5 - V_2 < V_{f1} \\ I_2 &= 0 & 0 - V_2 < V_{f2} \\ I_R &= 0 \\ V_2 &= V_1 \\ \downarrow \end{aligned}$$

Check: $5 - V_1 < V_{f1} \rightarrow 5 - V_{f1} < V_1$

$0 - V_1 < V_{f2} \rightarrow V_1 > -V_{f2}$

Given assumption: $2.5 < V_1 < 7.5$ $V_1 > 2.5$

Case 3: #1 off, #2 on

$$\begin{aligned} I_1 &= 0 & 5 - V_2 < V_{f1} \\ I_2 &> 0 & 0 - V_2 = V_{f2} \end{aligned}$$

$$V_2 = -V_{f2}$$

$$-I_2 = I_R = \frac{V_1 - V_2}{R} = \frac{V_1 + V_{f2}}{R}$$

Check: $I_2 > 0 \rightarrow \frac{V_1 + V_{f2}}{R} > 0$

$$\rightarrow -\frac{V_1 + V_{f2}}{R} > 0 \rightarrow V_1 < -V_{f2} \quad \checkmark$$

$5 - V_2 < V_{f1} \rightarrow 5 + V_{f2} < V_{f1}$ Given assumptions, this never happens

Case 4: #1 on, #2 off

$$I_1 > 0 \quad + \quad 5 - V_2 = V_{f1}$$

$$I_2 = 0 \quad + \quad 0 - V_2 < V_{f2} \rightarrow V_2 > -V_{f2}$$

$$V_2 = 5 - V_{f1}$$

$$+I_1 = -I_R = -\frac{V_1 - V_2}{R} = \frac{5 - V_{f1} - V_1}{R}$$

$$\text{Check: } I_1 > 0 \rightarrow \frac{5 - V_{f1} - V_1}{R} > 0$$

$$\rightarrow V_1 < 5 - V_{f1} \quad \checkmark$$

$$\boxed{V_1 < 2.5 \text{ V. or } 1/2}$$

$$V_2 > -V_{f2} \rightarrow 5 - V_{f1} > -V_{f2}$$

$$\rightarrow 5 > V_{f1} + V_{f2}$$

Given Assumptions, this is true

Summary: Case 2 when ~~#1~~ $V_1 > 2.5$

Case 4 when $V < 2.5$

Cases 1 & 3 never happen

Answer to part B:

