

# Embedded Systems (CS [45]163)

## Homework 2


March 4, 2009

This homework assignment is due on Thursday, March February 12th at 5:00pm. Your work may be handed in electronically (use the **Homework 2** digital dropbox on D2L) or in hardcopy form (in person or under door).

This assignment must be done individually: do not share/discuss your answers with others or look at the answers of others.

### Question 1

Consider the following circuit:

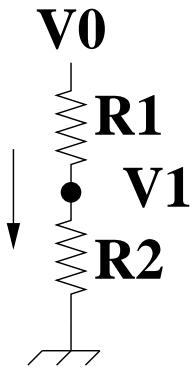


Assume  $V0 = 5V$ .


1. (10pts) Assume  $R2 = 100\Omega$ . Show  $V1$  and  $I$  as a function of  $1\Omega \leq R1 \leq 299\Omega$ . Show your derivation.

2. (10pts) Assume  $R2 = 300 - R1$ . Show  $V1$  and  $I$  as a function of  $R1$  (same range). Show your derivation.

## Question 2

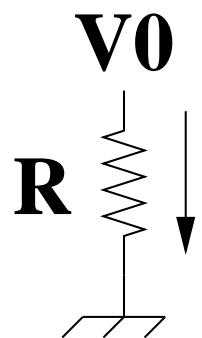

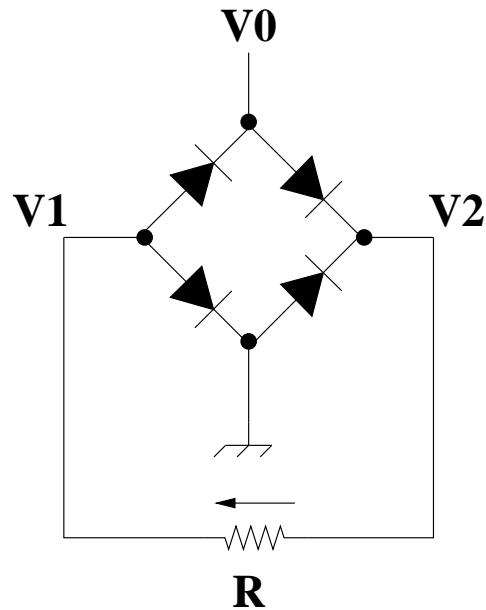1. (10pts) Consider the above circuit. Assume  $R = 500\Omega$ . Show  $IR$  as a function of  $V_0$ . Show your derivation.



2. (20pts) Consider the above circuit. Assume  $V_f = 0.5V$  and  $R = 500\Omega$ . Show  $IR$  as a function of  $V_0$ . Show your derivation.

## Question 3

Suppose we want to produce a regular interrupt at a period of approximately  $32.8\text{ ms}$ . Assume that we are using a  $16\text{ MHz}$  crystal for our clock.

1. (5 pts) Which timer should we use?
2. (5 pts) How should we configure this timer?

## Question 4

Suppose we want to produce a regular interrupt at a frequency of  $1.953\text{ KHz}$ . Assume that we are using a  $16\text{ MHz}$  crystal for our clock.

1. (5 pts) Which timer should we use?

2. (5 pts) How should we configure this timer?

## **Question 5 (ALL)**

How much time did you spend on this homework assignment?