


Embedded Systems (CS [45]163)

Homework 4 Solutions

May 5, 2010

Question 1

Consider the following circuit:

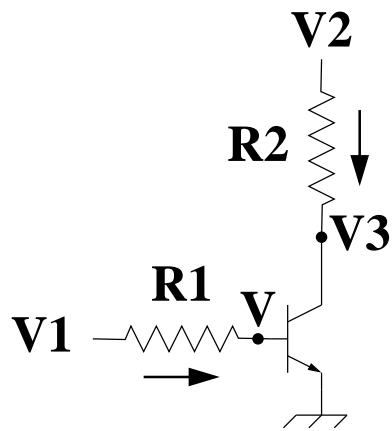


1. (5pts) What is always true no matter the state of the transistor? (i.e., what are the fundamental equations?)

$$\begin{aligned}
 I_2 &= I_{ce} \\
 V_2 - V_3 &= R_2 I_2 \\
 V_1 - V &= R_1 I_1 \\
 I_1 &= I_{be} \\
 0 \leq I_{ce} &\leq gI_{be} \\
 0 &\leq V_3
 \end{aligned}$$

2. (15pts) Assume that $V1 = 5V$, $V_f = 0.7V$, $R1 = 2K\Omega$, $g = 10000$ and $R2 = 10\Omega$. Show I_{CE} , V and $V3$ as a function of $-2 \leq V_2 \leq 20$.

V is always V_f .

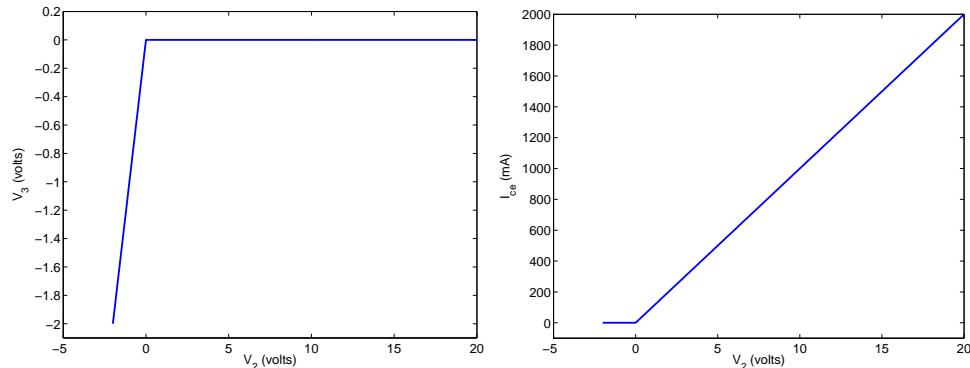


3. (10pts) Assume the same resistances as above and that $V2 = 20V$.
What would $V1$ have to be such that $V3 = 15V$?

In this case:

$$\begin{aligned}I_{ce} &= \frac{V2 - V3}{R2} \\&= 0.5A \\I_{be} &= I_{ce}/g \\&= \frac{V1 - V_f}{R1} \\V_1 &= R_1 I_{ce}/g + V_f \\&= 0.8V\end{aligned}$$

Question 2

Consider the following circuit:

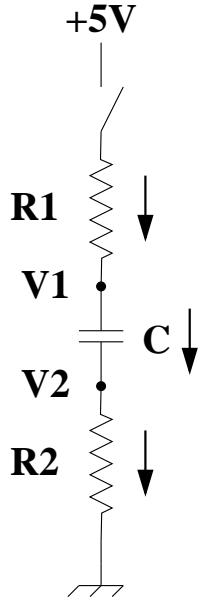

Assume that the switch closes at $t = 0$ and that $V1(0) = V2(0) = 0V$.
Define $V = V_1 - V_2$

1. (10pts) What are the fundamental equations that determine the behavior of this circuit?

$$\begin{aligned}
I_{R1} &= I_C \\
I_{R2} &= I_C \\
C \frac{d(V_1 - V_2)}{dt} &= I_C \\
V_2 - 0 &= R_2 I_{R2} \\
5 - V_1 &= R_1 I_{R1}
\end{aligned}$$

(this latter equation is only true when the switch is closed)

2. (10pts) Derive an equation for I_C in terms of V , R_1 , and R_2 .

$$\begin{aligned} V_1 - 5 - V_2 &= -R_1 I_{R1} - R_2 I_{R2} \\ V_1 - V_2 - 5 &= -I_C (R_1 + R_2) \\ I_C &= \frac{5 - V}{R_1 + R_2} \end{aligned}$$

3. (20pts) Derive an equation for $V(t)$. Hint: V_1 and V_2 should drop out of the equations.

$$\begin{aligned} C \frac{dV}{dt} &= \frac{5 - V}{R_1 + R_2} \\ C(R_1 + R_2) \frac{dV}{5 - V} &= dt \end{aligned}$$

Take $u = 5 - V$. Therefore: $du = -dV$.

$$C(R_1 + R_2) \frac{du}{u} = -dt$$

Integrate both sides:


$$\begin{aligned} \int_{u(0)}^{u(T)} C(R_1 + R_2) \frac{du}{u} &= \int_0^T -dt \\ C(R_1 + R_2) \int_{u(0)}^{u(T)} \frac{du}{u} &= - \int_0^T dt \\ C(R_1 + R_2) \ln(u) \Big|_{u(0)}^{u(T)} &= -t \Big|_0^T \\ C(R_1 + R_2) \ln \left(\frac{u(T)}{u(0)} \right) &= -T \\ \ln \left(\frac{5 - V(T)}{5 - V(0)} \right) &= \frac{-T}{C(R_1 + R_2)} \\ \frac{5 - V(T)}{5 - V(0)} &= e^{-\frac{T}{C(R_1 + R_2)}} \\ V(T) &= 5 - (5 - V(0)) e^{-\frac{T}{C(R_1 + R_2)}} \\ V(T) &= 5 - 5 e^{-\frac{T}{C(R_1 + R_2)}} \end{aligned}$$

4. (10pts) Derive equations for $V_1(t)$ and $V_2(t)$.

$$\begin{aligned}
 V_2 &= R_2 I_{R2} \\
 &= R_2 I_C \\
 &= (5 - V) \frac{R_2}{R_1 + R_2} \\
 V_1 &= 5 - R_1 I_{R1} \\
 &= 5 - R_1 I_C \\
 &= 5 - (5 - V) \frac{R_1}{R_1 + R_2}
 \end{aligned}$$


(and we already know $V(t)$)

For $C = 1\mu F$, $R1 = 100\Omega$, and $R2 = 200\Omega$:

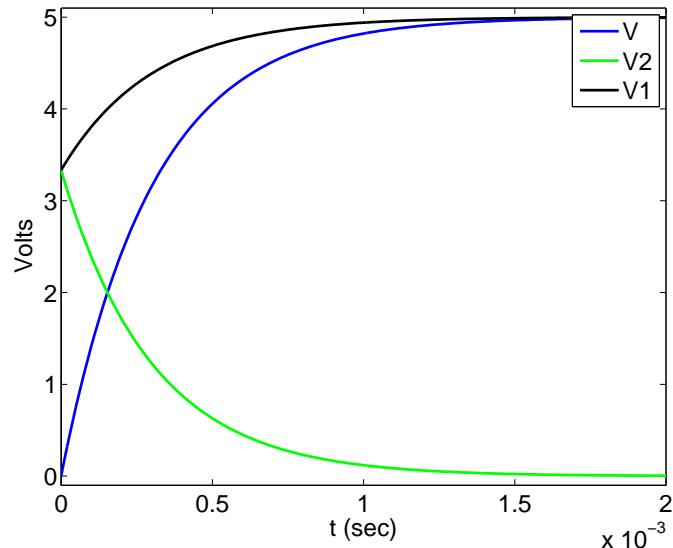

Question 3

Consider the following circuit:

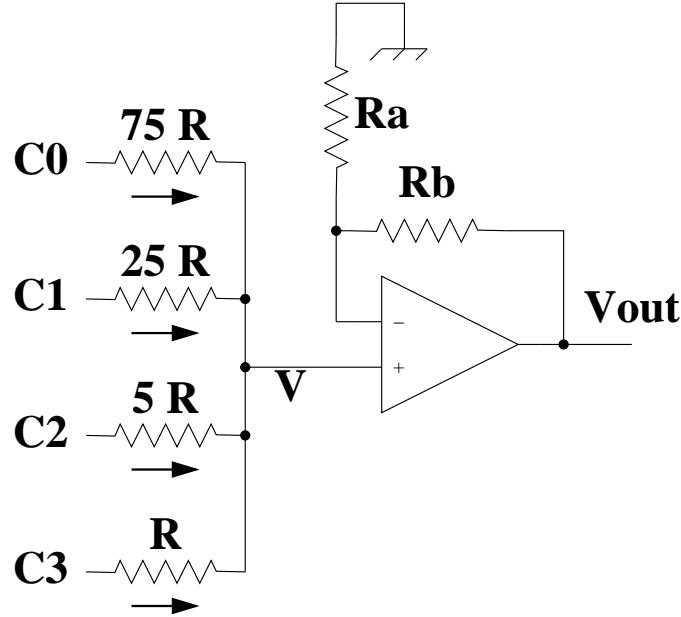

1. (10 pts) What are the fundamental equations that determine V and other associated unknown variables (for the left-hand-side of the circuit).

For each resistor:

$$5C_i - V = 5^{3-i}RI_i$$

except the last:

$$5C_0 - V = 75RI_0$$

Kirchhoff's current law (we can assume that the leg to the op amp is carrying zero current):

$$\sum_{i=0}^3 I_i = 0$$

2. (10 pts) Derive an equation for V .

$$\begin{aligned}
\frac{5C_0 - V}{75R} + \sum_{i=1}^3 \frac{5C_i - V}{5^{3-i}R} &= 0 \tag{1} \\
\frac{5C_0}{75} + \sum_{i=1}^3 \frac{5C_i}{5^{3-i}} &= \frac{V}{75} + \sum_{i=1}^3 \frac{V}{5^{3-i}} \\
5 \left(\frac{C_0}{75} + \sum_{i=1}^3 \frac{C_i}{3^{3-i}} \right) &= V \left(\frac{1}{75} + \sum_{i=1}^3 \frac{1}{5^{3-i}} \right) \\
V &= 5 \left(\frac{C_0}{75} + \sum_{i=1}^3 \frac{C_i}{5^{3-i}} \right) / \left(\frac{1}{75} + \sum_{i=1}^3 \frac{1}{5^{3-i}} \right) \\
&= \frac{5}{94} (C_0 + 3C_1 + 15C_2 + 75C_3)
\end{aligned}$$

3. (10 pts) Assume that $R_a = 100\Omega$ and $R_b = 300\Omega$. Show an equation for V_{out} in terms of V .

Assume V_- is the input to the negative side of the op amp.

Our voltage divider gives us:

$$V_- = V_{out} \frac{R_a}{R_a + R_b}$$

The op amp gives us:

$$V_{out} = \beta(V - V_-)$$

Combining gives us:

$$\begin{aligned}
V_{out} &= \beta \left(V - V_{out} \frac{R_a}{R_b + R_a} \right) \\
V_{out} \left(1 + \beta \frac{R_a}{R_b + R_a} \right) &= \beta V \\
V_{out} &= \frac{\beta V}{1 + \beta \frac{R_a}{R_b + R_a}}
\end{aligned}$$

For large β , this gives us:

$$\begin{aligned} V_{out} &\approx \frac{R_b + R_a}{R_a} V \\ &= 4V \end{aligned}$$

4. (10 pts) Show V_{out} as a function of the binary number C . (show a graph)

