

# Input/Output Systems

Processor needs to communicate with other devices:

- Receive signals from sensors
- Send commands to actuators
- Or both (e.g., disks, audio, video devices)

# I/O Systems

Communication can happen in a variety of ways:

- Binary parallel signal (e.g., project 1)
- Analog
- Serial signals

# An Example: SICK Laser Range Finder

- Laser is scanned horizontally
- Using phase information, can infer the distance to the nearest obstacle
- Resolution: ~.5 degrees, 1 cm
- Can handle full 180 degrees at 20 Hz



# Serial Communication

- Communicate a set of bytes using a single signal line
- We do this by sending one bit at a time:
  - The value of the first bit determines the state of a signal line for a specified period of time
  - Then, the value of the 2<sup>nd</sup> bit is used
  - Etc.

# Serial Communication

The sender and receiver must have some way of agreeing on when a specific bit is being sent

- Typically, each side has a clock to tell it when to write/read a bit
- In some cases, the sender will also send a clock signal (on a separate line)
- In other cases, the sender/receiver will first synchronize their clocks before transfer begins

# Asynchronous Serial Communication

- The sender and receiver have their own clocks, which they do not share
- This reduces the number of signal lines
- Bidirectional transmission, but the two halves do not need to be synchronized in time


But: we still need some way to agree that data is valid. How?

# Asynchronous Serial Communication

How can the two sides agree that the data is valid?

- Must both be operating at essentially the same transmit/receive frequency
- A data byte is prefaced with a bit of information that tells the receiver that data is coming
- The receiver uses the arrival time of this **start bit** to synchronize its clock

# A Typical Data Frame

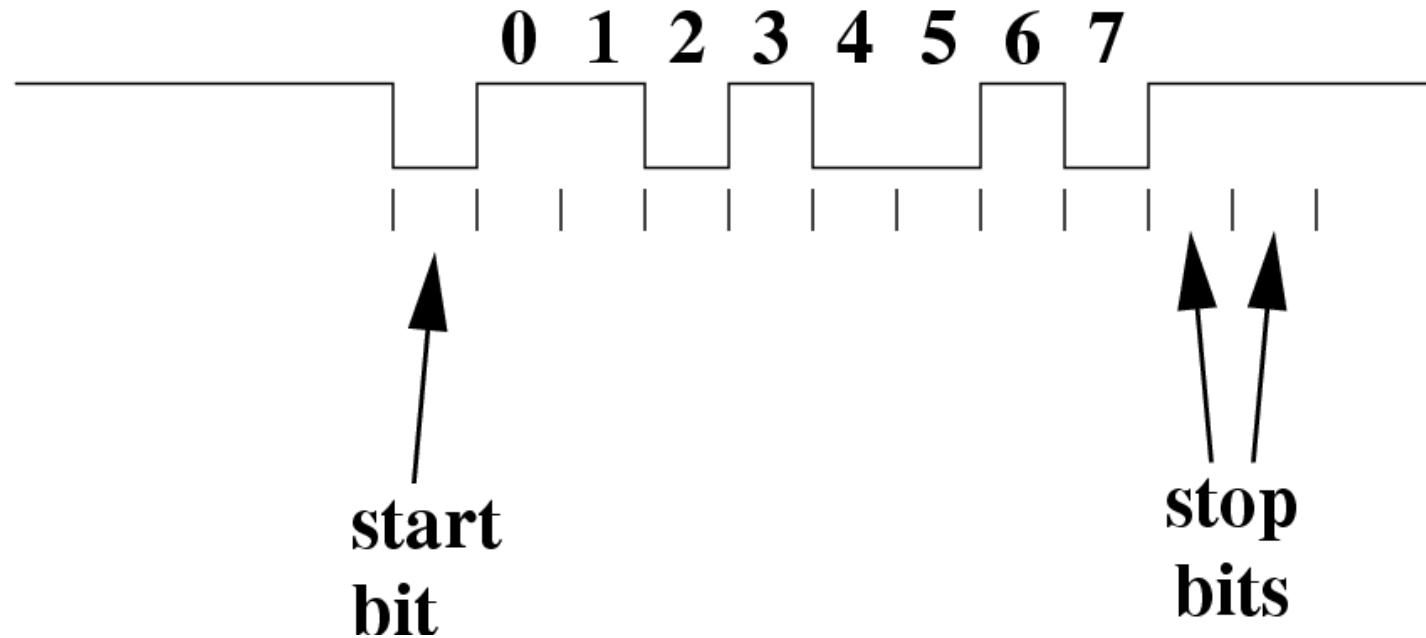

The stop bits allow the receiver to immediately check whether this is a valid frame

- If not, the byte is thrown away

# Data Frame Handling

Most of the time, we do not personally deal with the data frame level. Instead, we rely on:

- Hardware solutions: Universal Asynchronous Receiver Transmitter (UART)
  - Very common in computing devices
- Software solutions in libraries

# One Standard: RS232-C

Defines a logic encoding standard:

- “High” is encoded with a voltage of -5 to -15 (-12 to -13V is typical)
- “Low” is encoded with a voltage of 5 to 15 (12 to 13V is typical)

# RS232-C

Originally intended to connect:

- Data Terminal Equipment (DTE)
  - Teletypes
- to Data Communication Equipment (DCE)
  - Modems

Now that we are connecting a computer to some peripheral, it is not always clear which is the DTE and which is the DCE

# RS232-C

Defines a pin assignment standard. For example, with the DB-9 connectors:

- Pin 2: receive (to DTE from DCE)
- Pin 3: transmit (from DTE to DCE)
- Pin 5: common (ground)

Also common to have DB-25 connectors (older standard)

# RS232 on the Mega8

Our mega 8 has a Universal, Asynchronous serial Receiver/Transmitter (UART)

- Handles all of the bit-level manipulation
- You only have to interact with it on the byte level

# Mega8 UART C Interface

OUlib support:

`ioinit()` : initialize the port @9600 bits per second

`getchar()` : receive a character

`kbhit()` : is there a character in the buffer?

`putchar()` : put a character out to the port

See the Atmel HOWTO

# Character Representation


- A “char” is just an 8-bit number
- In some cases, we just interpret it differently.
- But: we can still perform mathematical operations on it

# Character Representation: ASCII

Andrew H. Fag  
Time System


Binary	Dec	Hex	Glyph
010 0000	32	20	SP
010 0001	33	21	!
010 0010	34	22	"
010 0011	35	23	#
010 0100	36	24	\$
010 0101	37	25	%
010 0110	38	26	&
010 0111	39	27	'
010 1000	40	28	(
010 1001	41	29	)
010 1010	42	2A	*
010 1011	43	2B	+
010 1100	44	2C	,
010 1101	45	2D	-
010 1110	46	2E	.
010 1111	47	2F	/
011 0000	48	30	0
011 0001	49	31	1
011 0010	50	32	2
011 0011	51	33	3
011 0100	52	34	4
011 0101	53	35	5
011 0110	54	36	6
011 0111	55	37	7
011 1000	56	38	8
011 1001	57	39	9
011 1010	58	3A	:
011 1011	59	3B	;
011 1100	60	3C	<
011 1101	61	3D	=
011 1110	62	3E	>
011 1111	63	3F	?
100 0000	64	40	@
100 0001	65	41	A
100 0010	66	42	B
100 0011	67	43	C
100 0100	68	44	D
100 0101	69	45	E
100 0110	70	46	F
100 0111	71	47	G
100 1000	72	48	H
100 1001	73	49	I
100 1010	74	4A	J
100 1011	75	4B	K
100 1100	76	4C	L
100 1101	77	4D	M
100 1110	78	4E	N
100 1111	79	4F	O
101 0000	80	50	P
101 0001	81	51	Q
101 0010	82	52	R
101 0011	83	53	S
101 0100	84	54	T
101 0101	85	55	U
101 0110	86	56	V
101 0111	87	57	W
101 1000	88	58	X
101 1001	89	59	Y
101 1010	90	5A	Z
101 1011	91	5B	[
101 1100	92	5C	\
101 1101	93	5D	]
101 1110	94	5E	^
101 1111	95	5F	_
110 0000	96	60	`
110 0001	97	61	a
110 0010	98	62	b
110 0011	99	63	c
110 0100	100	64	d
110 0101	101	65	e
110 0110	102	66	f
110 0111	103	67	g
110 1000	104	68	h
110 1001	105	69	i
110 1010	106	6A	j
110 1011	107	6B	k
110 1100	108	6C	l
110 1101	109	6D	m
110 1110	110	6E	n
110 1111	111	6F	o
111 0000	112	70	p
111 0001	113	71	q
111 0010	114	72	r
111 0011	115	73	s
111 0100	116	74	t
111 0101	117	75	u
111 0110	118	76	v
111 0111	119	77	w
111 1000	120	78	x
111 1001	121	79	y
111 1010	122	7A	z
111 1011	123	7B	{
111 1100	124	7C	
111 1101	125	7D	}
111 1110	126	7E	~

# Mega8 UART

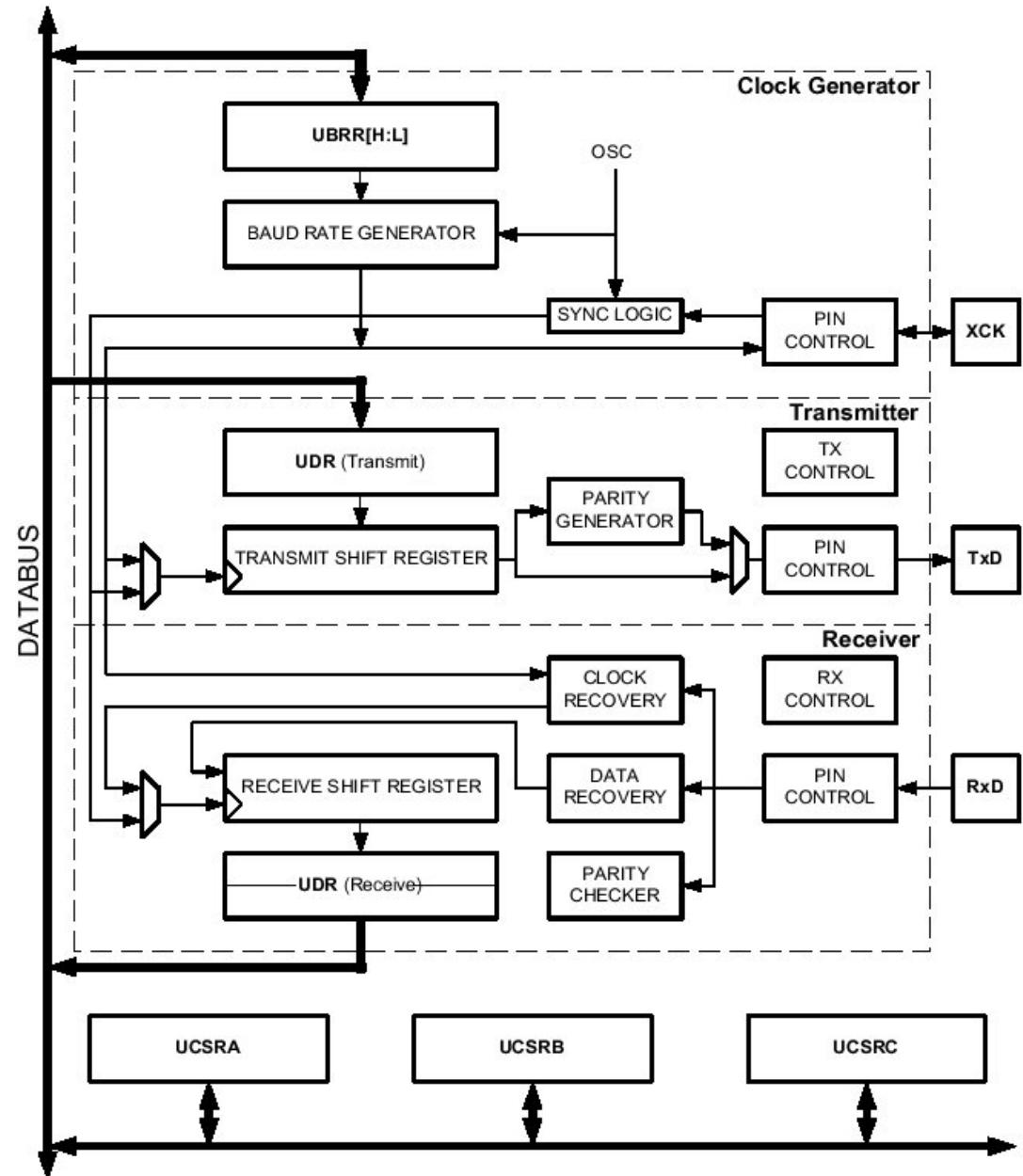


# Mega8 UART

- Transmit pin  
(PD1)

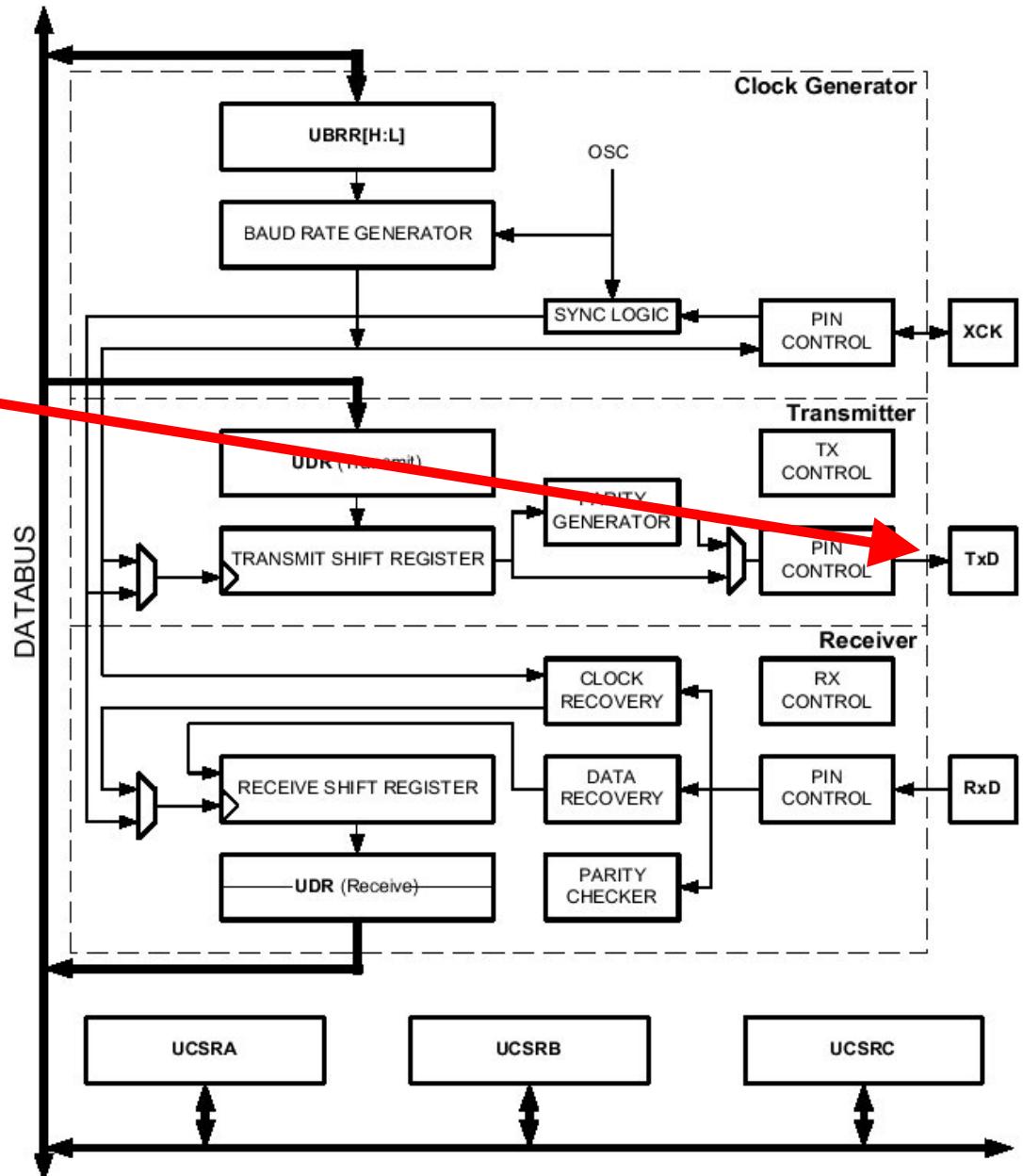
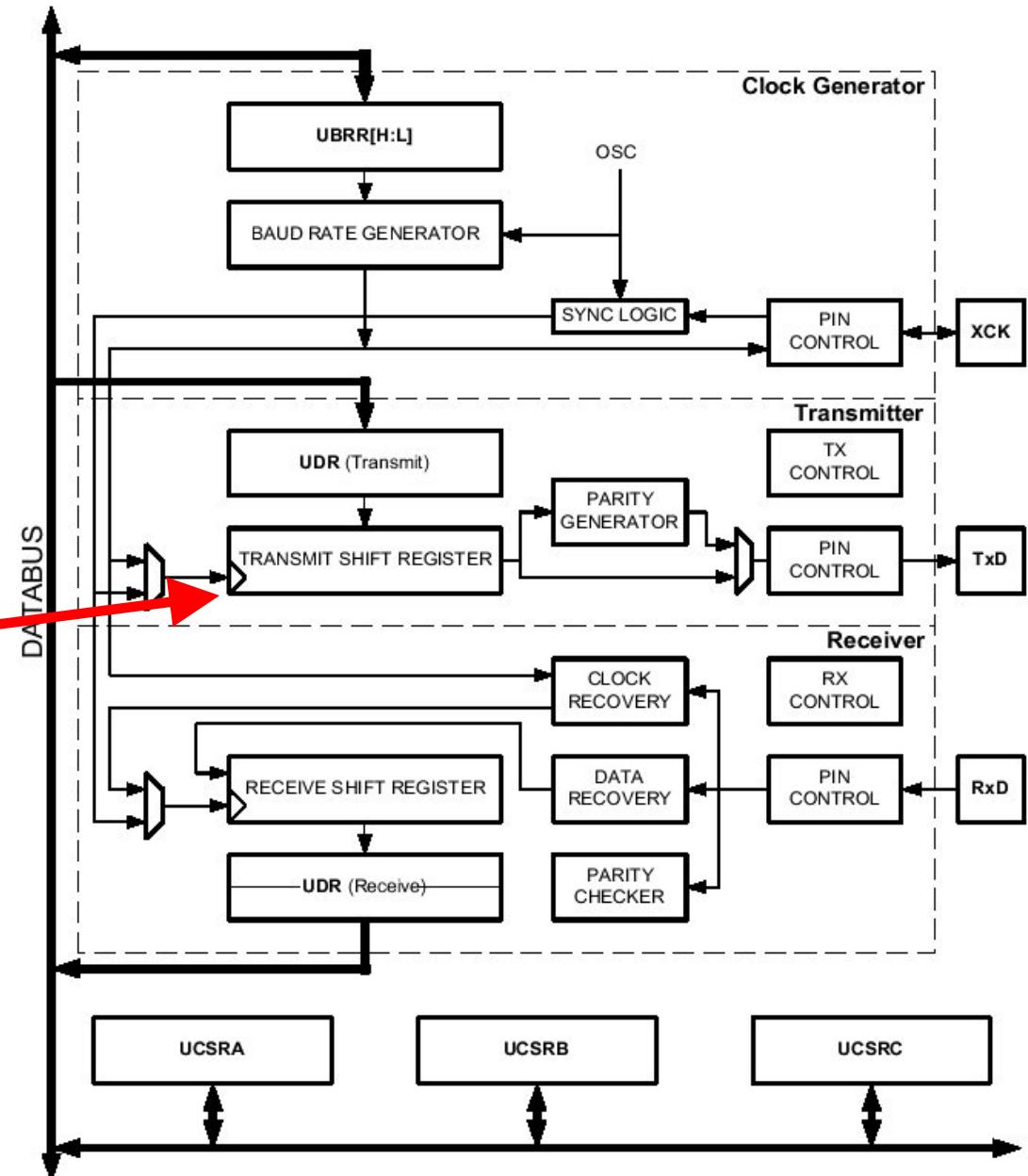
# Mega8 UART

- Transmit pin (PD1)
- Transmit shift register




# Writing a Byte to the Serial Port

```
putchar( 'A' );
```


# Transmit

`putchar ('A' );`

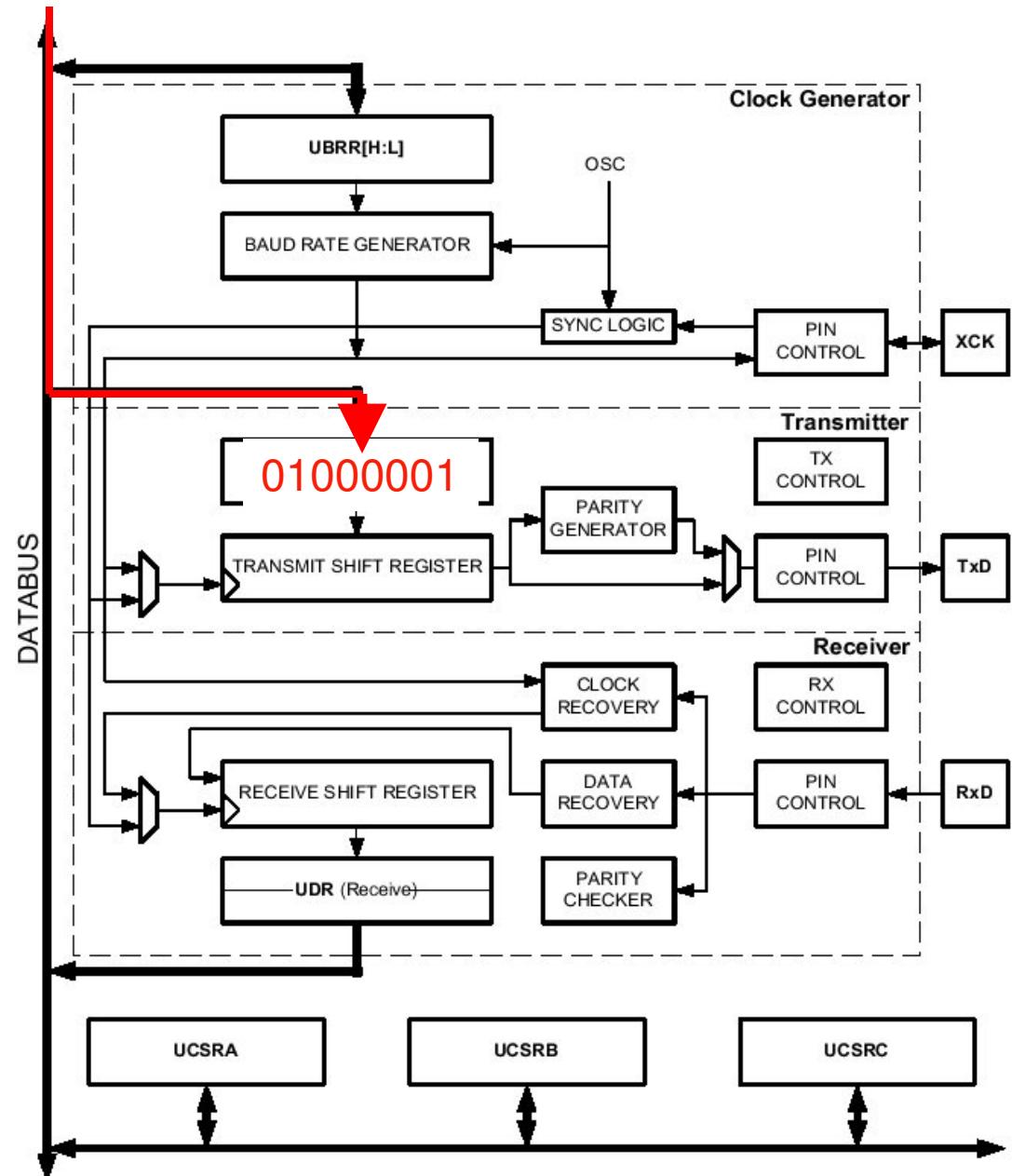

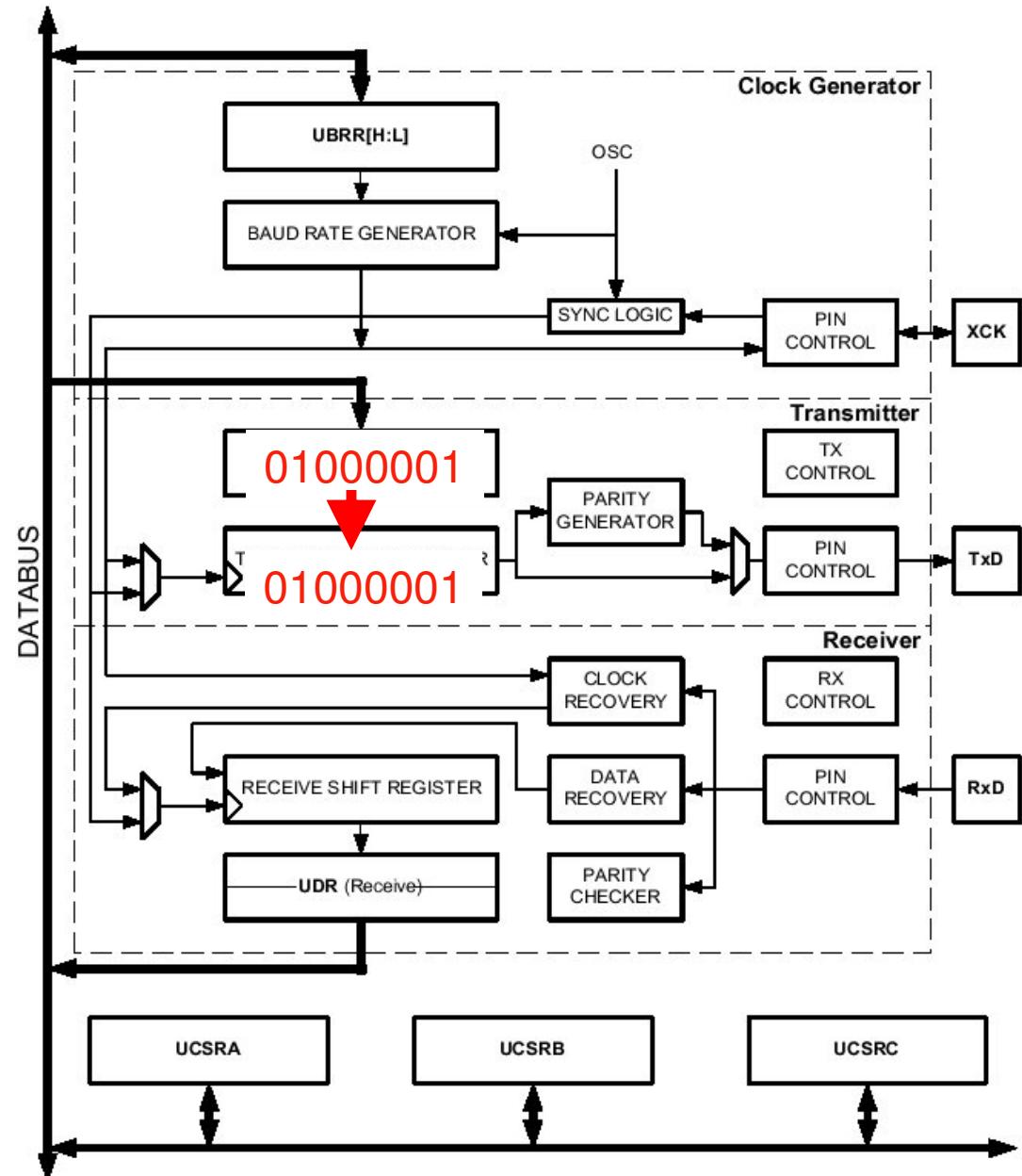
# Transmit

When UART is ready, the buffer contents are copied to the shift register


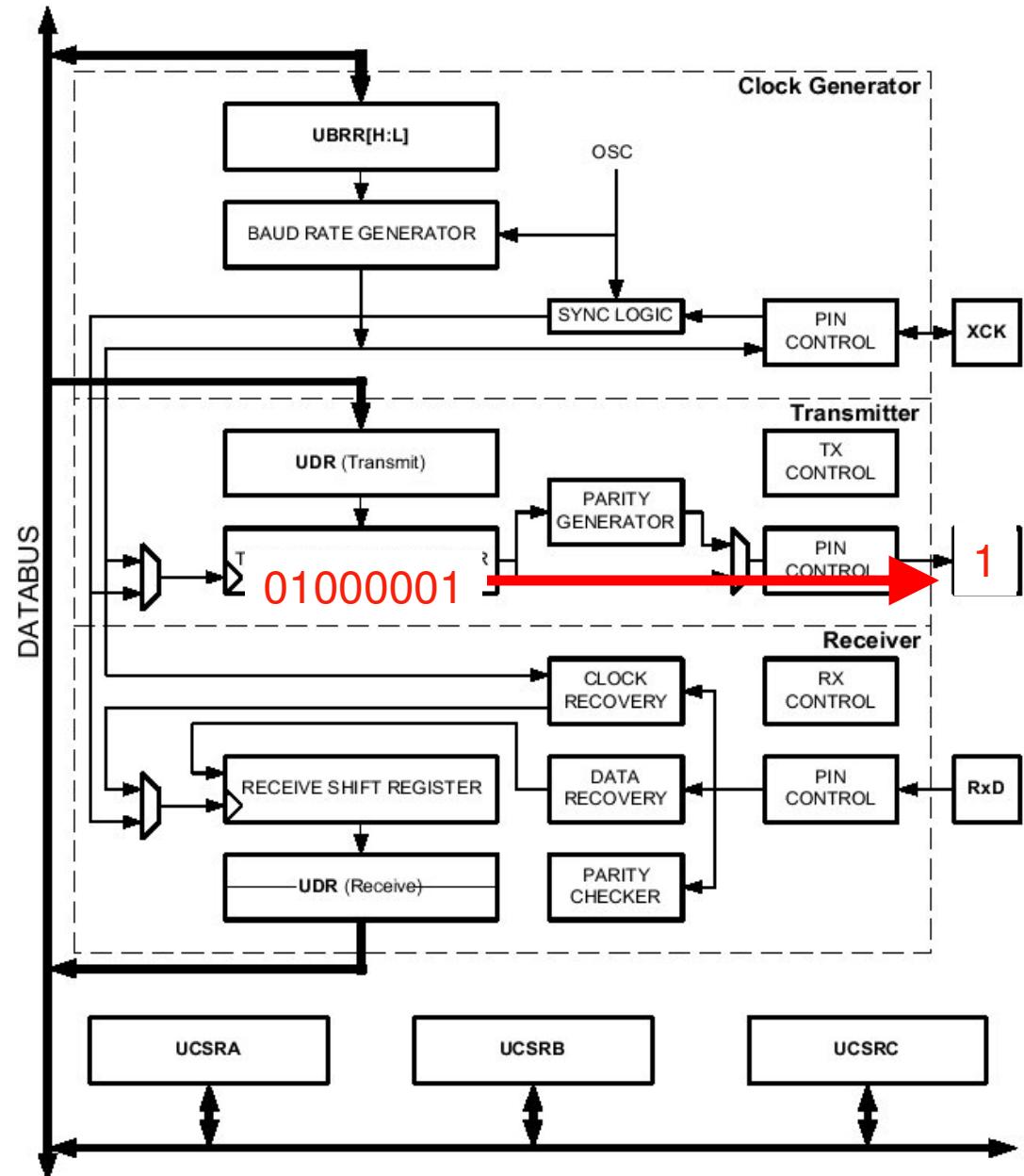
# Transmit


The least significant bit (LSB) of the shift register determines the state of the pin




# Transmit

After a delay, the  
UART shifts  
the values to  
the right


$x$  = value doesn't  
matter

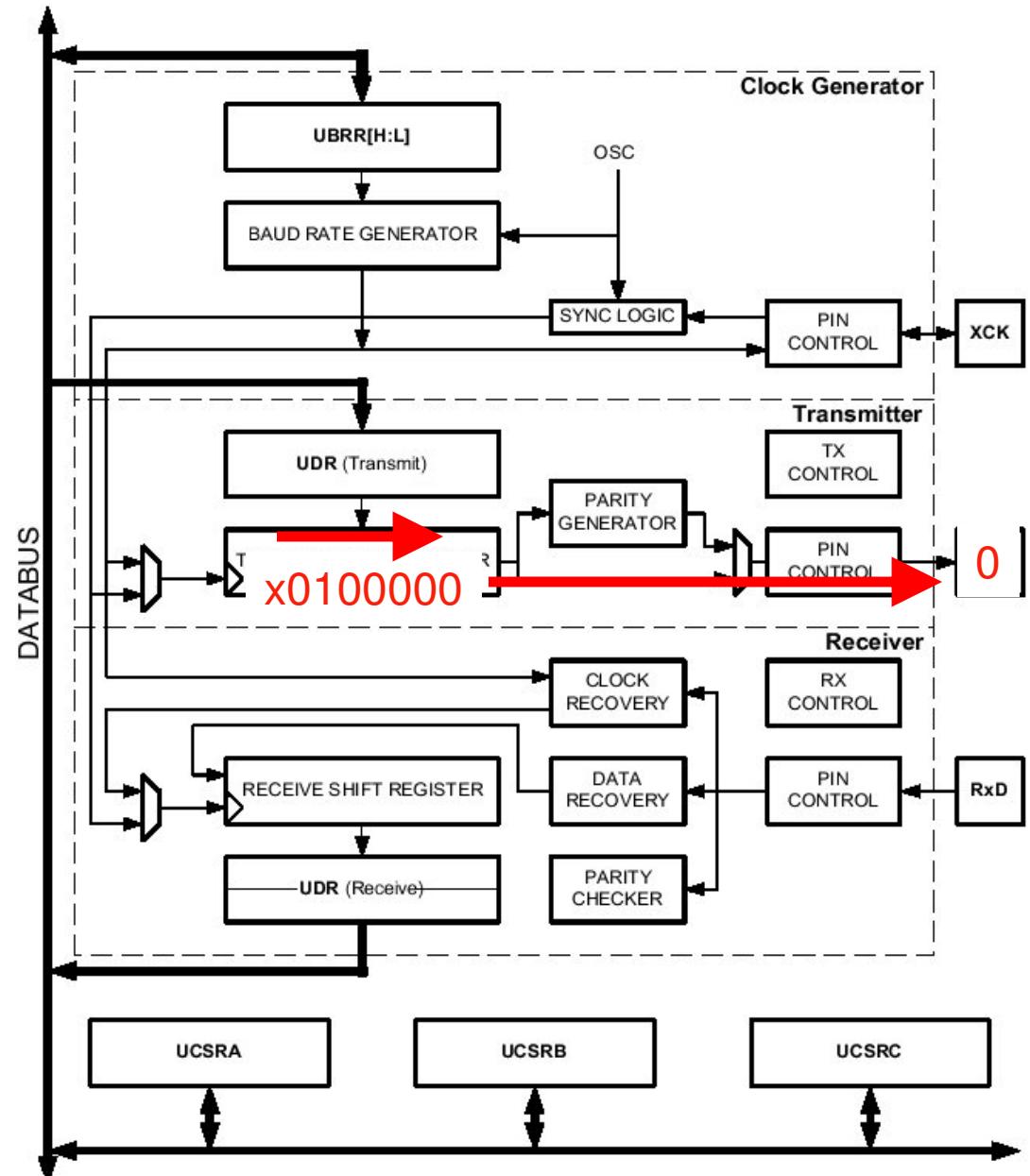

Transmit  
Next shift

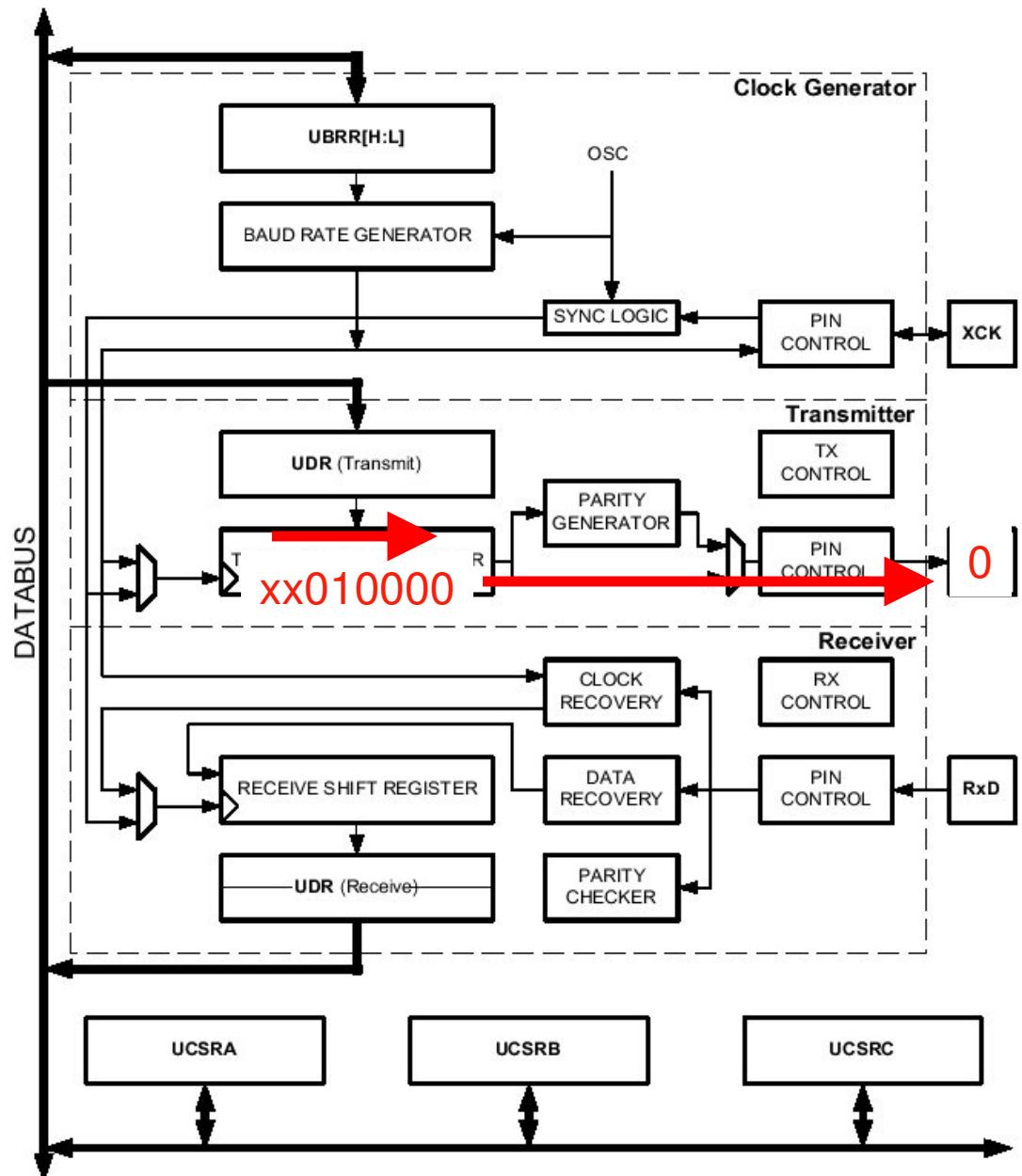

Transmit  
Several shifts  
later...

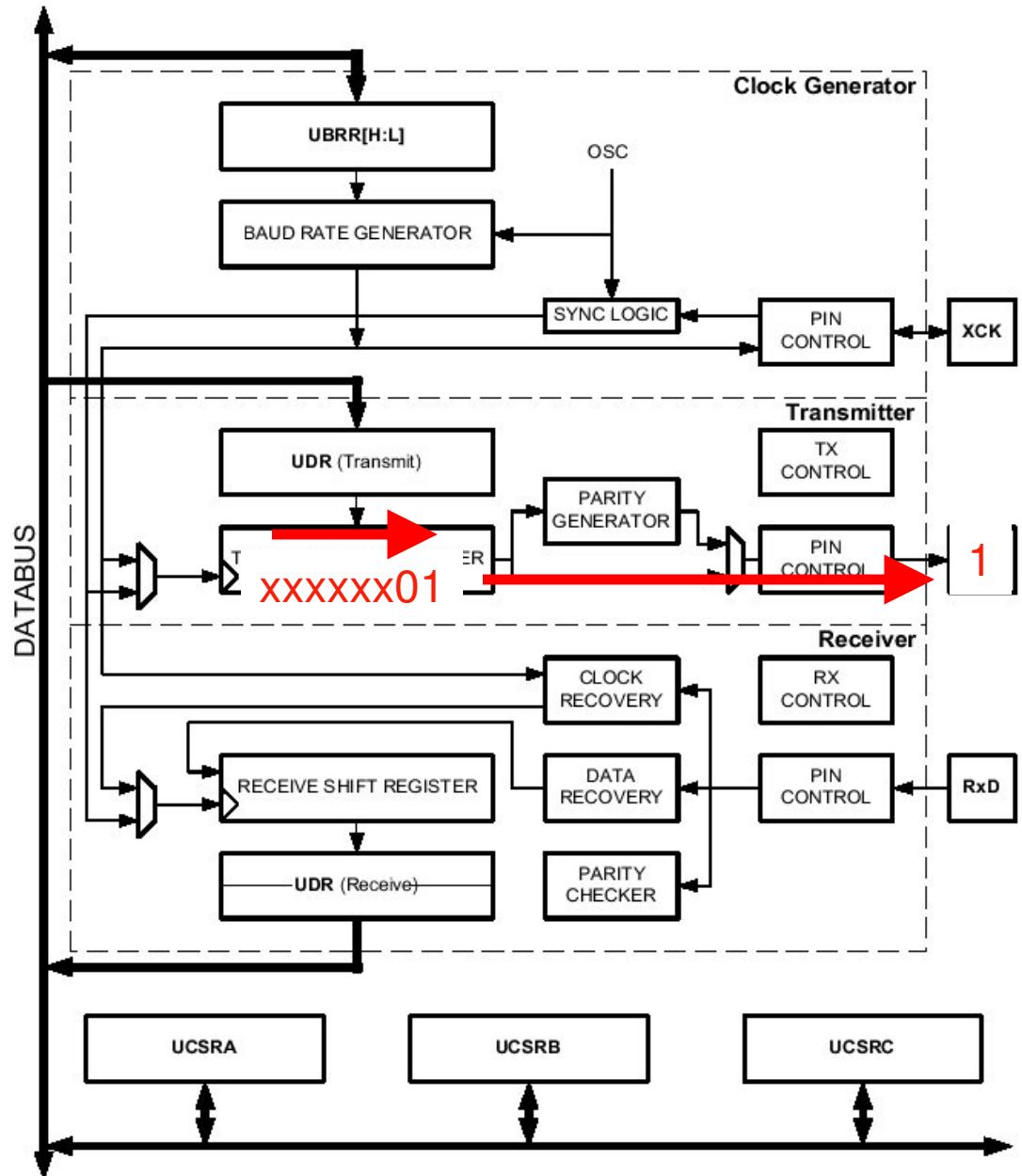

# Last Time

- Bit manipulation
- Serial communication
  - Asynchronous serial
  - Mega8 hardware support

# Today


- More on mega8 serial
- Circuit building in practice
- Project 2

# Administrivia

- Homework 3 is posted (already).
  - Due in one week
- Project 2 out today.
  - Due March 29<sup>th</sup> (but don't wait!)
  - One heli ready now; other units will follow in the next few days
  - Group assignments will be completed tonight:
    - Announcement on D2L


# Receive

- Receive pin (PD0)

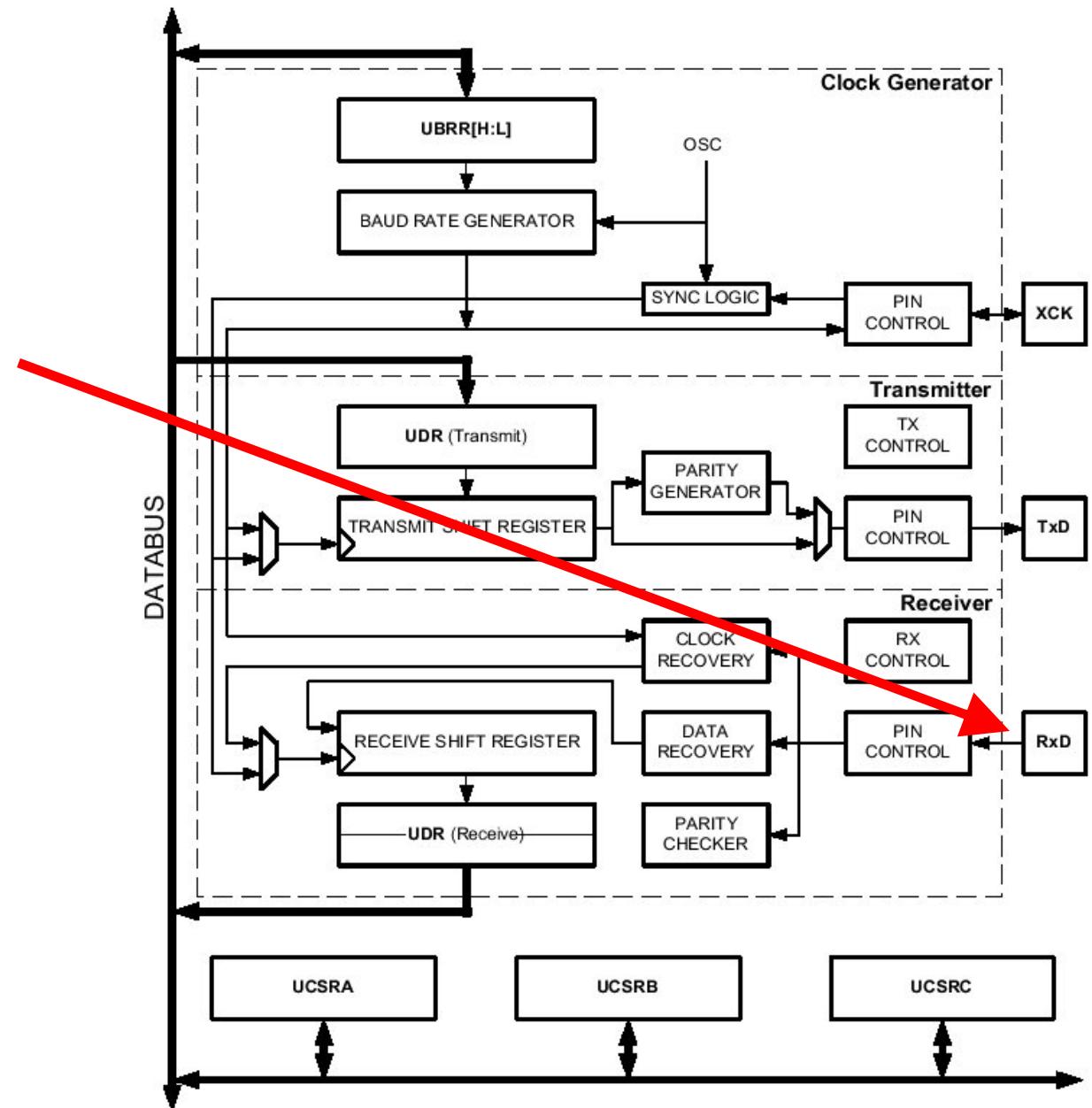

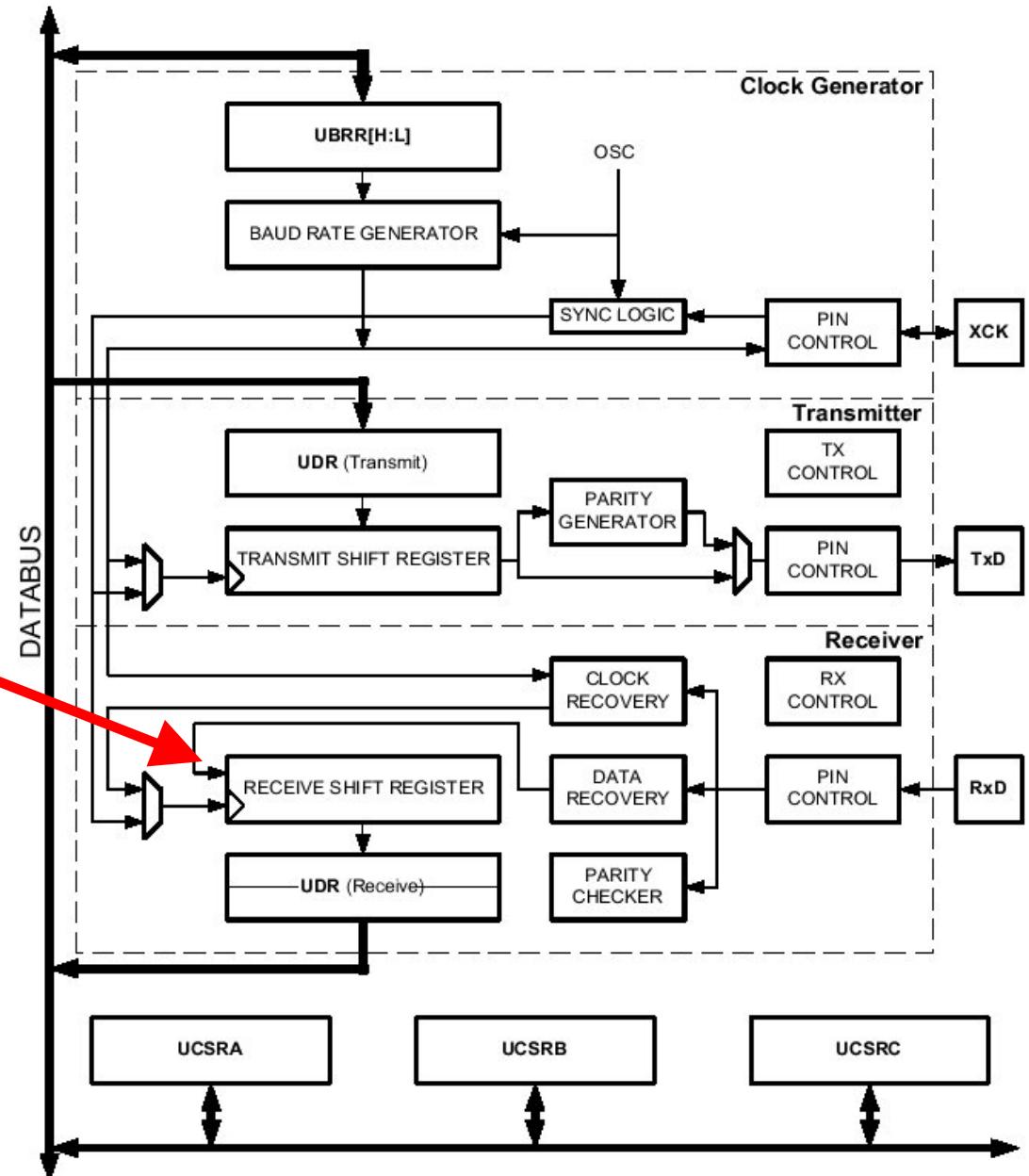
# Receive

- Receive pin (PD0)
- Receive shift register



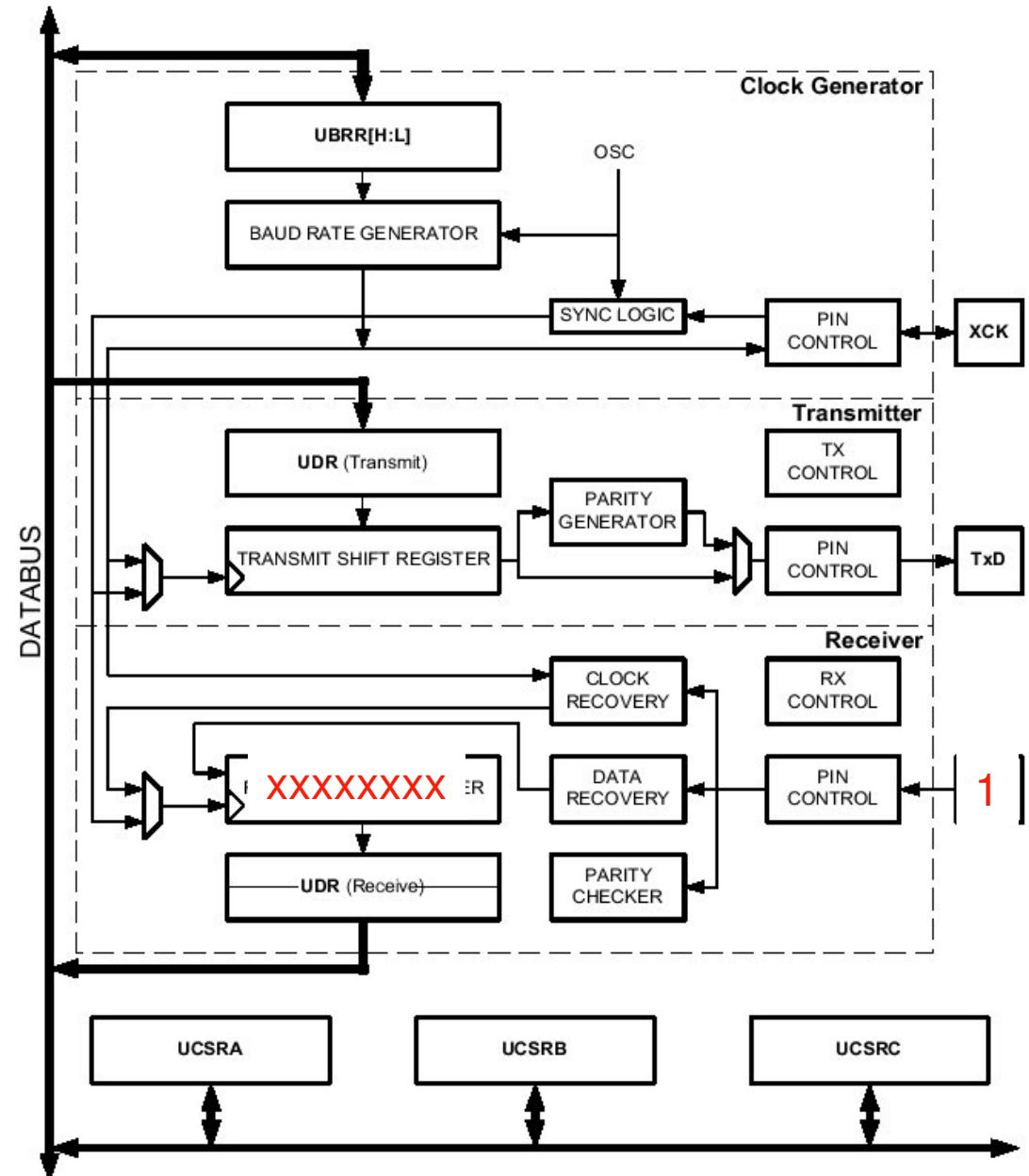
# Receive

- “1” on the pin
- Shift register initially in an unknown state




# Receive

“1” is presented to the shift register

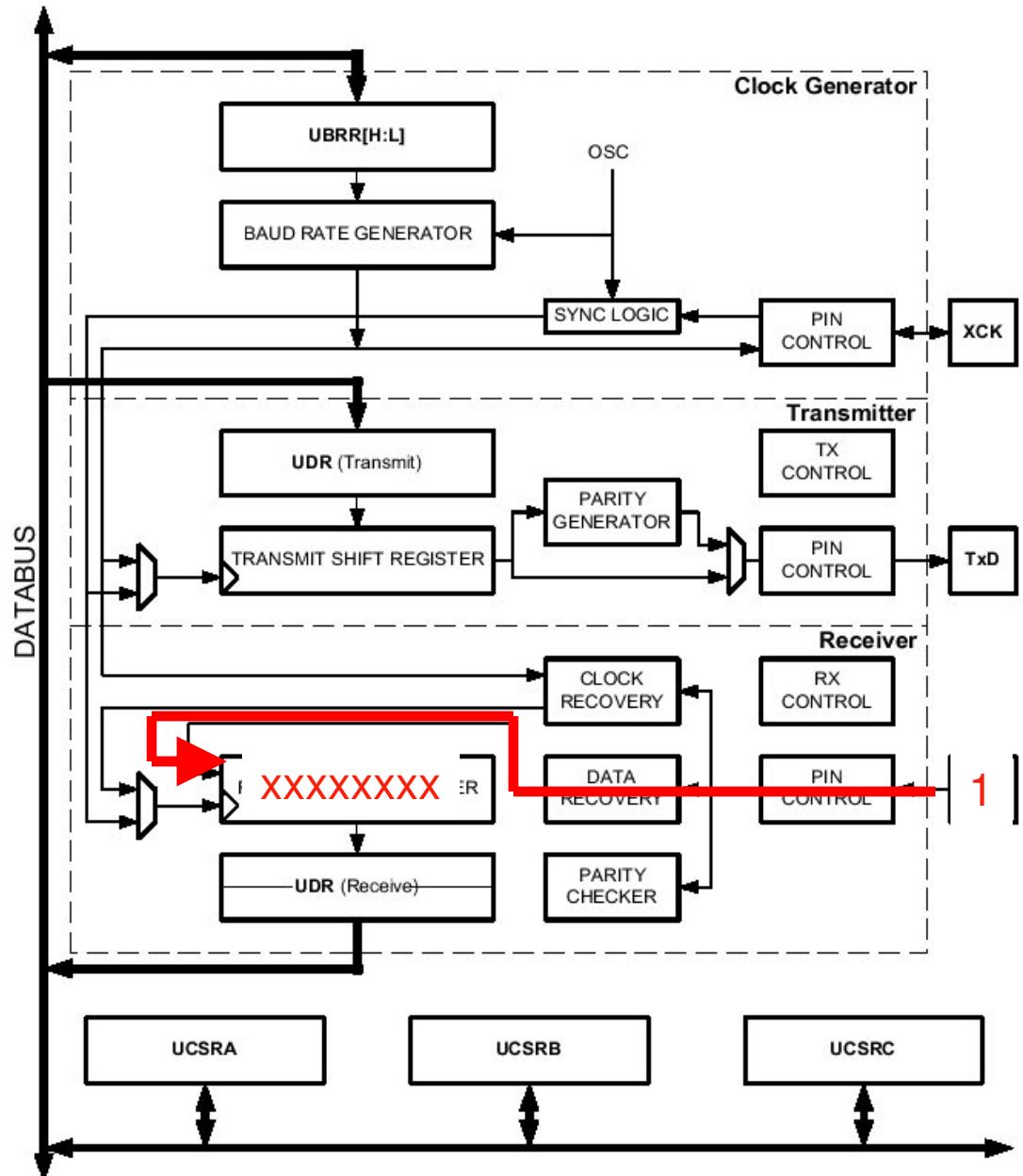

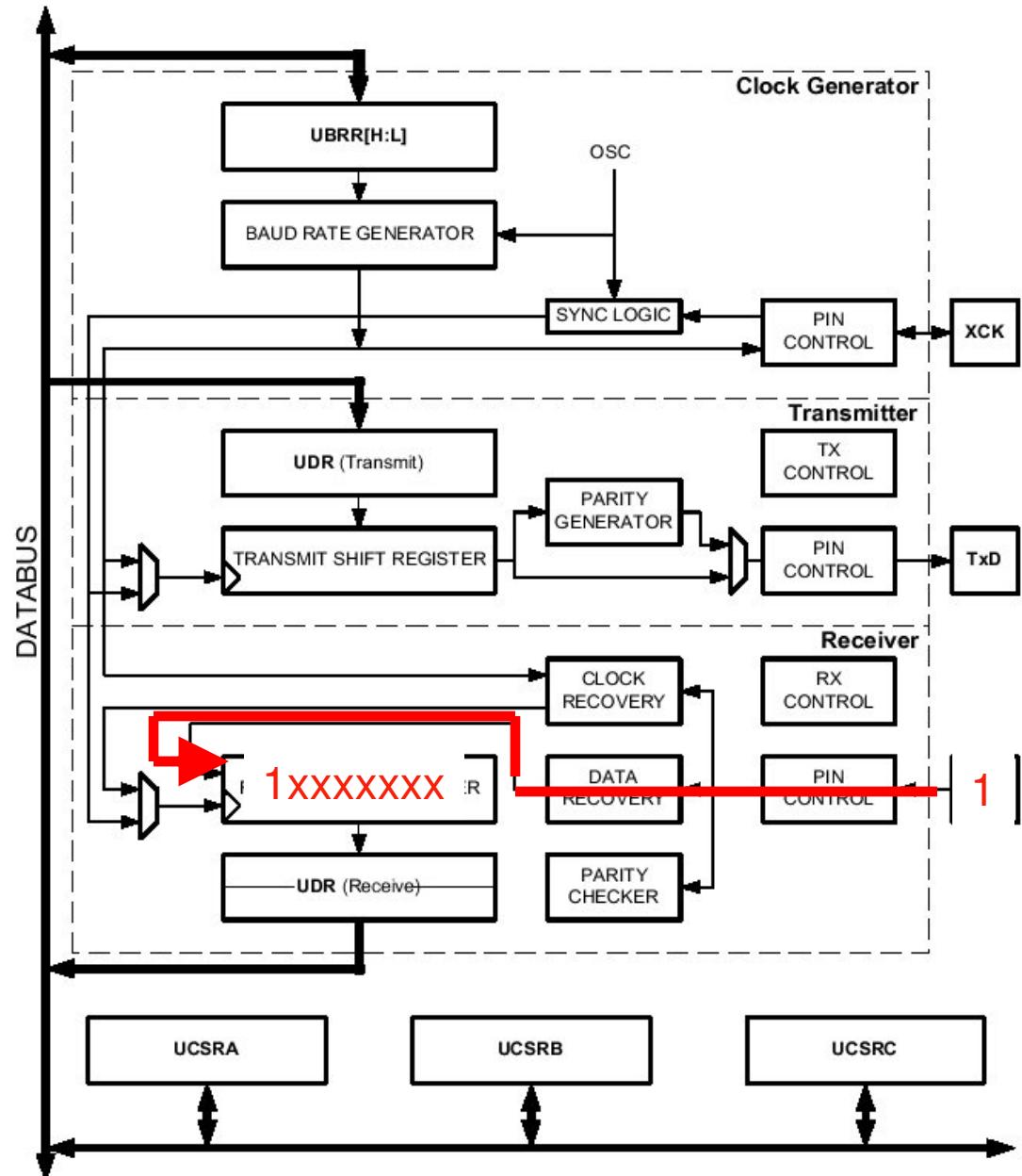
# Receive

“1” is shifted into the **most significant bit** (msb) of the shift register




# Receive

Next bit is shifted in

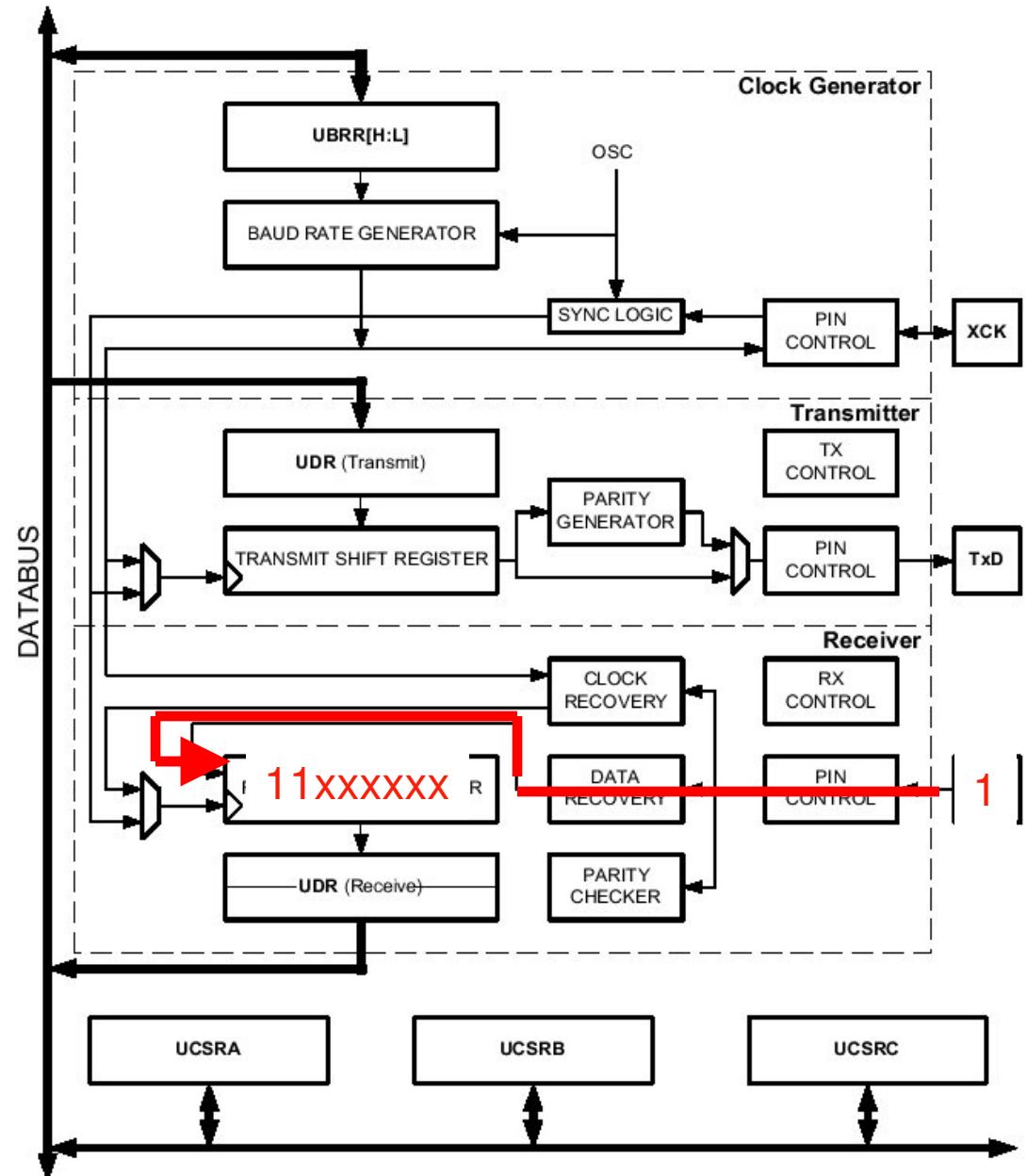


# Receive

And the next bit...

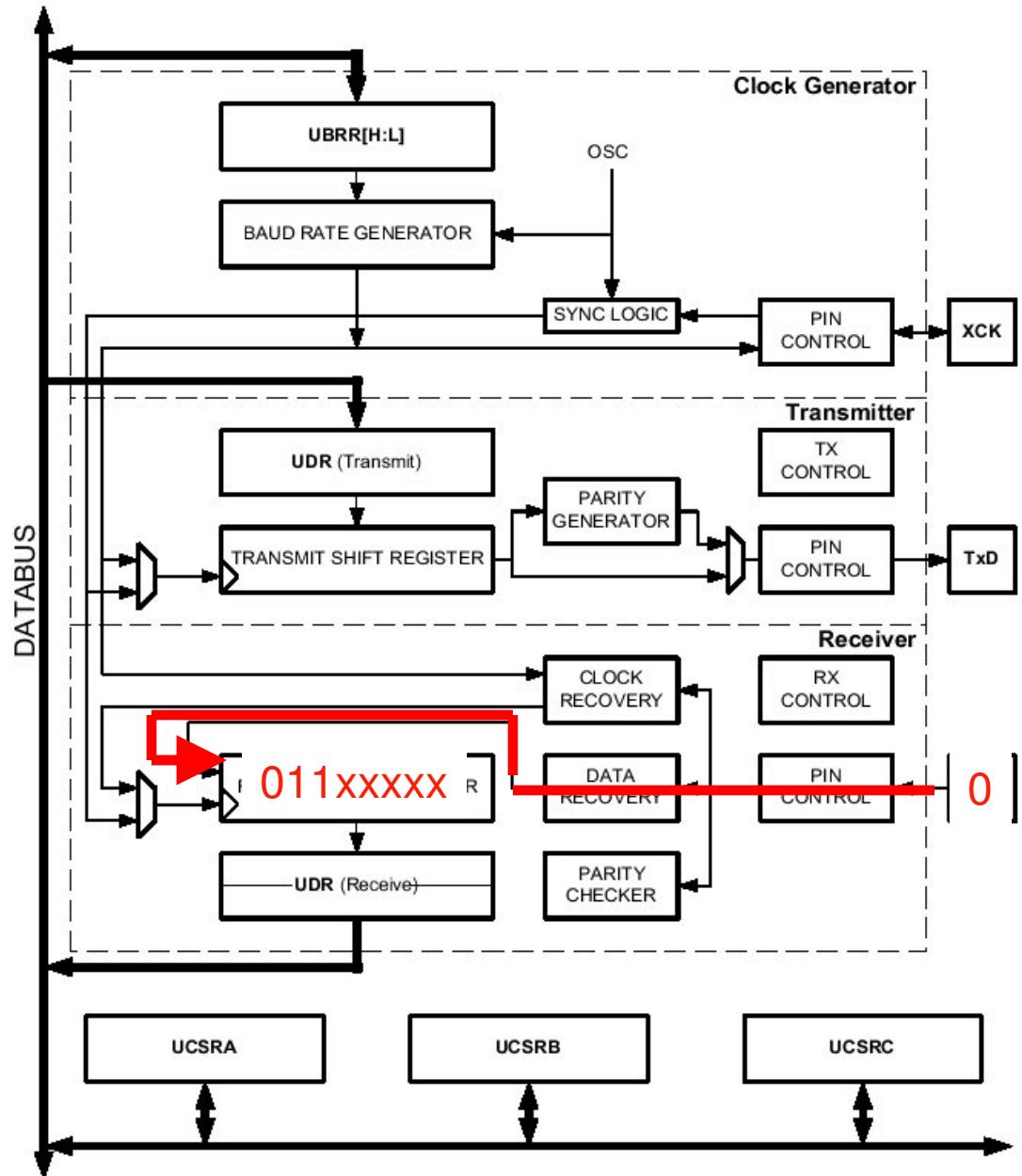


# Receive

## And the 8<sup>th</sup> bit

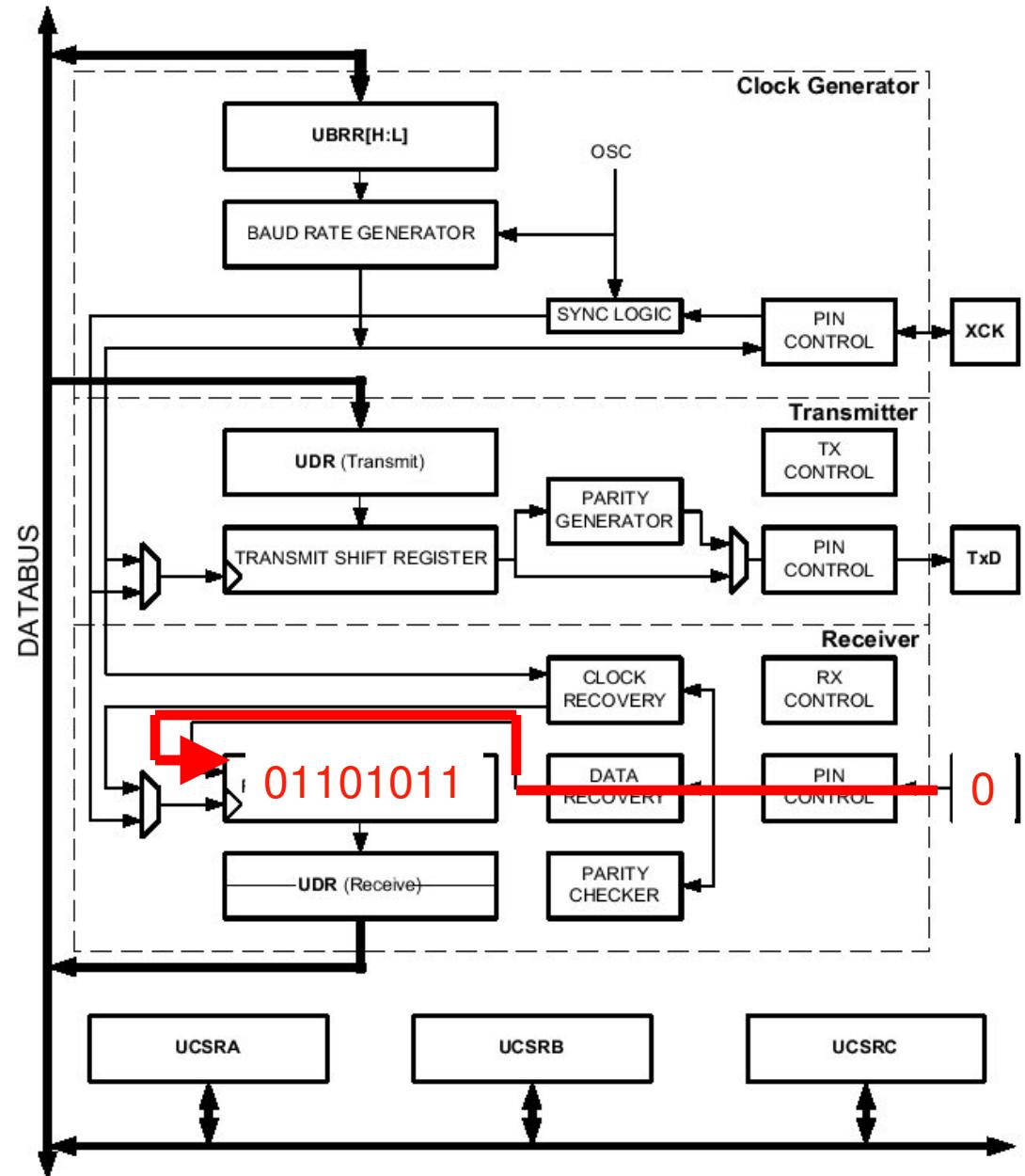
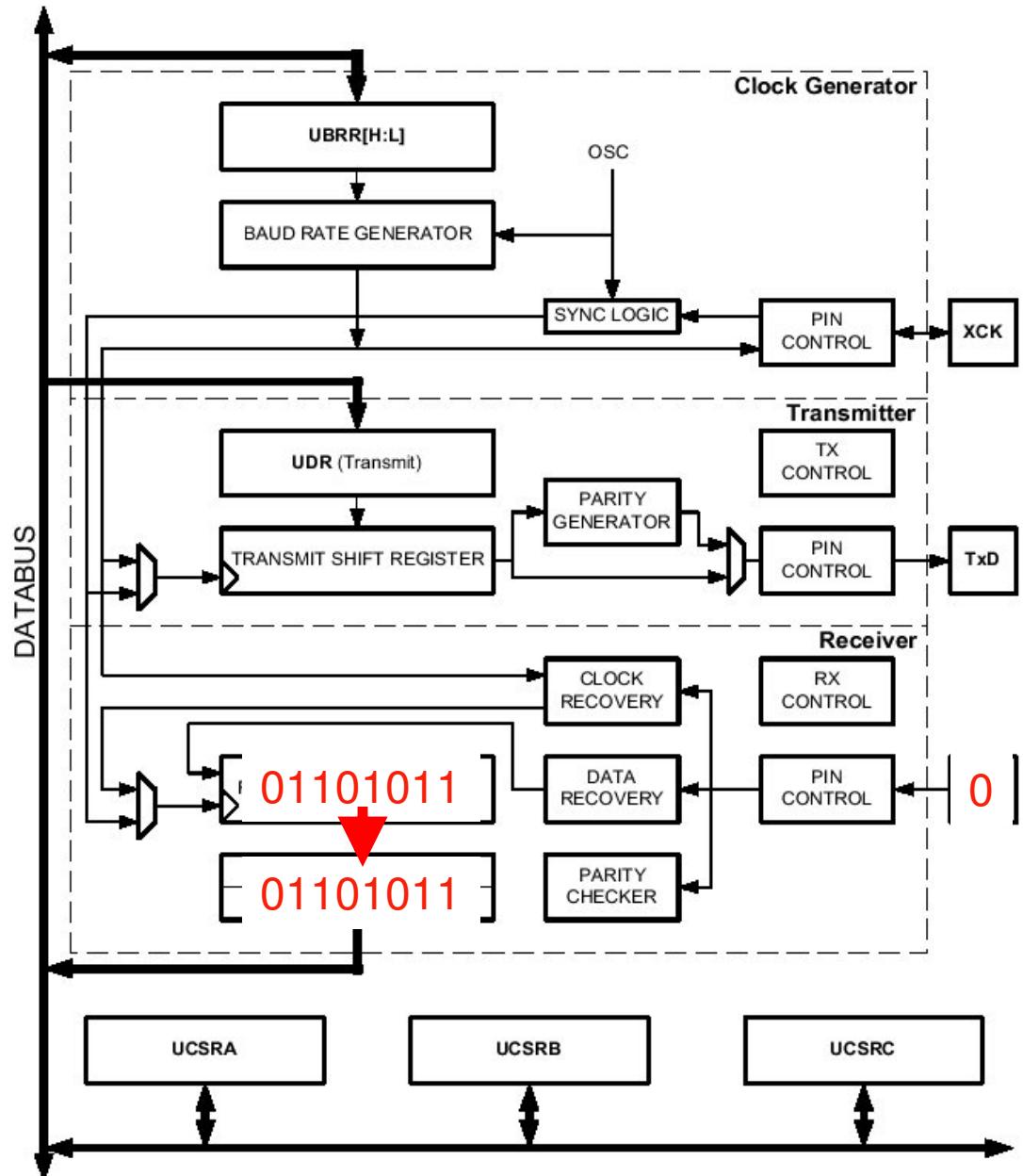
# Receive

Completed byte  
is stored in  
the UART  
buffer




# Reading a Byte from the Serial Port

```
int c;
```

```
c=getchar();
```
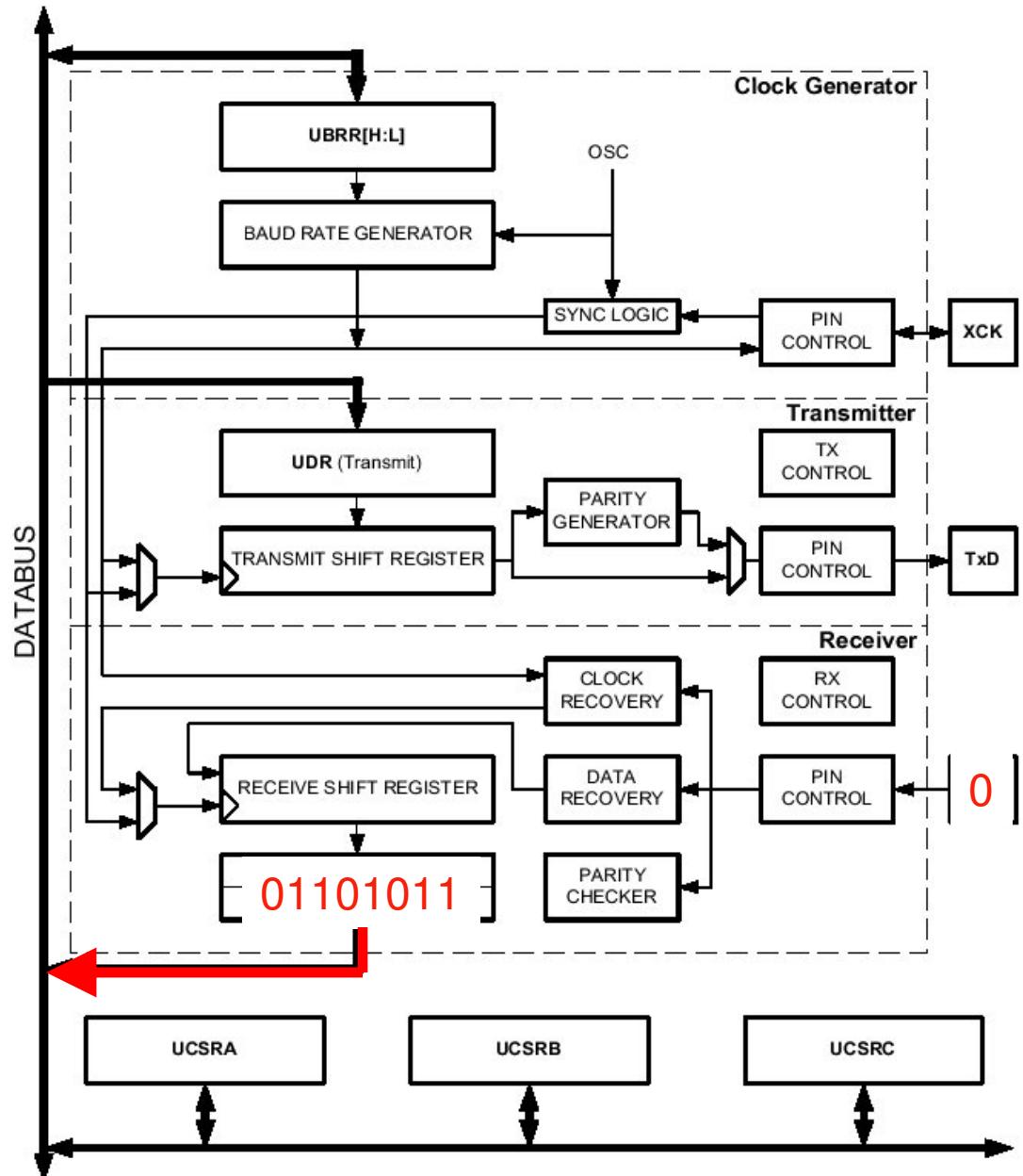
# Receive

getchar()  
retrieves this  
byte from the  
buffer



# Reading a Byte from the Serial Port

```
int c;
```

```
c=getchar();
```

Note: `getchar()` “blocks” until a byte is available

- Will only return with a value once one is available to be returned

# Processing Serial Input

```
int c;  
while(1) {  
    if(kbhit()) {  
        // A character is available for reading  
        c = getchar();  
        <do something with the character>  
    }  
    <do something else while waiting>  
}
```

**kbhit()** tells us whether a byte is ready to be read

# Mega8 UART C Interface

`printf()` : formatted output

`scanf()` : formatted input

See the LibC documentation or the AVR C textbook

# Serial I/O by Polling

```
int c;  
while(1) {  
    if (kbhit()) {  
        // A character is available for reading  
        c = getchar();  
        <do something with the character>  
    }  
    <do something else while waiting>  
}
```